

Analog (Integrated) Circuit Design

Harald Pretl
Johannes Kepler University
harald.pretl@jku.at

Michael Koefinger

Simon Dorrer

2026-10-06

Table of contents

1	Introduction	3
1.1	IHP's SG13G2 130nm CMOS Technology	4
1.2	Schematic Entry Using Xschem	5
1.3	Circuit Simulation Using ngspice	5
1.4	Integrated IC Design Environment (IIC-OSIC-TOOLS)	6
1.5	Setting up the Design Directory	6
1.5.1	Creating Backups	7
1.5.2	Updating the Repository	7
2	First Steps	7
2.1	The Metal-Oxide-Semiconductor Field-Effect-Transistor (MOSFET)	7
2.1.1	Large-Signal MOSFET Model	12
2.1.2	Small-Signal MOSFET Model	14
2.2	Conclusion	19
3	Transistor Sizing Using gm/ID Methodology	20
3.1	MOSFET Characterization Testbench	20
3.2	NMOS Characterization in Saturation	23
3.3	PMOS Characterization in Saturation	31
3.4	Tradeoffs in Saturation	36
3.5	NMOS and PMOS Characterization in Triode	37
3.6	Tradeoffs in Triode	39
4	First Circuit: MOSFET Diode	40
4.1	MOSFET Diode Sizing	42
4.2	MOSFET Diode Large-Signal Behavior	43
4.3	MOSFET Diode Small-Signal Analysis	44
4.4	MOSFET Diode Stability Analysis	46
4.5	MOSFET Diode Noise Calculation	49
4.6	Conclusion	53
5	Common-Source Amplifier	53
5.1	Sense Amplifier Driving 50 Ohm Matched Load	54
6	Current Mirror	57
7	Differential Pair	58
7.1	Differential Operation of the Diffpair	59
7.2	Common-Mode Operation of the Diffpair	60
8	A Basic 5-Transistor OTA	62

8.1	Voltage Buffer with OTA	63
8.2	Large-Signal Analysis of the OTA	64
8.3	Small-Signal Analysis of the OTA	66
8.3.1	OTA Small-Signal Transfer Function	67
8.3.2	OTA Noise	69
8.4	5T-OTA Sizing	71
8.5	5T-OTA Simulation	74
8.6	Component Mismatch	74
8.6.1	MOSFET Mismatch	74
8.6.2	Resistor Mismatch	76
8.6.3	Capacitor Mismatch	76
8.7	5T-OTA Simulation versus PVT and MC	76
8.7.1	PVT Simulation Analysis	79
8.7.2	Monte Carlo Simulation Analysis	79
8.8	OTA Variants	79
9	Cascode Stage	82
9.1	Cascode Output Impedance	84
9.2	Cascode Input Impedance	86
10	Improved Current Mirrors	87
10.1	Low-Voltage Regulated Current Mirror	95
10.2	Current Source Variations Summary	96
10.3	Current Mirror Matching	97
11	Improved (Telescopic) OTA	101
11.1	Sizing the Improved OTA	102
11.2	Designing the Improved OTA	104
11.2.1	Discussion of the OTA Design	105
11.3	Simulation of Improved OTA	106
11.4	Corner Simulation of Improved OTA	108
12	Biasing	110
12.1	Bandgap Reference	111
12.2	Banba Bandgap Reference	116
13	Differential OTAs	118
13.1	Miller Compensation	119
13.2	Common-Mode Regulation	122
13.3	Final Differential OTA	125
13.4	Differential OTA Variants	127
14	An RC-OPAMP Filter	128
15	Summary & Conclusion	128
16	Appendix: Middlebrook's Method	129
17	Appendix: Useful Circuit Theorems	130
17.1	Miller's Theorem	130
17.2	Bode's Noise Theorem	132
18	Appendix: 5T-OTA Small-Signal Output Impedance	132
18.1	Open-Loop Configuration	132
18.2	Closed-Loop Configuration	134
19	Appendix: Linux Cheatsheet	134

20	Appendix: Xschem Cheatsheet	135
21	Appendix: ngspice Cheatsheet	137
21.1	Commands	137
21.2	Options	138
21.3	Convergence Helper	138
21.4	Internal Variables	138
22	Appendix: Circuit Designer's Etiquette	139
22.1	Prolog	139
22.2	Pins	139
22.3	Schematics	140
22.4	Symbols	141
22.5	Design Robustness	141
22.6	Rules for Good Mixed-Signal and RF Circuits	142
22.7	VHDL/Verilog Coding Guide	142
22.8	Further Reading	143
23	Exemplary Examination Questions	144
23.1	MOSFET Fundamentals	144
23.2	gm/ID Sizing Methodology	146
23.3	MOSFET Diode	148
23.4	Current Mirror	149
23.5	Differential Pair	151
23.6	Basic 5-Transistor OTA	152
23.7	Improved (Telescopic) OTA	154
23.8	Cascode Stage	156
23.9	Biasing and Bandgap Reference	157
23.10	Noise Analysis	159
23.11	Mismatch and Variability	160
23.12	Design Problems	162
23.13	Short Conceptual Questions	164
	Bibliography	166

1 Introduction

This is the material for an intermediate-level MOSFET analog circuit design course, held at JKU under course number 336.009 ("KV Analoge Schaltungstechnik").

The course makes heavy use of circuit simulation, using **Xschem** for schematic entry and **ngspice** for simulation. The 130nm CMOS technology **SG13G2** from IHP Microelectronics is used.

Tools and PDK are integrated in the **IIC-OSIC-TOOLS** Docker image, which will be used during the coursework.

! Important

All course material (source code of this document, Jupyter notebooks for calculations, Xschem circuits, etc.) is made publicly available on GitHub (follow this link) and shared under the Apache-2.0 license.

Please feel free to submit pull requests on GitHub to fix errors and omissions!

The production of this document would be impossible without these (and many more) great open-source software products: VS Code, Quarto, Pandoc, TexLive, Jupyter Notebook, Python, Xschem, ngspice, CACE, pygmid, schemdraw, Numpy, Scipy, Matplotlib, Pandas, Git, Docker, Ubuntu, Linux, ...

! Important

Please use the IIC-OSIC-TOOLS image with tag 2026.06 or later!

i Further Reading

These notes are considered to be self-contained, although some explanations are kept short and probably lack depth. To dive into details, there are many excellent textbooks on analog circuit design available. Among them, we can recommend the following ones:

- [1] is a classic book and a definitive read.
- [2] is an excellent introduction into CMOS analog circuit design.
- [3] is a book with a lot of very useful information hard to find elsewhere.
- [4] is a great reference for MOSFET device physics and modeling.
- [5] is the in-depth reference for MOSFET device operation.

Additionally, there are several noteworthy IEEE paper series that we recommend:

- *Shop Talk: What you didn't Learn in School* by Chris Mangelsdorf
- *The Analog Mind* by Behzad Razavi
- *A Circuit for All Seasons* by Behzad Razavi
- *Circuit Intuitions* by Ali Sheikholeslami

Finally, [6] collects fifty variations of two-transistor circuits, ranging from simple standard configurations to ingenious arrangements. It is also available as an interactive web version.

1.1 IHP's SG13G2 130nm CMOS Technology

SG13G2 is the name of a 130nm CMOS technology (strictly speaking BiCMOS) from IHP Microelectronics. It features low-voltage (thin-oxide) core MOSFET, high-voltage (thick-oxide) I/O MOSFET, various types of linear resistors, and 7 layers of Aluminum metallization (5 thin plus 2 thick metal layers). This PDK is open-source, and the complete process specification can be found at SG13G2 process specification. While we will not do layouts in this course, the layout rules can be found at SG13G2 layout rules.

For our circuit design, the most important parameters of the available devices are summarized in the following table. Matching properties are summarized in Table 4.

Table 1: IHP SG13G2 devices

Component		Device Name	Specifications
Low-voltage NMOS	(LV)	<code>sg13_lv_nmos</code>	operating voltage (nom.) $V_{DD} = 1.5\text{ V}$, $L_{\min} = 0.13\text{ }\mu\text{ m}$, $V_{th} \approx 0.5\text{ V}$; isolated NMOS available
Low-voltage PMOS	(LV)	<code>sg13_lv_pmos</code>	operating voltage (nom.) $V_{DD} = 1.5\text{ V}$, $L_{\min} = 0.13\text{ }\mu\text{ m}$, $V_{th} \approx -0.47\text{ V}$
High-voltage NMOS	(HV)	<code>sg13_hv_nmos</code>	operating voltage (nom.) $V_{DD} = 3.3\text{ V}$, $L_{\min} = 0.45\text{ }\mu\text{ m}$, $V_{th} \approx 0.7\text{ V}$; isolated NMOS available
High-voltage PMOS	(HV)	<code>sg13_hv_pmos</code>	operating voltage (nom.) $V_{DD} = 3.3\text{ V}$, $L_{\min} = 0.45\text{ }\mu\text{ m}$, $V_{th} \approx -0.65\text{ V}$
Silicided poly resistor		<code>rsil</code>	$R_s = 7\text{ }\Omega \pm 10\%$, $TC_1 = 3100\text{ ppm/K}$
Poly resistor		<code>rppd</code>	$R_s = 260\text{ }\Omega \pm 10\%$, $TC_1 = 170\text{ ppm/K}$
Poly resistor high		<code>rhigh</code>	$R_s = 1360\text{ }\Omega \pm 15\%$, $TC_1 = -2300\text{ ppm/K}$
MIM capacitor		<code>cap_cmim</code>	$C' = 1.5\text{ fF}/\mu\text{m}^2 \pm 10\%$, $VC_1 = -26\text{ ppm/V}$, $TC_1 = 3.6\text{ ppm/K}$, breakdown voltage $> 15\text{ V}$
MOM capacitor		n/a	The metal stack is well-suited for MOM capacitors due to 5 thin metal layers, but no primitive capacitor device is available at this point.

1.2 Schematic Entry Using Xschem

Xschem is an open-source schematic entry tool with emphasis on integrated circuits. For up-to-date information on the many features of Xschem and the basic operation of it please look at the available online documentation. Usage of Xschem will be learned with the first few basic examples, essentially using a single MOSFET. The usage model of Xschem is that the schematic is hierarchically drawn, and the simulation and evaluation statements are contained in the schematics. Further, Xschem offers embedded graphing, which we will mostly use.

A summary of important Xschem keyboard shortcuts is provided in Section 20.

1.3 Circuit Simulation Using ngspice

ngspice is an open-source circuit simulator based on SPICE [7]. Besides the usual simulation types like `op` (operating point), `dc` (dc sweeps), `tran` (time domain), `ac` (small-signal frequency sweeps), and `noise` (small-signal noise analysis), ngspice offers a script-like control interface, where many different simulation controls and result evaluations can be done. For detailed information please refer to the latest online manual.

Important ngspice simulation commands and options (e.g., how to control convergence settings) are listed in Section 21.

1.4 Integrated IC Design Environment (IIC-OSIC-TOOLS)

In order to make it easier to use the various required components (tools like Xschem and ngspice, PDKs like SG13G2), we will use the **IIC-OSIC-TOOLS**. This is a pre-compiled Docker image which enables circuit design on a virtual machine on virtually any type of computing equipment (personal PC, Raspberry Pi, cloud server) on various operating systems (Windows, macOS, Linux). For further information like installed tools, how to setup a VM, etc., please look at IIC-OSIC-TOOLS GitHub page.

⚠ Preparation

Please make sure to receive information about your personal VM access ahead of the course start.

Experienced users can install this image on their personal computer, for JKU students the IIC will host a VM on our compute cluster and provide personal login credentials.

⚠ Linux

In this course, we assume that students have a basic knowledge of Linux and how to operate it using the terminal (shell). If you are not yet familiar with Linux (which is basically a must when doing integrated circuit design as many tools are only available on Linux), then please check out a Linux introductory course or tutorial online, there are many resources available.

A summary of important Linux shell commands is provided in Section 19.

1.5 Setting up the Design Directory

- Open your VM by entering the URL in your browser.
- Open a terminal (third icon in the taskbar at the bottom). You should get the following prompt: `/foss/designs >`
- Clone the git repository into the current directory: `git clone https://github.com/iic-jku/analog-circuit-design.git`
- This GitHub repository includes a file called `.designinit`, which sets the PDK and certain paths. However, this must be located in `/foss/designs/`
- Therefore, we first need to copy it there: `cp analog-circuit-design/.designinit .`
- Then we adjust the variable `XSCHM_USER_LIBRARY_PATH` by opening the file in an editor e.g. `nano .designinit`
 - Change the last line from `export XSCHM_USER_LIBRARY_PATH=$DESIGNS/xschem` to `export XSCHM_USER_LIBRARY_PATH=$DESIGNS/analog-circuit-design/xschem`
- To apply the changes, we need to close the current terminal window: `exit`
- Open again a terminal
- Test if the correct PDK gets selected: `echo $PDK` (you should get `sg13g2` as the answer)
- Change into the GitHub repository: `cd analog-circuit-design`
- Start xschem using `xschem` or directly open a specific schematic using `xschem xschem/dc_lv_nmos.sch`

1.5.1 Creating Backups

You can easily create backups of your work by creating a zip archive of the complete directory:

- Change to the parent directory: `cd /foss/designs`
- Create a zip archive from the complete design folder: `zip backup.zip analog-circuit-design -r`

1.5.2 Updating the Repository

- **Create a backup!**
- Go to directory: e.g. `cd /foss/designs/analog-circuit-design`
- Fetch newest changes from the origin: `git fetch origin`
- Merge changes from the origin into your local branch `main`: `git merge origin/main`

⚠ Git Merge Conflicts

It is possible that `git merge` does not complete successfully. Either you are able to resolve the merge conflict manually, or it may be easier to make a fresh clone of the repository and adding your local changes manually from the backup.

! Important

Please think twice before executing any git command without a backup, as this could lead to permanent loss of data!

2 First Steps

In this first chapter we will learn to use Xschem for schematic entry, and how to operate the ngspice SPICE simulator for circuit simulations. Further, we will make ourselves familiar with the transistor and other passive components available in the IHP Microelectronics SG13G2 technology. While this is strictly speaking a BiCMOS technology offering MOSFETs as well as SiGe heterojunction bipolar transistors (HBTs), we will use it as a pure CMOS technology, which is available from IHP under the name SG13C.

2.1 The Metal-Oxide-Semiconductor Field-Effect-Transistor (MOSFET)

In this course, we will **not** dive into semiconductor physics and derive the device operation bottom-up starting from a fundamental level governed by quantum mechanics or a simplified solid-state physics based approach resulting in the well-known square-law model. Instead, we will treat the MOSFET behaviorally by assuming a 4-terminal device, and the performance of this device regarding its terminal voltages and currents we will largely derive from the simulation model.



Figure 1: Circuit symbols for different voltage-controlled amplifiers (from left to right: MOSFET, bipolar junction transistor, junction FET, triode).

Look at the transistor symbols shown in Figure 1. By treating them as a black box, where the output current is controlled by an input voltage, we can design circuits with all of them, even vacuum tubes would work in the same way.

Since we have an emphasis on integrated circuit design in this course, the size of the MOSFET can be adapted by changing its width W and its length L . As we will see later, L has a profound impact on the MOSFET performance allowing to trade-off speed versus output conductance versus device-to-device matching. The width W is more of a scaling parameter to adapt the current **density** (strictly speaking charge density) forming in the MOSFET channel to a desired current. More about this later.

The circuit symbol that we will use for the n-channel MOSFET is shown in Figure 2, and for the p-channel MOSFET it is shown in Figure 3. A control voltage between gate (“G”) and source (“S”) controls the current flow between drain (“D”) and source. The MOSFET is a 4-terminal device, so the bulk (“B”) can also control the drain-source current flow. Often, the bulk is connected to source, and then the bulk terminal is not shown to declutter the schematics.

i MOSFET Background

Strictly speaking, the drain-source current of a MOSFET is controlled by the voltage between gate and bulk (V_{GB}) and the voltage between drain and source (V_{DS}). Since bulk is often connected to source anyway, and many circuit designers historically were already familiar with the operation of the bipolar junction transistor (BJT), it is common to consider the gate-source voltage (besides the drain-source voltage) as the controlling voltage.

This focus on gate-source suggests that the source is special compared to the drain. In a typical physical MOSFET, however, the drain and source are constructed exactly the same (i.e., the MOSFET is a symmetric device), and which terminal is drain, and which terminal is source, is only determined by the applied voltage potentials, and can change dynamically during operation (think of a MOSFET operating as a switch... which side is the drain, which side is the source?).

Unfortunately, this focus on a “special” source has made its way into some MOSFET compact models. The model that is used in SG13G2 luckily uses the PSP model, which is formulated symmetrically with regards to drain and source, and is thus very well suited for analog and RF circuit design. For a detailed understanding of the PSP model please refer to the model documentation.

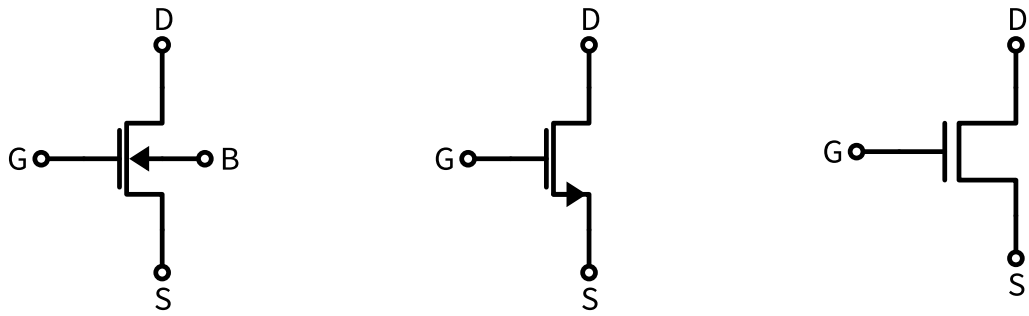


Figure 2: Circuit symbol of n-channel MOSFET. For circuit design in this course, we will mostly use the middle symbol without bulk connection and an arrow indicating the source terminal.

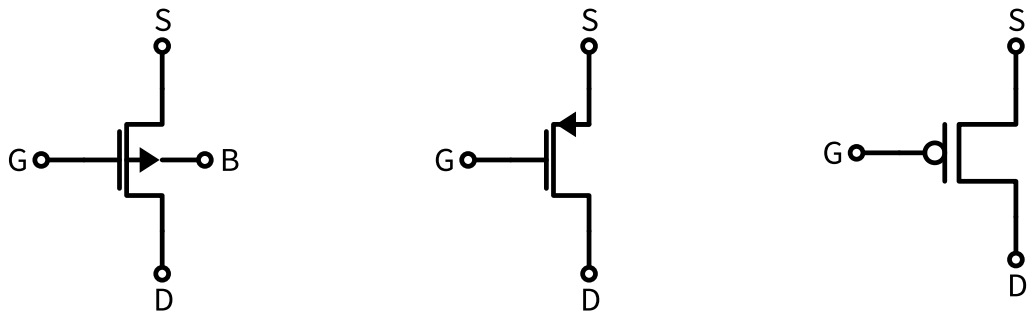


Figure 3: Circuit symbol of p-channel MOSFET. As for n-channel MOSFETs, we will mostly use the middle symbol without bulk connection and an arrow indicating the source terminal.

! MOSFET Symbol

Looking at the MOSFET symbols in Figure 2 and Figure 3, you might have noticed that the left and the right symbols are symmetric for the drain and source terminals, while the middle symbol shows an arrow in the source connection.

This is a common “error” in many important textbooks and online resources [1], [2], [3], and it is important to be aware of this. The drain and source of a MOSFET are (usually) symmetric, and the current flow can be reversed by changing the applied voltages (and then also drain and source swap; generally, for an NMOS, the connection with the higher potential is the drain, the one with the lower potential is the source. For a PMOS, the situation is inverted).

The symbol in the middle of Figure 2 and Figure 3 is thus misleading, because it suggests that the source is special and that the current can only flow in one direction. This is not the case, and it is important to be aware of this when designing circuits, especially when using MOSFETs as switches. As many symbols are drawn this way, we will also use this symbol in this course (and the resemblance to a bipolar junction transistor is intentional), but please be aware of the fact that the drain and source are symmetric, and the current can flow in both directions depending on the bias voltages!

For hand calculations and theoretical discussions we will use the following simplified large-signal model, shown in Figure 4. A current source I_D models the current flow between drain and source, and it is controlled by the three control voltages V_{GS} , V_{DS} , and V_{SB} . Note that in this way (since $I_D = f(V_{DS})$) also a resistive behavior between D and S can be modelled. In case that B and S are shorted then simply $V_{SB} = 0$ and C_{SB} is shorted.

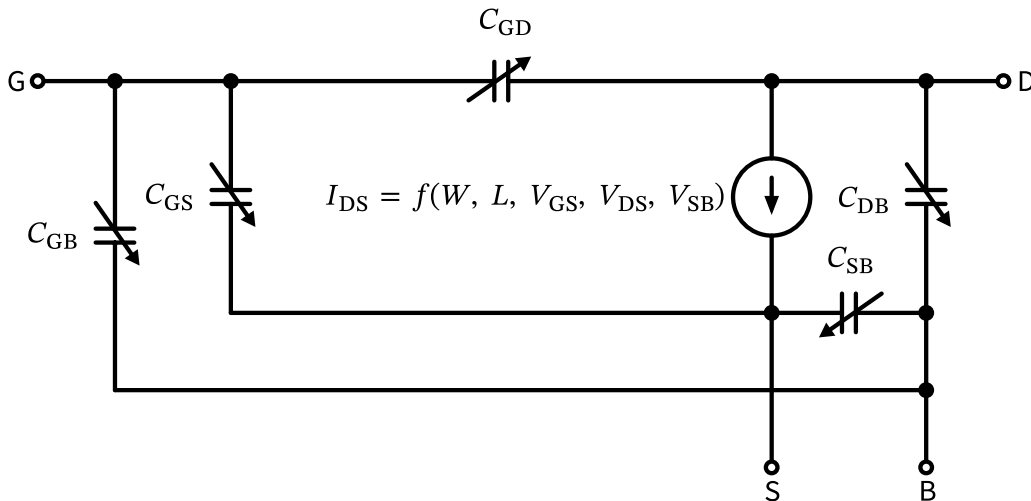


Figure 4: The MOSFET large-signal model. In general, all capacitors are nonlinear, i.e., they depend on their terminal voltages.

In an ideal MOSFET no dc current is flowing into the gate, the behavior is purely capacitive. We model this by two capacitors: $C_{GG} = C_{GS} + C_{GD} + C_{GB}$ is the total capacitance when

looking into the gate of the MOSFET. C_{GS} is usually the dominant capacitance, and C_{GD} models the capacitive feedback between D and G, usually induced by a topological overlap capacitance in the physical construction of the MOSFET. This capacitance is often small compared to C_{GS} , but in situations where we have a large voltage swing at the drain, this capacitance will be affected by the Miller effect (see Section 17.1). In hand calculations we will often set $C_{GD} = C_{GB} = C_{DB} = C_{SB} = 0$.

To model a physical MOSFET there will be also a requirement for resistors in the model to account for terminal access resistances (R_G , R_D , and R_S) as well as resistors to model second-order effects like non-quasistatic operation. For lower frequencies and bulk MOSFETs we will not consider these resistors, and just deal with the capacitive behavior.

i MOSFET Bulk Terminal

In many situations we will connect the bulk and source terminals of a MOSFET together, which results in a simplified large-signal model. As an exercise, look at Figure 4 and draw this simplified model (hint: look at Figure 6 and Figure 7 for inspiration).

Now, as we are skipping the bottom-up approach of deriving the MOSFET large-signal behavior from basic principles, we need to understand the behavior of the elements of the large-signal model in Figure 4 by using a circuit simulator and observing what happens. And generally, a first step in any new IC technology should be to investigate basic MOSFET performance, by doing simple dc sweeps of V_{GS} and V_{DS} and looking at I_D and other large- and small-signal parameters.

As a side note, the students who want to understand MOSFET behavior from a physical angle should consult the MOSFET chapter from the JKU course “Design of Complex Integrated Circuits” (VL 336.048). A great introduction into MOSFET operation and fabrication is given in [4], which is available freely online and is a recommended read. A very detailed description of the MOSFET (leaving usually no question unanswered) is provided in [5].

Now, in order to get started, basic Xschem testbenches are prepared, and first simple dc sweeps of various voltages and currents will be done. But before that, please look at the important note below!

! Mathematical Notation

Throughout this material, we will largely stick to the following notation standardized by IEEE:

- A **dc quantity** is shown with an upper-case variable name with upper-case subscripts, like V_{GS} .
- Double-subscripts denote **dc sources**, like V_{DD} and V_{SS} .
- An **ac (small-signal) quantity** (incremental quantity) has a lower-case variable name with a lower-case subscript, like g_m .
- A **total quantity** (dc plus ac) is shown as a lowercase variable name with upper-case subscript, like i_{DS} .
- An upper-case variable name with a lower-case subscript is used to denote signal *amplitudes* (phasors), like V_{gs} , V_{ds} , I_d .

i A Comment on Active and Passive Devices and Linear vs. Nonlinear

In contrast to the **passive** devices resistor R , inductor L , and capacitor C , which can only dissipate energy (and are often treated in a linearized fashion), transistors (like the MOSFET) are called “**active**”, since they can provide signal power amplification. However, transistors can not create energy out of thin air, but merely convert **dc** energy (supplied by the power supply) into **ac** energy [8]. They have to have nonlinear transfer characteristics to do this, but it has been shown that a piecewise-linear characteristic is sufficient [9]. This is very good news for circuit design, as usually we strive for linear behaviour!

2.1.1 Large-Signal MOSFET Model

We start with an investigation into the large-signal MOSFET model shown in Figure 4 by using the simple testbench for the LV NMOS shown in Figure 5.

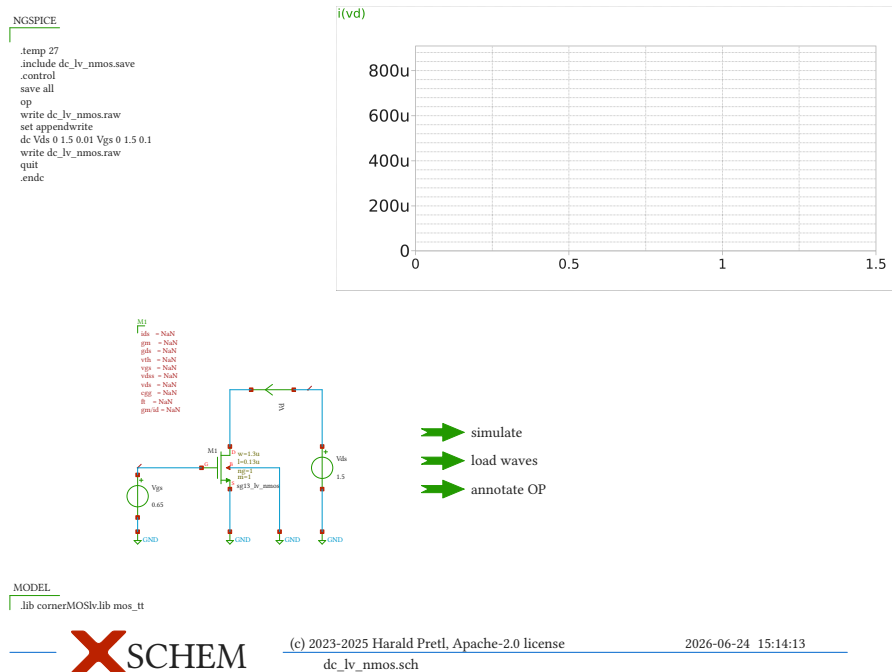


Figure 5: Testbench for NMOS dc sweeps.

i MOSFET Simulation Model

For modelling the MOSFET behavior in a circuit simulator like ngspice different models are available. Some of these models have been widely adopted, like the BSIM (Berkeley Short-channel IGFET Model) or PSP (Philips Penn State) model. The PSP model version 103.6 is used in the IHP SG13G2 PDK for the LV and HV MOSFET. This model has several advantages:

- Physics-based surface-potential model
- Symmetric formulation with respect to drain and source
- Support for mobility reduction, velocity saturation, DIBL, gate current, lateral doping gradient effects, STI stress, NQS, etc.

The PSP 103.6 model documentation can be found [here](#). In chapter 8 the dc operating point output of the model (these parameters can be queried in ngspice) is explained, which is helpful to interpret the simulation output.

Exercise: MOSFET Investigation

Please try to execute the following steps and answer these questions:

1. Get the LV NMOS testbench (available at https://github.com/iic-jku/analog-circuit-design/blob/main/xschem/dc_lv_nmos.sch) working in your IIC-OSIC-TOOLS environment.
2. Make yourself familiar with Xschem (change the schematic in various ways, run a simulation, graph the result).
3. Make yourself familiar with ngspice (run various simulations, save nets and parameters, use the embedded Xschem graphing, explore the interactive ngspice shell to look at MOSFET model parameters).
4. Explore the LV NMOS `sg13_lv_nmos`:
 1. How is I_D affected by V_{GS} and V_{DS} ?
 2. Change W and L of the MOSFET. What is the impact on the above parameters? Can you explain the variations?
 3. Look at the capacitance values for C_{GS} , C_{GB} , C_{GD} , and C_{DB} . How are they affected by W and L and by changing the bias conditions (play with V_{GS} and V_{DS})?
 4. When looking at the model parameters in ngspice, you see that there is a C_{GD} and a C_{DG} . Why is this, what could be the difference? Sometimes these capacitors show a negative value, why? (Hint: Study Note 1)
5. Build testbenches in Xschem for the LV PMOS, the HV NMOS, and the HV PMOS. Explore the different results.
 1. For a given W and L , which device provides more drain current? How are the capacitances related?
 2. If you would have to size an inverter, what would be the ideal ratio of W_p/W_n ? Will you exactly design this ratio, or are the reasons to deviate?
 3. There are LV and HV MOSFETs, and you investigated the difference in performance. What is the rationale when designing circuits for selection either an LV type, and when to choose an HV type?
6. Build a test bench to explore the body effect, start with LV NMOS.
 1. What happens when $V_{SB} \neq 0$?

2.1.2 Small-Signal MOSFET Model

As you have seen in the previous investigations, the large-signal model of Figure 4 describes the behavior of the MOSFET across a wide range of voltages applied at the MOSFET terminals. Unfortunately, for hand analysis dealing with a nonlinear model is close to impossible, at the very least it is quite tedious.

However, for many practical situations, we bias a MOSFET with a set of dc voltages applied to its terminal, and only apply small signal excursions during operation. If we do this, we can linearize the large-signal model in this dc operating point, and resort to a small-signal model which can be very useful for hand calculations. Many experienced designers analyze their circuits by doing these kind of hand calculations and describing the circuit analytically, which is a great way to understand fundamental performance limits and relationships between parameters.

We will use the small-signal MOSFET model shown in Figure 6 for this course. The current-source $i_d = g_m v_{gs}$ models the drain current I_D as a function of V_{GS} with

$$g_m = \frac{\partial I_D(V_{GS}, V_{DS}, V_{SB})}{\partial V_{GS}},$$

and the output conductance g_{ds} models the dependence of the drain current on V_{DS} :

$$g_{ds} = \frac{\partial I_D(V_{GS}, V_{DS}, V_{SB})}{\partial V_{DS}}$$

The drain current dependency on the source-bulk voltage (the so-called “body effect”) is introduced by the current source $g_{mb} V_{sb}$:

$$g_{mb} = -\frac{\partial I_D(V_{GS}, V_{DS}, V_{SB})}{\partial V_{SB}} = \frac{\partial I_D(V_{GS}, V_{DS}, V_{BS})}{\partial V_{BS}}$$

Note the minus sign: raising the source potential above the bulk increases V_{th} and thus *lowers* I_D . By referencing g_{mb} to $V_{BS} = -V_{SB}$ it comes out **positive**, just like g_m , which is the common convention; typically $g_{mb}/g_m \approx 0.1 \dots 0.3$. This is why the $g_{mb} V_{sb}$ source in Figure 6 is drawn with its arrow pointing *opposite* to the $g_m V_{gs}$ source.

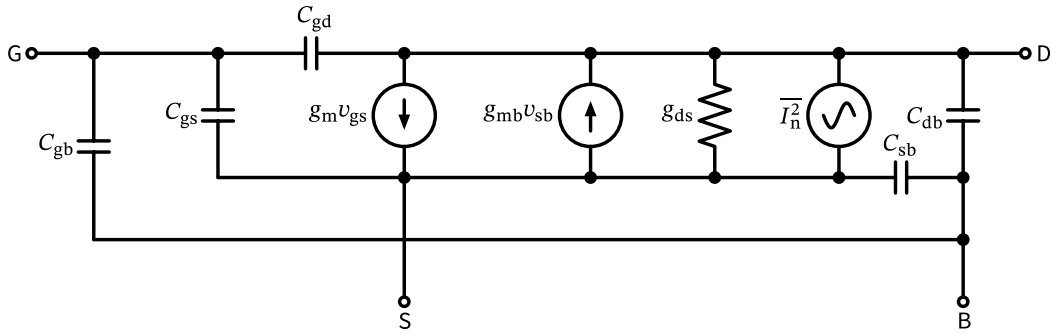


Figure 6: The MOSFET small-signal model.

As has been mentioned before, in many situations (and whenever we want to use a simplified model) we connect source and bulk of the MOSFET together. This results in the much simplified small-signal model shown in Figure 7.

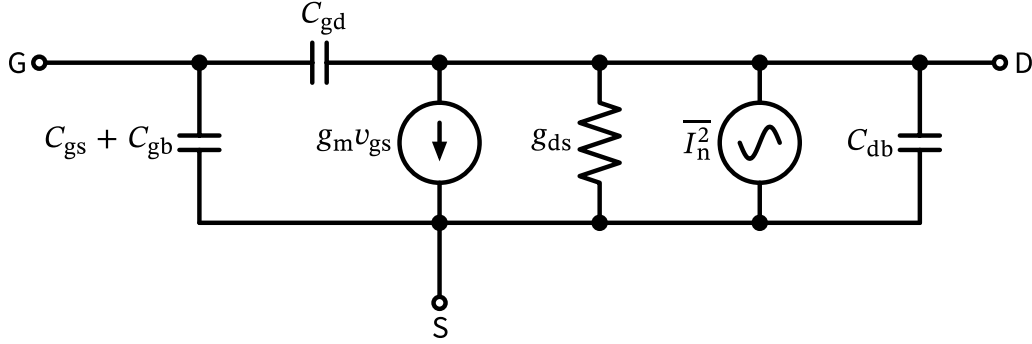


Figure 7: The MOSFET small-signal model when source and bulk are shorted.

Like any electronic device, the MOSFET introduces noise into the circuit. In this course we will only consider the **drain-source current noise** of the MOSFET, given by

$$\overline{I_n^2} = 4kT\gamma g_{d0}, \quad (1)$$

where $\overline{I_n^2}$ is the one-sided power-spectral density of the noise in A^2/Hz ; k is the Boltzmann constant; T is the absolute temperature; γ is a (fitting) parameter in simplified theory changing between $\gamma = 2/3$ in saturation and $\gamma = 1$ for triode operation; g_{d0} is equal to g_m in saturation and g_{ds} in triode.

i MOSFET Triode and Saturation Region

Sometimes we will refer to different operating modes of the MOSFET like “saturation” or “triode.” Generally speaking, when the drain-source voltage is small, then the MOSFET acts as a voltage-controlled resistor (since the impact of both V_{GS} and V_{DS} on I_D is large), and this mode of operation we call “**triode**” mode.

When the drain-source voltage V_{DS} is increased, at some point the drain-source current saturates and is only a weak function of the drain-source voltage, while still being well controlled by V_{GS} . This mode is called “**saturation**” mode.

As you can see in the large-signal investigations, these transitions happen gradually, and it is difficult to define a precise point where one operating mode switches to the other one. In this sense we use terms like “triode” and “saturation” only in an approximate sense.

We can also consider an even more reduced small-signal MOSFET model compared to Figure 7, which is shown in Figure 8. In this, we just consider the transconductance g_m , the input capacitor C_{gg} , as well as the output conductance g_{ds} . Note that we can redraw the pi-model of Figure 8 into the τ -model of Figure 9. Depending on the circuit configuration, either the first or the second form results in simpler calculations of the circuit equations.

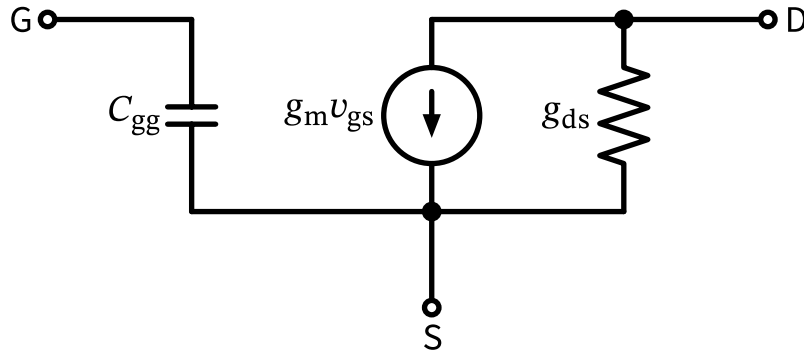


Figure 8: The MOSFET small-signal basic pi-model.

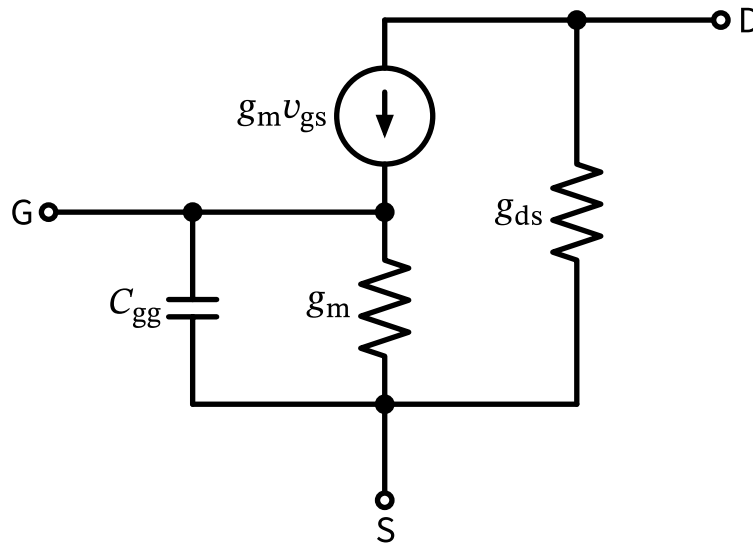


Figure 9: The MOSFET small-signal basic T-model.

💡 Exercise: MOSFET Model Transformation

Can you show, with which circuit manipulations you can transform the pi-model of Figure 8 into the T-model of Figure 9?

A metric which is useful to assess the speed of a MOSFET is the so-called **transit frequency** f_T . It is defined as the frequency where the small-signal current gain (output current divided by the input current) of a MOSFET driven by a voltage-source at the input and loaded by a voltage source at the output drops to unity (reaches one). It can easily be derived using the simplified MOSFET small-signal model of Figure 7 by driving it with a voltage source and shorting the output to ground (neglecting the feed-forward current introduced by C_{gd}):

$$\omega_T = 2\pi f_T \approx \frac{g_m}{C_{gg}} = \frac{g_m}{C_{gs} + C_{gd} + C_{gb}}. \quad (2)$$

This frequency is an extrapolated frequency where the MOSFET operation is dominated by several second-order effects (hence Equation 2 is not valid any longer). A rule-of-thumb is to use a MOSFET up to approximately $f_T/10$. In any case, f_T is a proxy of the speed of a MOSFET; in other words, how much input capacitance C_{gg} is incurred when creating a certain g_m .

💡 Exercise: MOSFET Transit Frequency

As a home exercise, try to derive Equation 2 starting from Figure 7. This is a useful exercise to verify your understanding of the small-signal model.

Now we need to see how the small-signal parameters seen in Figure 6 can be investigated and estimated using circuit simulation.

💡 Exercise: MOSFET Small-Signal Parameters

Please try to execute the following steps and answer the following questions:

1. Reuse the LV NMOS testbench (available at https://github.com/iic-jku/analog-circuit-design/blob/main/xschem/dc_lv_nmos.sch).
2. Explore the LV NMOS `sg13_lv_nmos`:
 1. How are g_m and g_{ds} changing when you change the dc node voltages?
 2. What is the ratio of g_m to g_{mb} ? What is the physical reason behind this ratio (you might want to revisit MOSFET device physics at this point)?
 3. Take a look at the device capacitances C_{gs} , C_{gd} , and C_{gb} . Why are they important? What is the f_T of the MOSFET?
 4. Look at the drain noise current according to the MOSFET model and compare with a hand calculation of the noise. In the noise equation there is the factor γ , which in triode is $\gamma = 1$ and in saturation is $\gamma = 2/3$ according to basic text books. Which value of γ are you calculating? Why might it be different?
3. Go back to your testbench for the LV PMOS `sg13_lv_pmos`:
 1. What is the difference in g_m , g_{ds} , and other parameters between the NMOS and the PMOS? Why could they be different?

i Note 1: Maxwell Capacitance Matrix

A Maxwell capacitance matrix [10] provides the relation between voltages on a set of conductors and the charges on these conductors. For a given conductor set with N conductors (and thus N terminals) the relation is

$$\mathbf{Q} = \mathbf{C} \cdot \mathbf{V}$$

where $\mathbf{Q}$ is a vector of the charges on the N conductors, $\mathbf{C}$ is a $N \times N$ capacitance matrix, and $\mathbf{V}$ is the potential vector. In the case of two conductors and physical capacitances between them, $\mathbf{C}$ is given by

$$\mathbf{C} = \begin{pmatrix} C_{11} + C_{12} & -C_{12} \\ -C_{12} & C_{12} + C_{22} \end{pmatrix}$$

where C_{11} and C_{22} are the **auto capacitances** of the conductors towards infinity (ground), and $C_{12} = C_{21}$ is the **mutual capacitance** between the two conductors. Note that these are the *physical* capacitances, and that they are therefore **not** identical to the entries of $\mathbf{C}$: a diagonal entry of $\mathbf{C}$ is the sum of all capacitances touching a node ($\partial Q_1 / \partial V_1 = C_{11} + C_{12}$), whereas an off-diagonal entry is *negative* ($\partial Q_1 / \partial V_2 = -C_{12}$).

Using the above equation to calculate Q_1 (the charge on conductor 1) results in

$$Q_1 = (C_{11} + C_{12})V_1 - C_{12}V_2 = C_{11}(V_1 - 0) + C_{12}(V_1 - V_2)$$

which is the expected result.

Such a Maxwell capacitance formulation is also used in the MOSFET model to describe the charge at a terminal as a function of potential at another terminal. So,

$$C_{GD} = \frac{\partial Q_G}{\partial V_D}$$

or

$$C_{GG} = \frac{\partial Q_G}{\partial V_G}$$

with Q_G the charge at terminal G in response to either V_D or V_G . Note that in a MOSFET, generally $C_{xy} \neq C_{yx}$!

This also explains the negative capacitance values that a simulator sometimes reports (see the exercise above): the off-diagonal entries of a Maxwell capacitance matrix carry a negative sign by construction, so a reported C_{GD} of, e.g., -1 fF simply means a physical coupling capacitance of 1 fF between gate and drain.

2.2 Conclusion

Congratulations for making it thus far! By now you should have a solid grasp of the tool handling of Xschem and ngspice, and you should be familiar with the large- and small-signal operation of both NMOS and PMOS, and the parameters describing these behaviors. If you feel

you are not sufficiently fluent in these things, please go back to the beginning of Section 2.1 and revisit the relevant sections, or dive into further reading about the MOSFET operation, like in [4].

3 Transistor Sizing Using g_m/I_D Methodology

When designing integrated circuits it is an important question how to select various parameters of a MOSFET, like W , L , or the bias current I_D . In comparison to using discrete components in PCB design, or also compared to a bipolar junction transistor (BJT), we have these degrees of freedom, which make integrated circuit design so interesting.

Often, transistor sizing in entry-level courses is based on the square-law model, where a simple analytical equation for the drain current can be derived. However, in nanometer CMOS, the MOSFET behavior is much more complex than these simple models. Also, these highly simplified derivations introduce concepts like the threshold voltage or the overdrive voltage, which are interesting from a theoretical viewpoint, but have little practical use.

i MOSFET Square-Law Model

One of the many simplifications of the square-law model is that the mobility of the charge carriers is assumed constant (it is not). Further, the existence of a threshold voltage is assumed, but in fact this voltage exists only given a certain definition, and depending on definition, its value changes. In addition, in nm CMOS, the threshold voltage is a function of many things, like W and L .

An additional shortcoming of the square-law model is that it is only valid in strong inversion, i.e. for large V_{GS} where the drain current is dominated by the drift current. As soon as the gate-source voltage gets smaller, the square-law model breaks, as the drain current component based on diffusion currents gets dominant. Modern compact MOSFET models (like the PSP model used in SG13G2) use hundreds of parameters and fairly complex equations to somewhat properly describe MOSFET behavior over a wide range of parameters like W , L , and temperature. A modern approach to MOSFET sizing is thus based on the thought to use exactly these MOSFET models, characterize them, put the resulting data into tables and charts, and thus learn about the complex MOSFET behavior and use it for MOSFET sizing.

Being a well-established approach we select the g_m/I_D methodology introduced by [11] and extended in [12]. A brief introduction is available here as well.

The g_m/I_D methodology has the huge advantage that it catches MOSFET behavior quite accurately over a wide range of operating conditions, and the curves look very similar for pretty much all CMOS technologies, from micrometer bulk CMOS down to nanometer FinFET devices. Of course the absolute values change, but the method applies universally.

3.1 MOSFET Characterization Testbench

In order to get the required tabulated data we use a testbench in Xschem which sweeps the length L and the terminal voltages (V_{GS} , V_{DS} and V_{SB}) for a fixed device width $W = 5\text{ }\mu\text{m}$ and records various large- and small-signal parameters, which are then stored in large tables. The testbench for the LV NMOS is shown in Figure 10, and the TB for the LV PMOS is shown in Figure 11.

i Note on Characterization Testbench

The testbenches are relatively straightforward, with one exception: The drain current noise is sensed via the drain voltage source **vd** and converted to a noise voltage (node **n**) using a current-controlled voltage source (CCVS). This is necessary as the **.noise** simulation statement works with voltages.

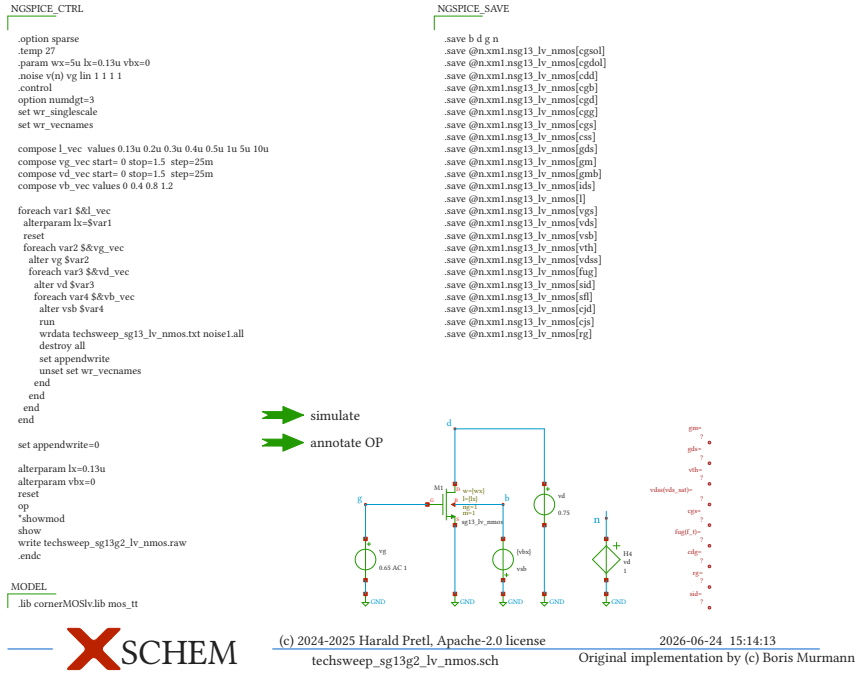


Figure 10: Testbench for LV NMOS g_m/I_D characterization.

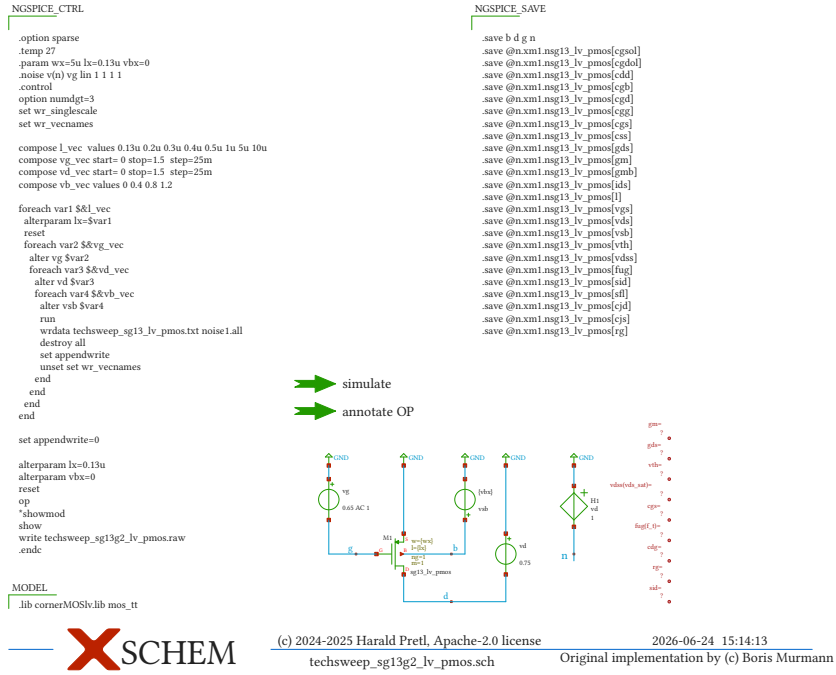


Figure 11: Testbench for LV PMOS g_m/I_D characterization.

We will use Jupyter notebooks to inspect the resulting data, and interpret some important graphs. This will greatly help to understand the MOSFET behavior.

Note on width W

In general, the device width could be included as a fifth sweep variable. However, this is not necessary since the parameters scale approximately linearly with W across the typical range encountered in analog design. For $W > 2 \mu\text{m}$ the error lies within about 1.5% for g_m/I_D , g_m/g_{ds} and g_m/C_{gg} as described in [12].

The resulting four-dimensional data is saved into a `.txt` file and imported into two Jupyter notebooks as visualized in Figure 12. The first notebook outputs `.mat` files, which are compatible with the `pygmid` Python package used for sizing. The second notebook generates vector graphic characterization plots, which are shown in Section 3.2 for LV NMOS and Section 3.3 for LV PMOS. With these plots, an immediate understanding of the tradeoffs for the given transistor can be acquired. Furthermore, they can be used for fast hand calculations in small circuits.

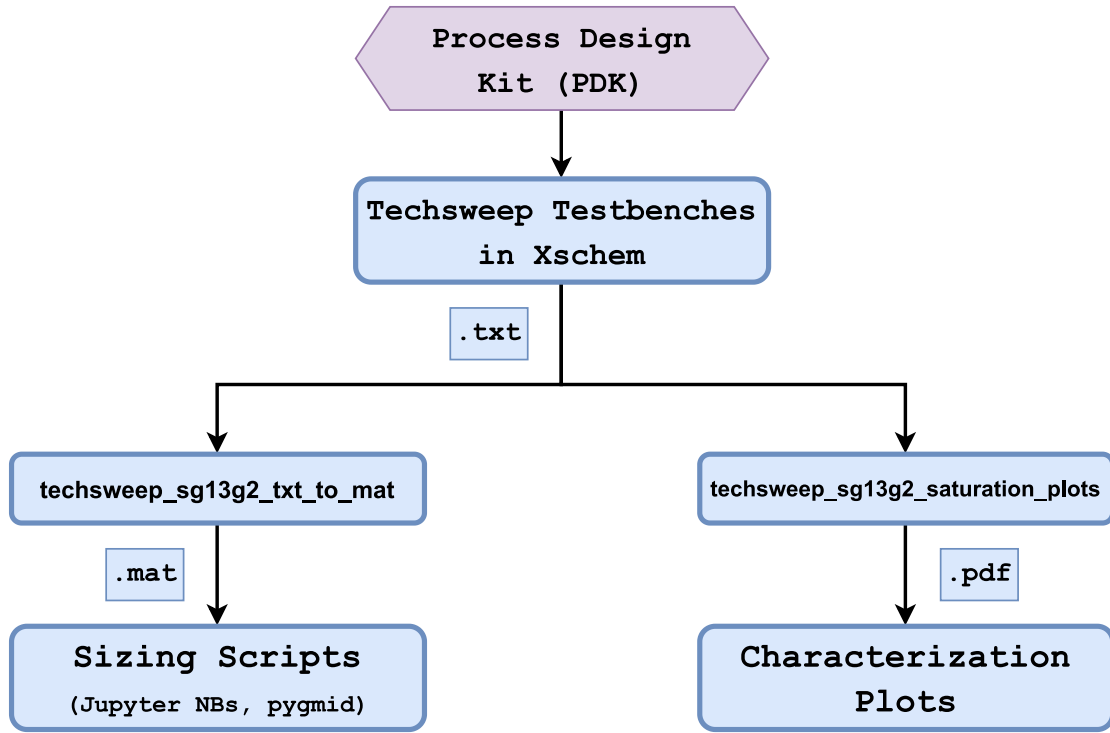


Figure 12: Overview of the g_m/I_D MOSFET characterization procedure [13].

3.2 NMOS Characterization in Saturation

First, we will start looking at the LV NMOS. In Section 3.3 we have the corresponding graphs for the LV PMOS. In this lecture, we will only use the LV MOSFETs. While there are also the HV types available, they are mainly used for high-voltage circuits, like circuits connecting to the outside world. Here, we only will design low-voltage circuits running at a nominal supply voltage of 1.5 V, so only the LV types are of interest to us.

In the plots that follow we will set $V_{DS} = V_{DD}/2$ to keep the MOSFET in saturation (as this is the region of operation where most MOSFETs are operated when working in class-A). We will later also look at the MOSFET performance in triode operation, as this is the operation mode where the MOSFET is used as a switch. While the g_m/I_D method is primarily intended to be used for circuits where the MOSFETs are held in saturation and are biased by a certain bias current (usually referred to class-A), the generated tables using the testbenches of Section 3.1 contain the data for all MOSFET bias points.

The first important graph is the plot of g_m/I_D and f_T versus the gate-source voltage V_{GS} . First let us answer the question why g_m/I_D is a good parameter to look at, and actually this is also the central parameter in the g_m/I_D methodology. In many circuits we want to get a large amplification from a MOSFET, which corresponds to a large g_m . We want to achieve this by spending the minimum biasing current possible (ideally zero), as we almost always design for lowest power consumption. Thus, a high g_m/I_D ratio is good.

i Power Consumption

Designing for minimum power consumption is pretty much always mandated. For battery-operated equipment it is a paramount requirement, but also in other equipment electrical energy consumption is a concern, and often severely limited by the cooling capabilities of the electrical system.

However, as can be seen in the below plot, there exists a strong and unfortunate trade-off with device speed, characterized here by the transit frequency f_T . It would be ideal if there exists a design point where we get high transconductance per bias current concurrently to having the fastest operation, but unfortunately, this is clearly not the case. The g_m/I_D peaks for $V_{GS} < 0.3$ V, and the highest speed we get at $V_{GS} \approx 1.2$ V. The dashed vertical line plots the nominal threshold voltage, as you can see in this continuum of parameter space, it marks not a particularly special point.

Note that

$$\frac{g_m}{I_D} = \frac{1}{nV_T} \quad (3)$$

for a MOSFET in weak inversion (i.e., small gate-source voltage). n is the subthreshold slope, and $V_T = kT/q$ which is 25.8 mV at 300 K. We thus have $n \approx 1.38$ for this LV NMOS, which falls nicely into the usual range for n of 1.3 to 1.5 for bulk CMOS (FinFET have n very close to 1).

For the classical square-law model of the MOSFET in strong inversion, g_m/I_D is given as

$$\frac{g_m}{I_D} = \frac{2}{V_{GS} - V_{th}} = \frac{2}{V_{od}} \quad (4)$$

with V_{th} the threshold voltage and V_{od} the so-called “overdrive voltage.” The latter is sometimes also dubbed the effective gate-source voltage V_{eff} [14].


i Why 300 K?

Why are we so often using a temperature of 300 K for a typical condition? As this corresponds to roughly 27° C, this accounts for some self heating compared to otherwise cooler usual room temperatures. Further, engineers like round numbers which are easy to remember, so 300 K is used as a proxy for room temperature.

As we can also see from the plot below, the peak transit frequency of the LV NMOS is about 75 GHz, which allows building radio-frequency circuits up to ca. $f_T/10 = 7.5$ GHz, which is a respectable number. It is no coincidence that the transition for RF design in the GHz-range switched from BJT-based technologies to CMOS roughly in the time frame when 130nm CMOS became available (ca. 2000).


Note that f_T saturates and even decreases again at around $V_{GS} = 1.2$ V due to second-order effects of the transistor like velocity saturation and DIBL. Velocity saturation describes the effect that the drift velocity of the electrons (or holes) no longer increases once the **lateral**

electric field along the channel becomes large, which in a short channel already happens at moderate V_{DS} . As a consequence, also g_m saturates. Since $f_T \propto g_m/C_{gg}$, f_T can not further increase. DIBL describes the effect where a high V_{DS} lowers the potential barrier at the source, effectively reducing the threshold voltage. Additionally, at high V_{GS} the channel is confined to a narrow region at the surface, leading to more carrier scattering and thus lower mobility (vertical-field mobility degradation).

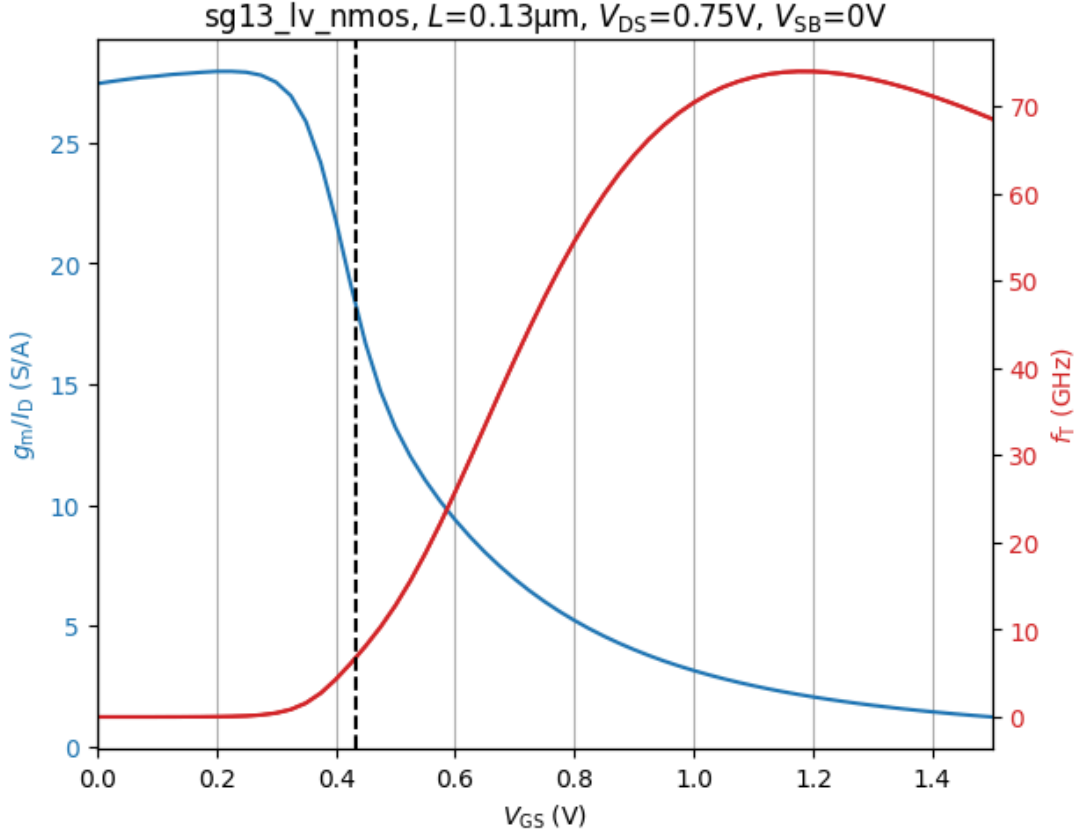


The following figure plots f_T against g_m/I_D for several different L . As you can see, device speed maximizes for a low g_m/I_D and a short L . Note that the drain-source voltage is kept at $V_{DS} = 0.75 \text{ V} = V_{DD}/2$, which is a typical value keeping the MOSFET in saturation across the characterization sweeps. Further, the source-bulk voltage is kept at $V_{SB} = V_S - V_B = 0 \text{ V}$, which means bulk and source terminals are connected. If $V_{SB} \neq 0 \text{ V}$, then the so-called body effect, bulk effect or back-gate effect occurs.


If $V_{SB} > 0 \text{ V}$, then V_{th} increases. If $V_{SB} < 0 \text{ V}$, then V_{th} decreases. At first glance, this effect may sound unwanted (and often also is), however, improved circuit designs by changing the bulk potential can be realized. For example, circuit 16 in [6] shows an implementation of a current mirror by exploiting the body effect. However, keep in mind that a deep-n-well (DNW), also called triple-well, is needed for NMOS transistors when the bulk is not tied to GND. This DNW may not be supported by the used PDK or can add additional costs to the wafer processing.

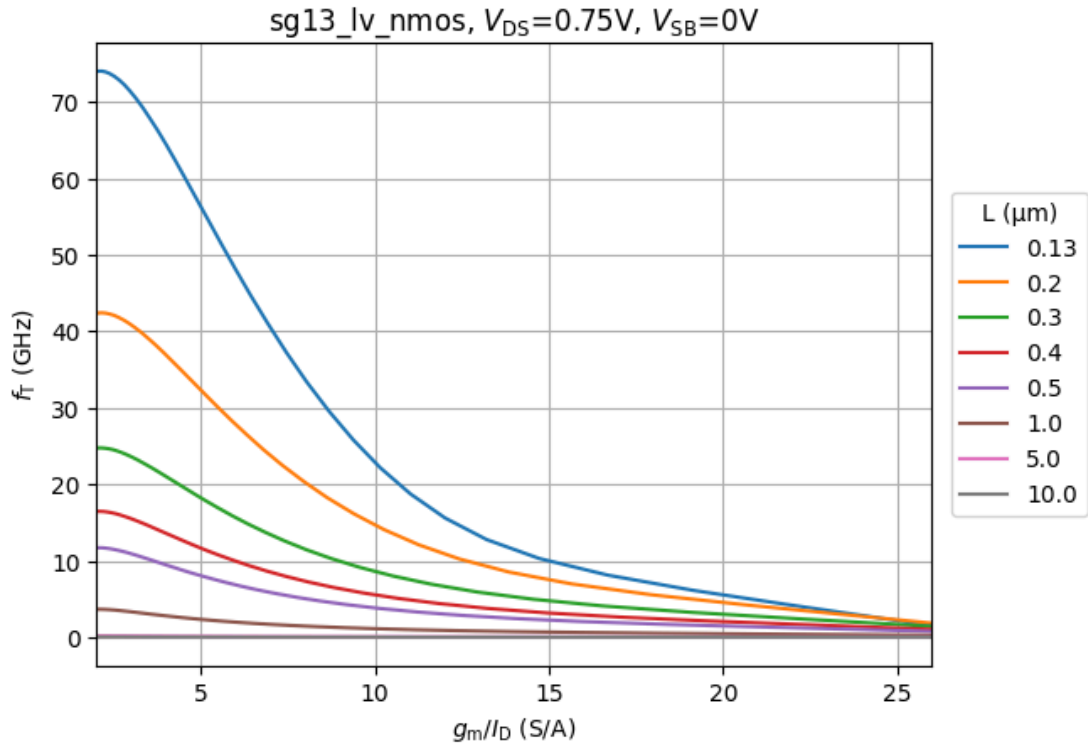


The next plot shows the ratio of g_m/g_{ds} versus g_m/I_D . The ratio g_m/g_{ds} is the so-called “**self-gain**” of the MOSFET, and shows the maximum voltage gain we can achieve in a single transistor configuration. As one can see the self gain increases for increasing L , but this also gives a slower transistor, so again there is a trade-off. This plot allows us to select the proper L of a MOSFET if we know which amount of self gain we need.

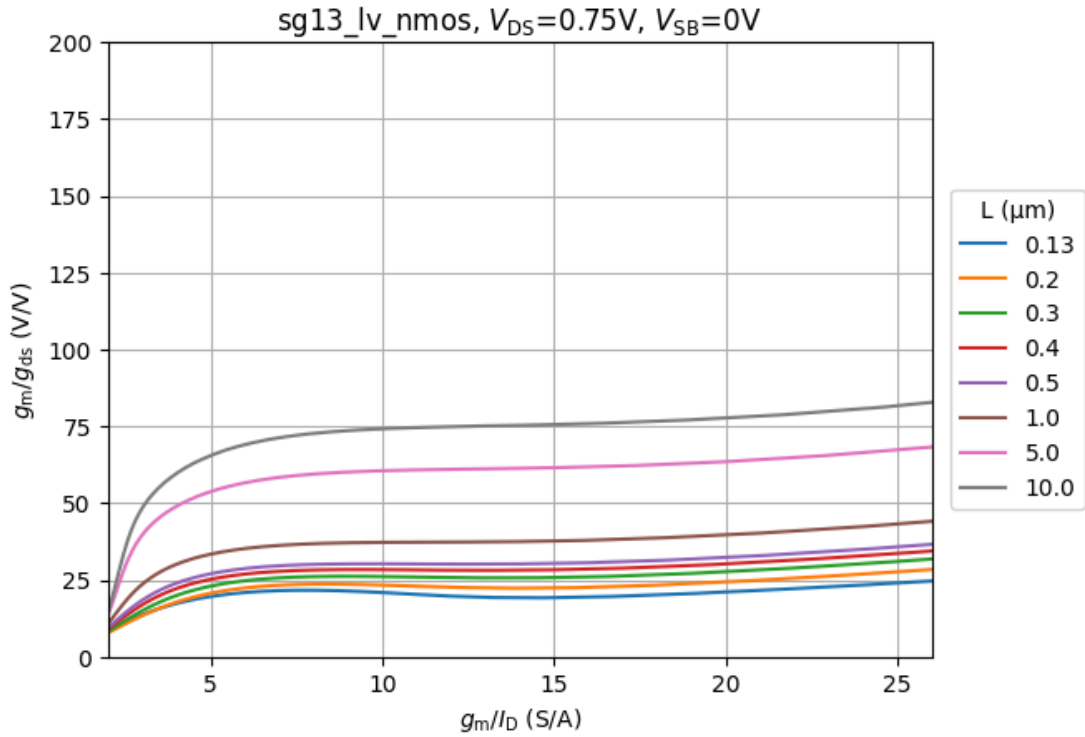

The following figure plots the drain current density I_D/W as a function of g_m/I_D and L . With this plot we can find out how to set the W of a MOSFET once we know the biasing current I_D , the L (selected according to self gain, f_T , and other considerations) and the g_m/I_D design point we selected. The drain current density I_D/W is a very useful normalized metric to use, because the physical action in the MOSFET establishes a charge density in the channel below the gate, and the changing of the W of the device merely transforms this charge density into an absolute parameter (together with L).

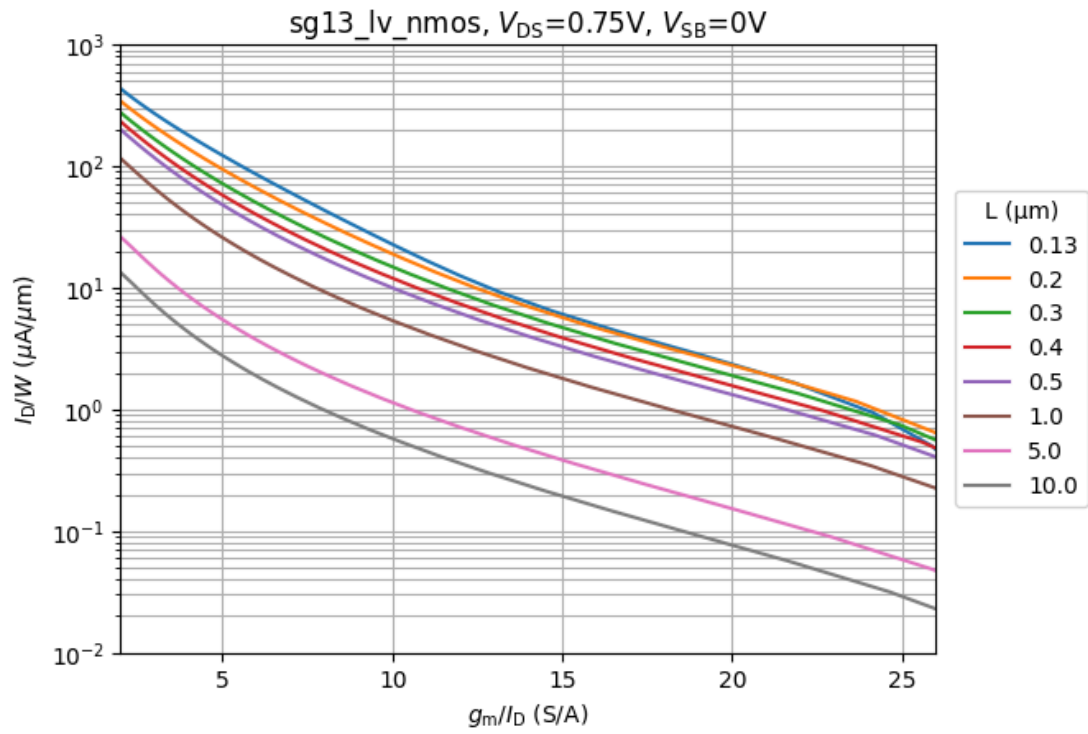

The following plot shows the minimum drain-source voltage $V_{ds,sat}$ that we need to establish in order to keep the MOSFET in saturation. As you can see, this value is almost independent of L , and increases for small g_m/I_D . So for low-voltage circuits, where headroom is precious, we tend to bias at $g_m/I_D \geq 10$, whereas for fast circuits we need to go to small $g_m/I_D \leq 5$ requiring substantial voltage headroom per MOSFET stage that we stack on top of each other.

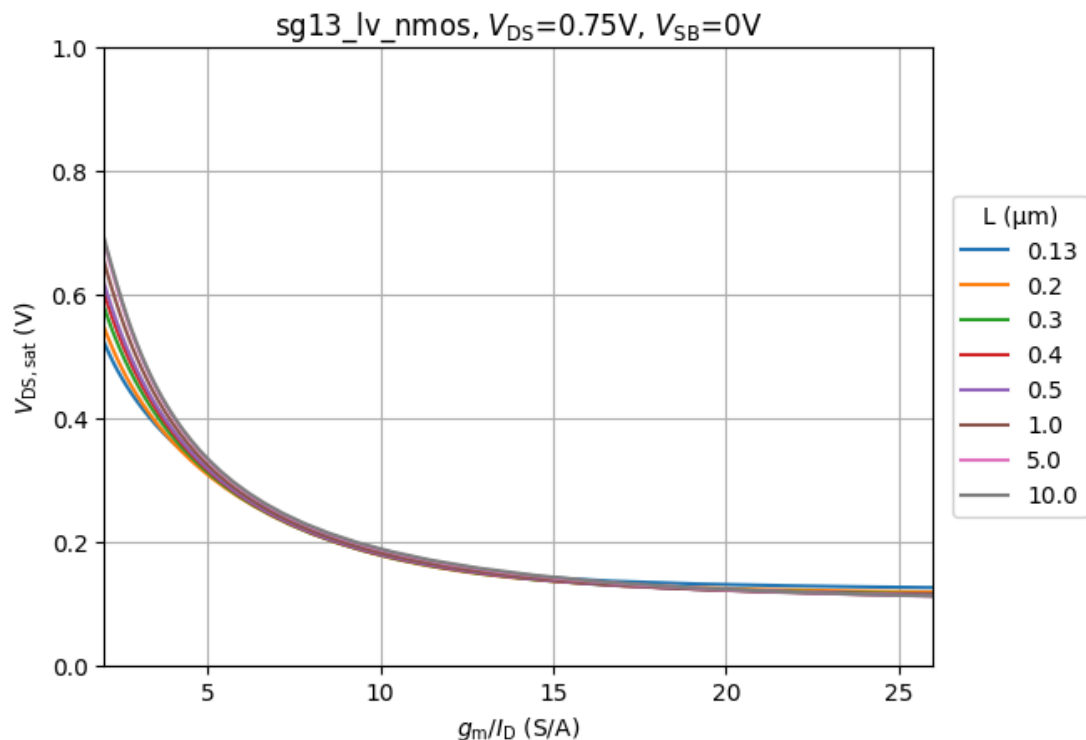

For analog circuits the noise performance is usually quite important. Thermal noise of a resistor (the Johnson-Nyquist noise) has a flat power-spectral density (PSD) given by $\overline{V_n^2}/\Delta f = 4kTR$, where k is Boltzmann's constant, T absolute temperature, and R the value of the resistor (the unit of $\overline{V_n^2}/\Delta f$ is V^2/Hz). This PSD is essentially flat until very high frequencies where quantum effects start to kick in.

i Noise Notation


We usually leave the Δf away for a shorter notation, so we write $\overline{V_n^2}$ when we actually mean $\overline{V_n^2}/\Delta f$. In case of doubt look at the unit of a quantity, whether it shows V^2 or V^2/Hz or $V/\sqrt{Hz}$ (or A^2 or A^2/Hz or $A/\sqrt{Hz}$).

Please also note that the pair of kT pretty much always shows up together, so when you do a calculation and you miss the one or the other, that is often a sign for miscalculation. Boltzmann's constant $k = 1.38 \cdot 10^{-23} J/K$ is just a scaling factor from thermal energy expressed as a temperature T to energy $E = kT$ expressed in Joule.

Further, when working with PSD there is the usage of a one-sided ($0 \leq f < \infty$) or two-sided power spectral density (PSD) ($-\infty < f < \infty$). The default in this lecture is the usage of the **one-sided PSD**.

In this lecture the only MOSFET noise we consider is the drain noise (as discussed in Section 2.1.2), showing up as a current noise between drain and source. For a realistic MOSFET noise model, also a (correlated) gate noise component and the thermal noise of the gate resistance needs to be considered.

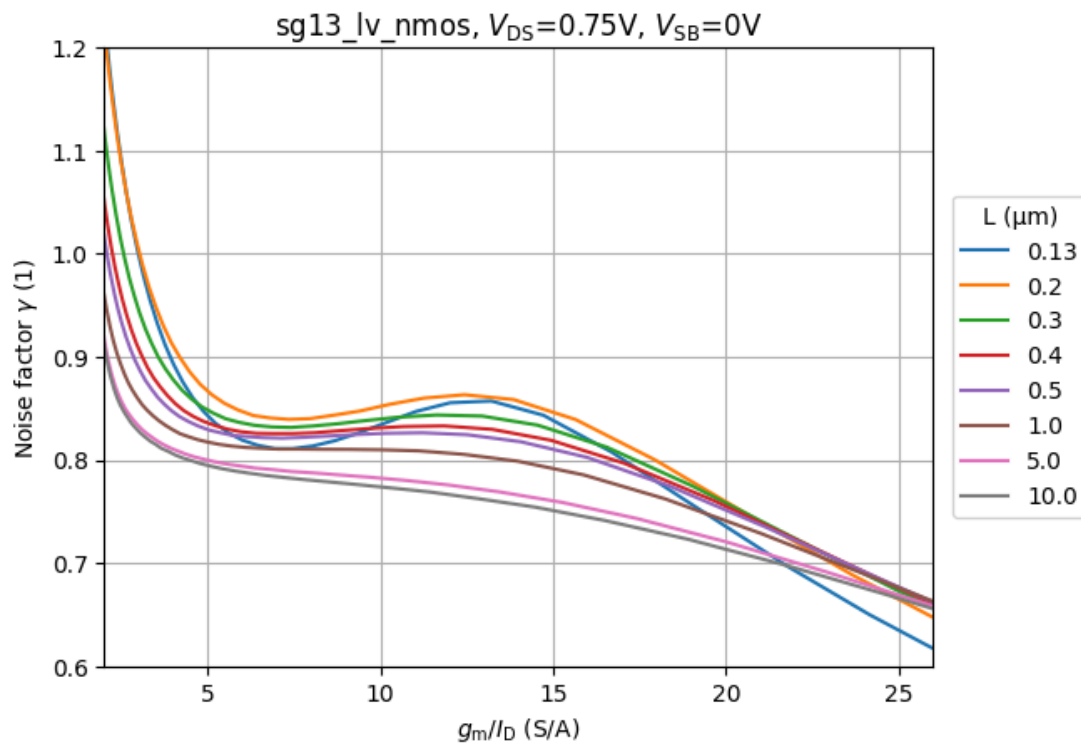The factor γ (Equation 1) is a function of many things (in classical theory, $\gamma = 2/3$ in saturation and $\gamma = 1$ in triode), and it is characterized in the following plot as a function of g_m/I_D and L . So when calculating MOSFET noise we can lookup γ in the below plot, and use Equation 1 to calculate the effective drain current noise.




In a MOSFET, unfortunately, besides the thermal noise according to Equation 1, there is also a substantial low-frequency excess noise, called “flicker noise” due to its characteristic $\overline{I_{d,nf}^2} = K_f/f$ behavior (this means that this noise PSD decreases versus frequency). In order to characterize this flicker noise the following plot shows the cross-over frequency f_{co} , where the flicker noise is as large as the thermal noise. As can be seen in the below plot, this frequency is a strong function of L and g_m/I_D . Generally, the flicker noise is proportional to $(WL)^{-1}$, so the larger the device is, the lower the flicker noise. The parameter g_m/I_D largely stays constant when we keep W/L constant, so for a given g_m/I_D flicker noise is proportional to $1/L^2$. However, increasing L lowers device speed dramatically, so here we have a trade-off between flicker-noise performance and MOSFET speed, and this can have dramatic consequences for high-speed circuits.

i MOSFET Flicker Noise

The physical origin of flicker noise is the crystal interface between silicon (Si) and the silicon dioxide (SiO₂). Since these are different materials, there are dangling bonds, which can capture charge carriers traveling in the channel. After a random time, these carriers are released, and flicker noise is the result. The amount of flicker noise is a function of the manufacturing process, and will generally be different between device types and wafer foundries.

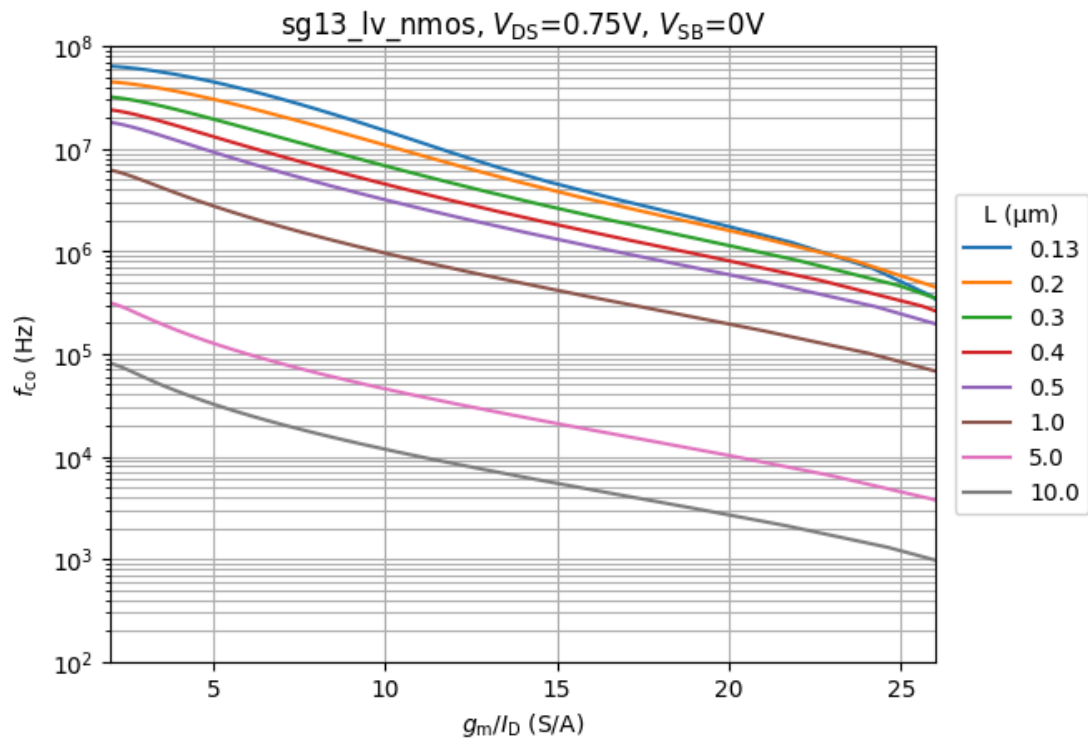As you can see in the following plot, f_{co} can reach well into the 10's of MHz for short MOSFETs, significantly degrading the noise performance of a circuit.



During the design phase, it might be convenient to have an overview of the most relevant sizing plots of the NMOS on one page. This overview can be downloaded [here](#).


3.3 PMOS Characterization in Saturation

In the following, we have the same plots as discussed in Section 3.2, but now for the PMOS.


i PMOS Sign Convention

In all PMOS plots we plot positive values for voltages and currents, to have compatible plots to the NMOS. Of course, in a PMOS, voltages and currents have different polarity compared to the NMOS.

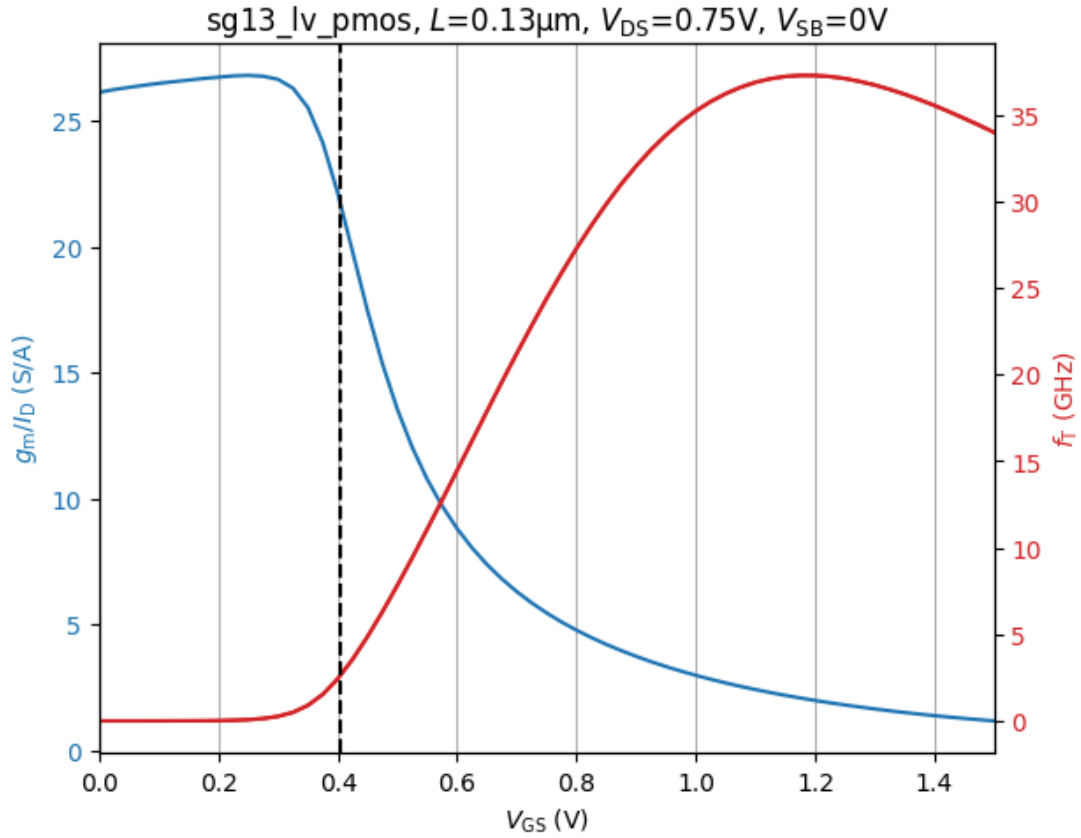g_m/I_D and f_T versus the gate-source voltage V_{GS} :



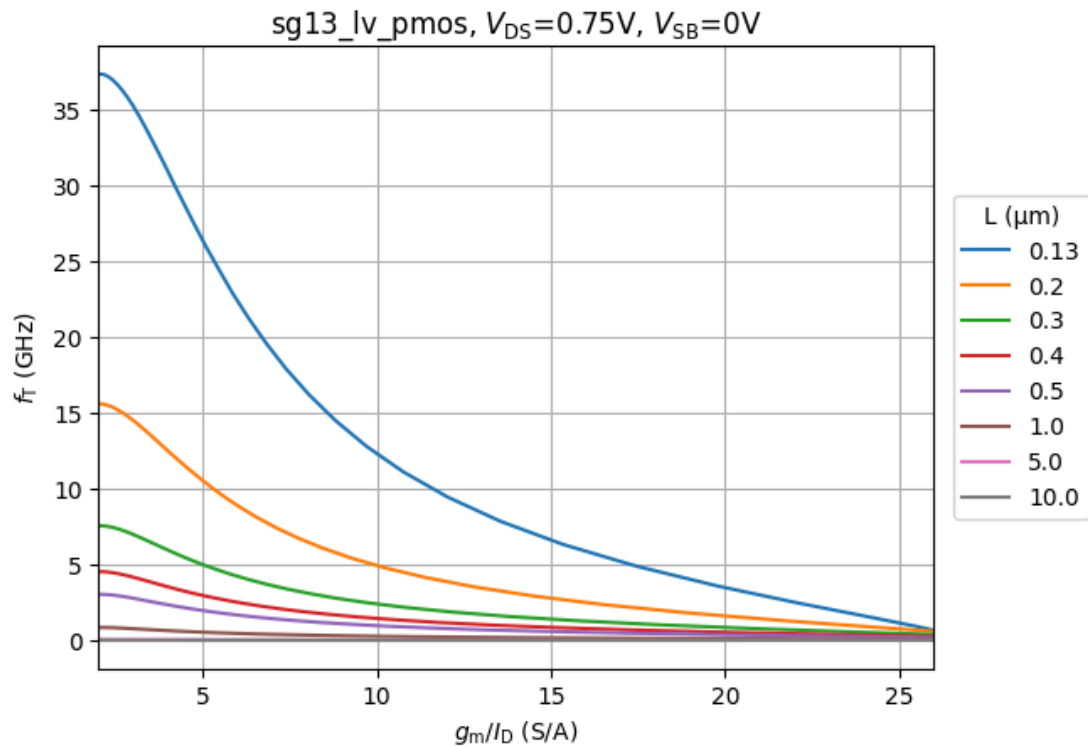
f_T against g_m/I_D for several different L . One can see a significantly lower top speed for the PMOS compared to the NMOS, which means for high-speed circuits the NMOS should be used. The reason for this is the approximately two to three times higher mobility of electrons compared to the mobility of holes.




g_m/g_{ds} versus g_m/I_D . Unfortunately, one can see a modelling error for the PMOS in this plot. The self gain g_m/g_{ds} reaches non-physical values, which indicates an issue with the g_{ds} modelling for the PMOS. We can not use these values for our circuit sizing, so we will use the respective NMOS plots also for the PMOS.

! Beware of Modelling Issues

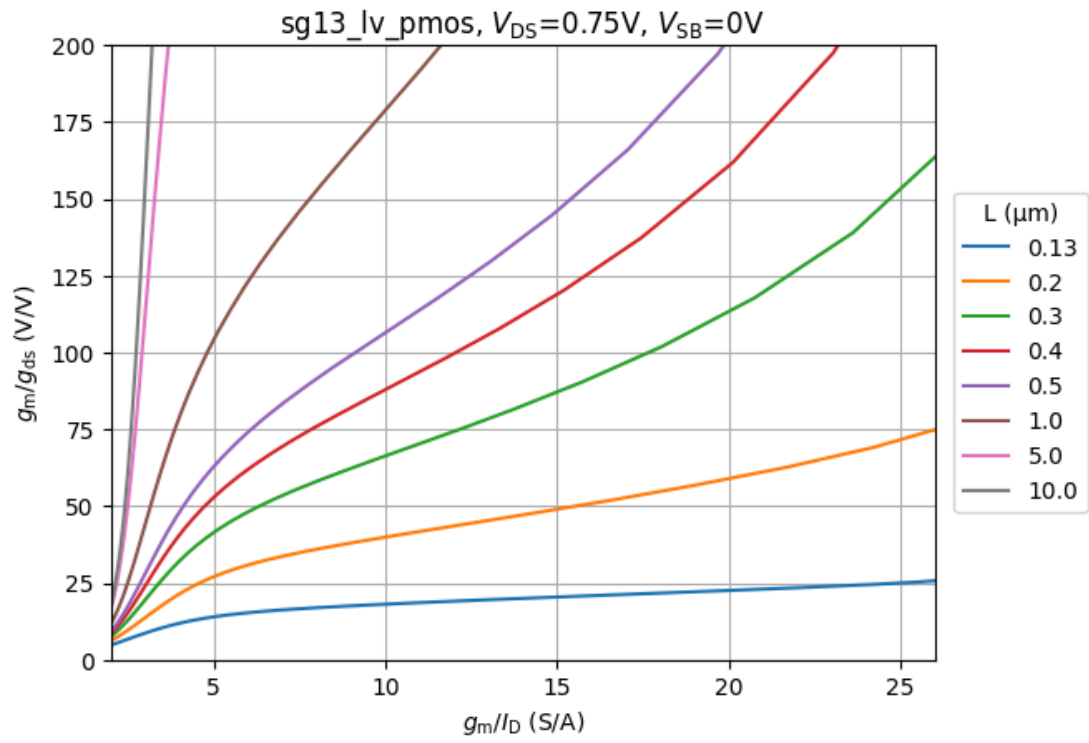
This example shows how important it is to benchmark the device models when starting to use a new technology. Modelling artifacts like the one shown are quite common, as setting up the device compact models and parametrize them according to measurement data is a very complex task. In any case, just be aware that modelling issues could exist in whatever PDK you are going to use!



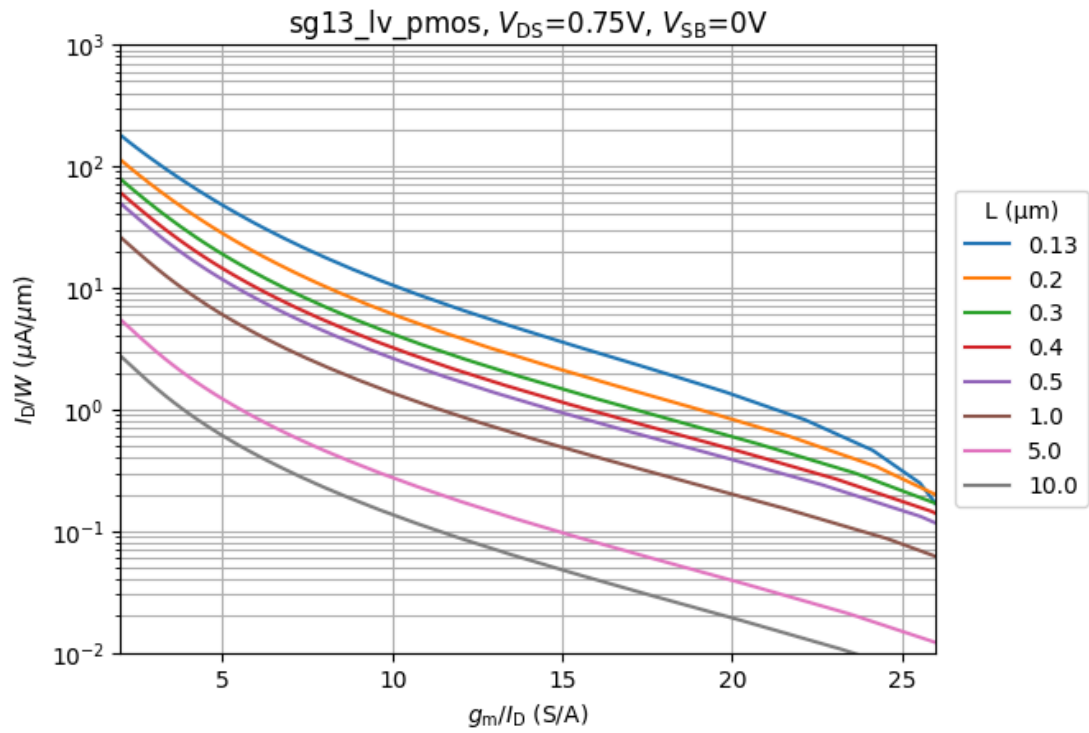
Drain current density I_D/W as a function of g_m/I_D and L :



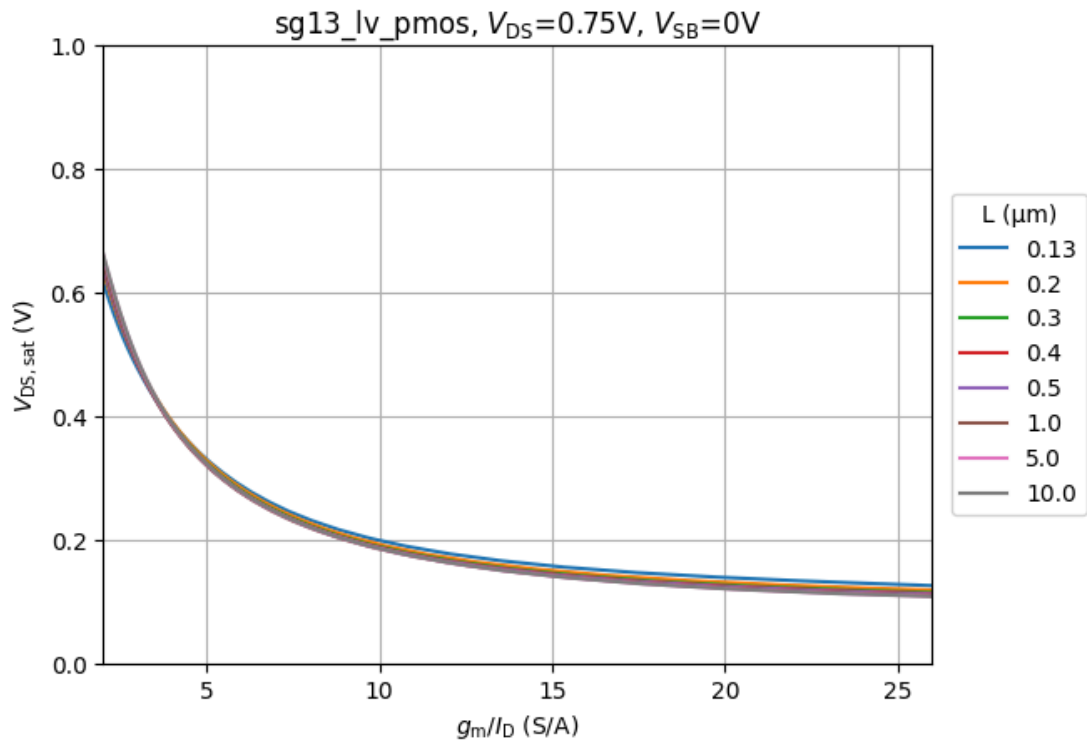Minimum drain-source voltage $V_{ds,sat}$ versus g_m/I_D and L :




Noise factor γ versus g_m/I_D and L :

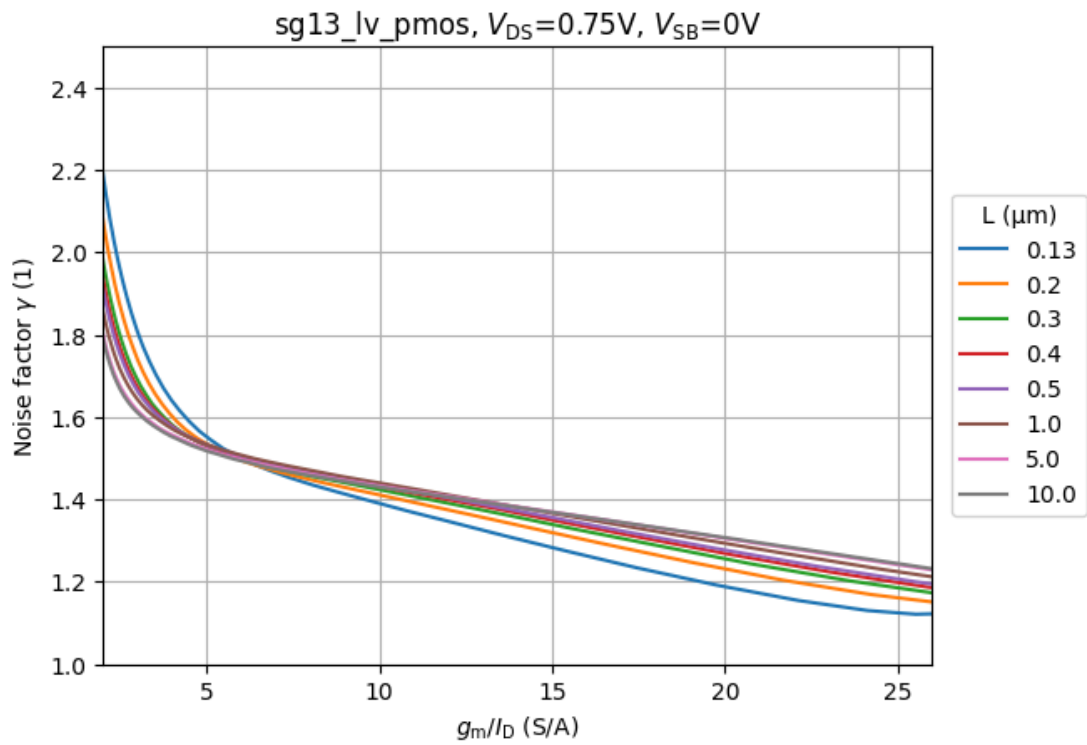

Flicker noise corner frequency f_{co} versus g_m/I_D and L . If you compare this figure carefully with the NMOS figure you can see that for some operating points the flicker noise for the PMOS is lower than for the NMOS. This is often true for CMOS technologies, so it can be an

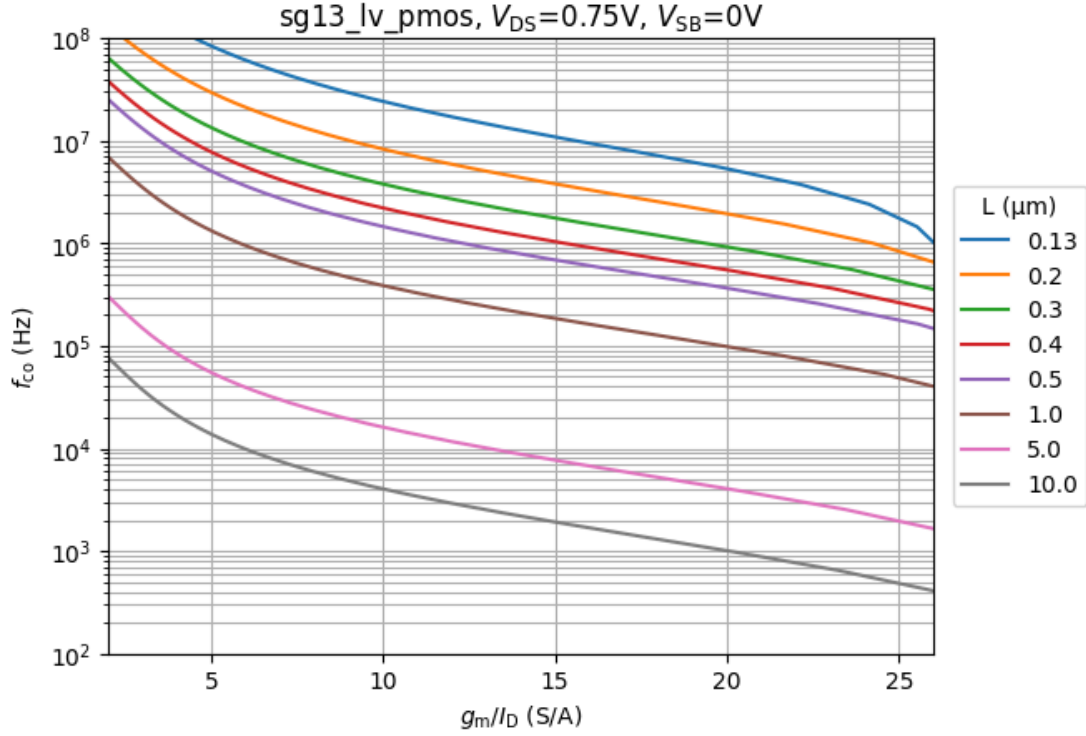advantage to use a PMOS transistor in places where flicker noise is critical, like an OTA input stage. Using PMOS has the further advantage that the bulk node can be tied to source (which for NMOS is only possible in a triple-well technology, which is often not available), which gets rid of the body effect.



During the design phase, it might be convenient to have an overview of the most relevant sizing plots of the PMOS on one page. This overview can be downloaded [here](#).

3.4 Tradeoffs in Saturation

In Figure 13, an overview of the tradeoffs mentioned above is presented. The design parameters are only shown once for their best-case implementation. Their worst-case value is then located at the opposite arrow. In conclusion, strong inversion with short channels is used for high-speed applications, whereas weak inversion with long channels is for low-power and low-noise applications. Moderate inversion with longer channels is used for current sources to maximize their output resistance. Note that the two arrows for strong inversion with long channels and weak inversion with short channels are empty since they make practically no sense. This tradeoff overview simplifies the choice of the starting g_m/I_D and L values in the sizing scripts.

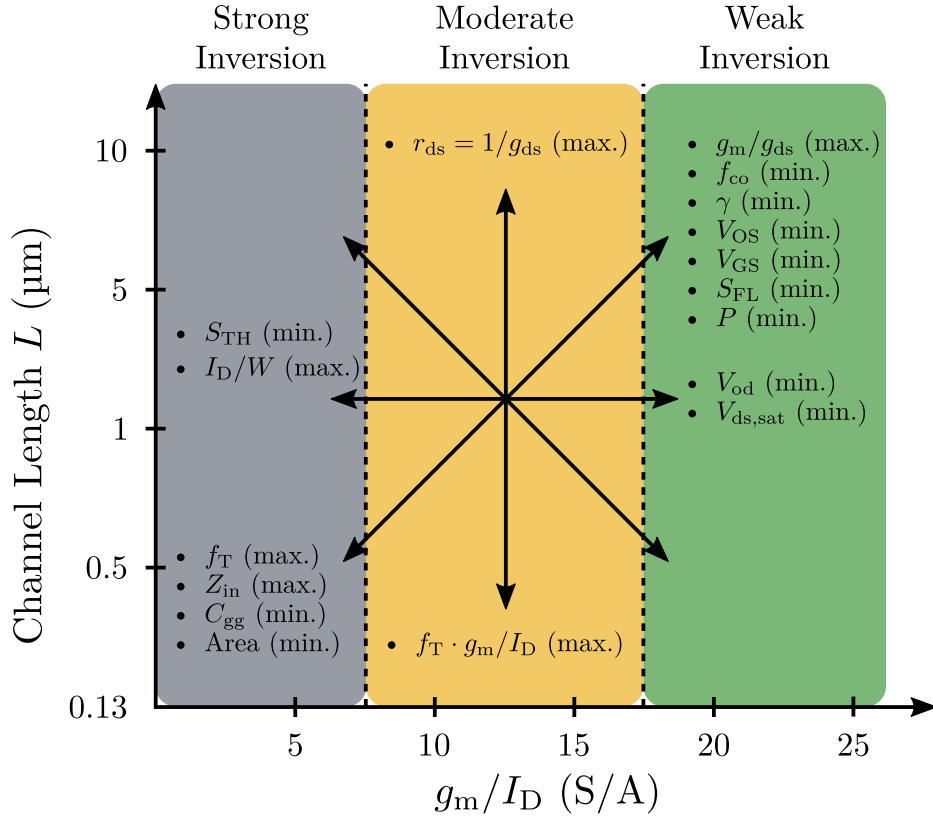


Figure 13: Overview of key design tradeoffs depending on the channel length L and transconductance efficiency g_m/I_D [13].


3.5 NMOS and PMOS Characterization in Triode

Besides using the MOSFET as a transconductor in saturation we often use the MOSFET as a switch in triode mode (to either switch voltages or currents). In this triode/switch mode of operation we are mainly interested in two parameters:


- The resistance of the switch/MOSFET when it is turned on ($R_{on} = 1/g_{ds}$).
- The shunt capacitance of the switch when it is turned off (C_{off} is defined by the coupling capacitances between drain and source).

In the operation of the NMOS as a switch the gate is usually pulled to V_{DD} and the bulk is permanently connected to V_{SS} to achieve the lowest R_{on} (to turn the switch off the gate is pulled towards V_{SS}). Likewise, to turn on a PMOS, the gate is usually pulled to V_{SS} and the bulk is connected to V_{DD} . In this situation the drain/source potential is somewhere between V_{DD} and V_{SS} , so the MOSFET will experience a $V_{SB} \neq 0$, leading to a quite noticeable bulk effect. Once the drain/source potential is sufficiently high for NMOS (low PMOS) the switch resistance will drastically degrade.

In order to get a feeling for the behavior of the MOSFET as a switch the following characterization plots show R_{on} and C_{off} for the NMOS and the PMOS, respectively. Both plots are for $L = L_{min} = 0.13\mu\text{m}$, as for switches usually minimum length devices are used. Only for special applications (e.g., the drain-source leakage current in off-mode is a concern) MOSFETs with increased L are used.

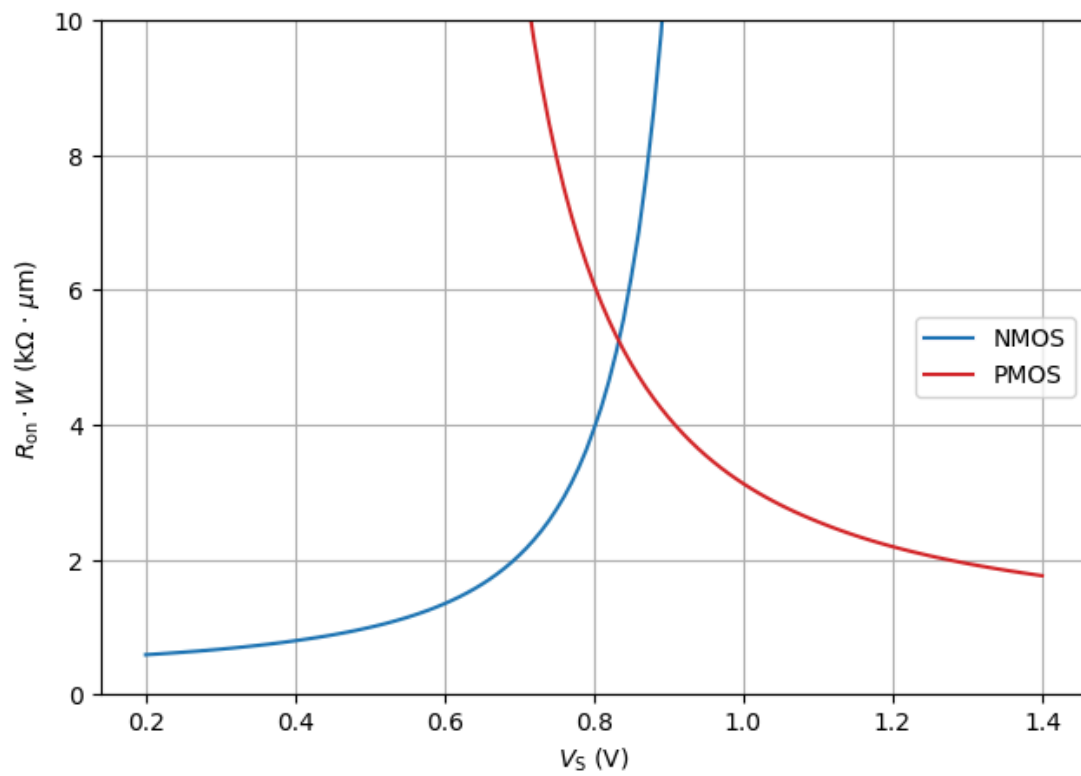

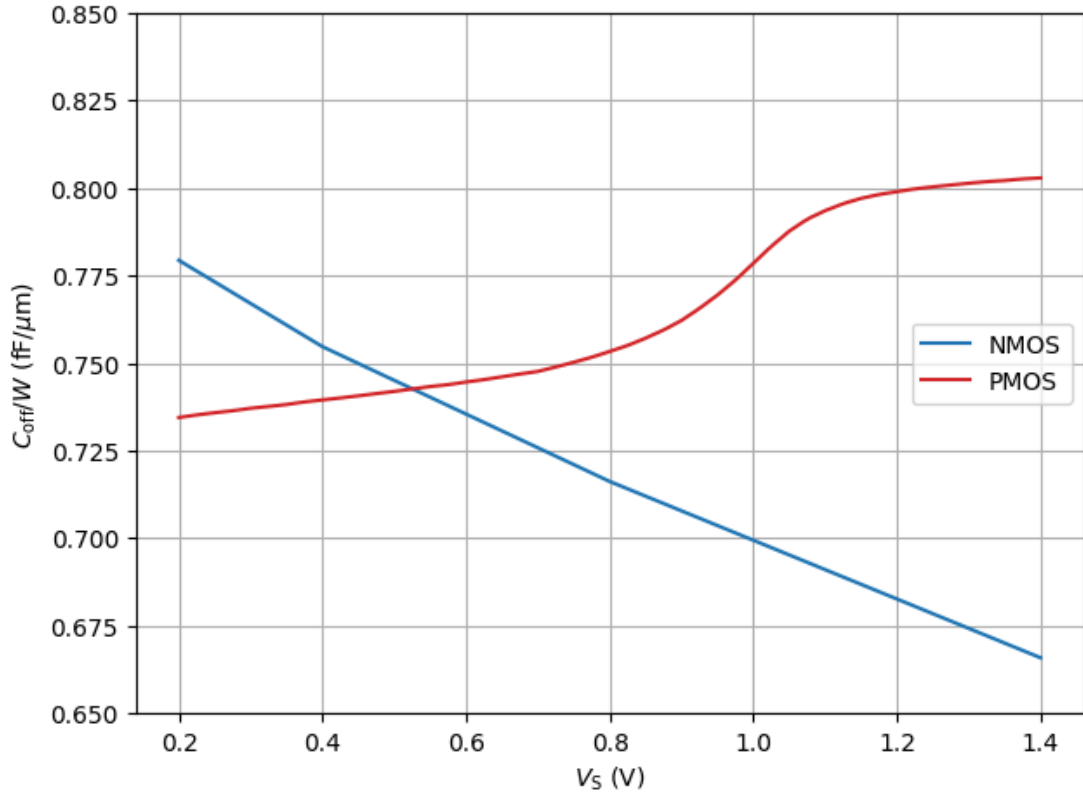As can be seen in the previous plot, an NMOS can be used to switch at potentials close to V_{SS} , while a PMOS is the better choice when switching at potentials close to V_{DD} . To construct a switch which can work for all voltage levels between V_{DD} and V_{SS} an NMOS is put in parallel to a PMOS, resulting in the well-known **transmission gate**.



As the switch on-resistance gets lower when increasing W , the off-capacitance gets larger. Thus, a good performance indicator for comparing switches in a given technology is the $R_{on}C_{off}$ product.

3.6 Tradeoffs in Triode

Some might think that sizing switches is a straightforward task, but in reality, they also come with several tradeoffs, and depending on the application, they can be incredibly complicated. The essential design parameters in switches are the on-resistance R_{on} , the off-capacitance C_{off} , the drain-source leakage current I_{leak} , and their impact on clock feedthrough and charge injection [14]. In Figure 14, an overview of the tradeoffs of these design parameters depending on the channel width W and the channel length L is presented. In conclusion, if W/L increases, R_{on} decreases, and the switching speed increases. If W/L decreases, I_{leak} , C_{off} , and the drain-source overlap capacitance decrease, effectively reducing clock feedthrough and charge injection [1]. Practically, it does not make sense to make the switch both wide and long.

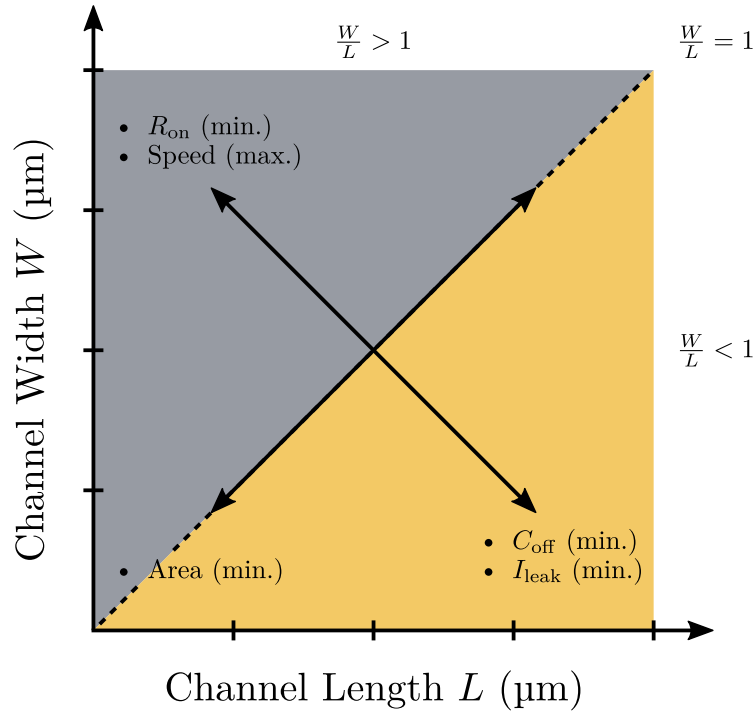


Figure 14: Overview of key design tradeoffs in switches depending on the channel width W and the channel length L [13].

4 First Circuit: MOSFET Diode

The first (simple) circuit which we will investigate is a MOSFET, where the gate is shorted with the drain, a so-called MOSFET “diode”, which is shown in Figure 15. This diode is one half of a current mirror, which we will investigate in Section 6.

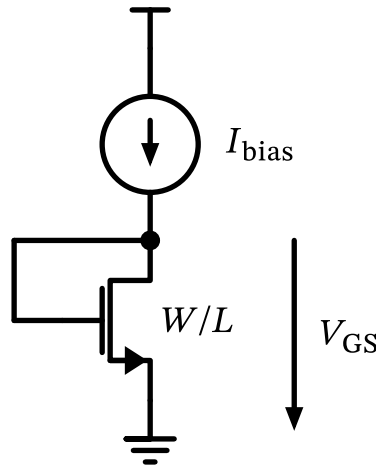


Figure 15: A MOSFET connected as a diode (drain shorted with gate).

Why look at a single-transistor circuit at all? By starting with the simplest possible circuit we can develop important skills in circuit analysis (setting up and calculating a small-signal model, calculating open-loop gain, calculating noise, etc.) and Xschem/ngspice simulation

testbench creation. We safely assume that the Mona Lisa also was not Leonardo da Vinci's first painting, so let's start slow.

This diode is usually biased by a current source, shown as I_{bias} in the figure. Depending on MOSFET sizing with W and L , a certain gate-source voltage V_{GS} will develop. This voltage can be used as a biasing voltage for other circuit parts, for example. For a representative MOSFET sizing the $V_{\text{GS}} = f(I_{\text{bias}})$ characteristic is shown in Figure 16. Note that in this MOSFET diode configuration $V_{\text{DS}} = V_{\text{GS}}$.

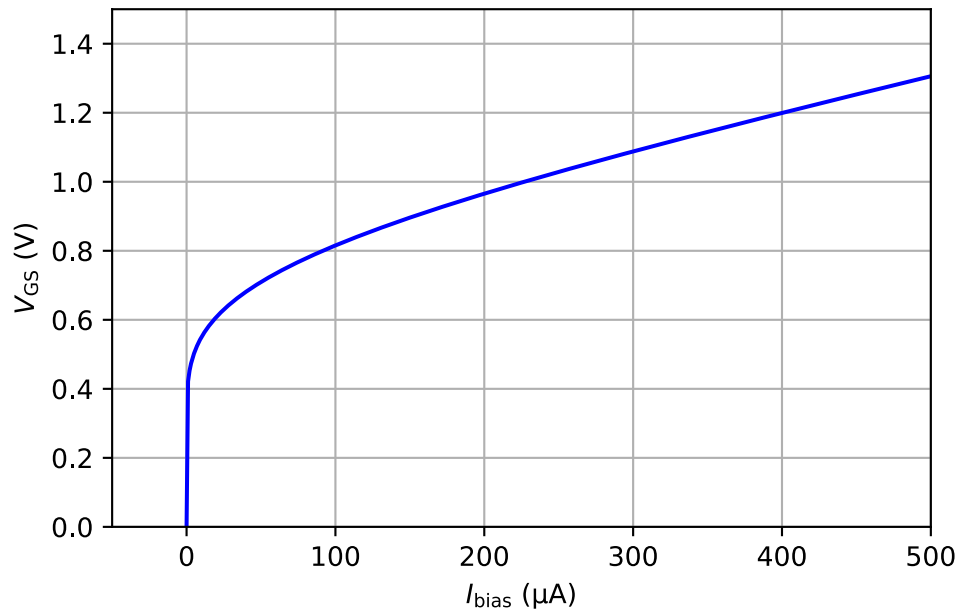


Figure 16: Gate-source voltage of a MOSFET diode with $W=1\mu\text{m}$ and $L=0.13\mu\text{m}$ showing the gate-source voltage as a function of the bias current.

If we flip Figure 16 by 90 degrees we can appreciate the name “MOSFET diode” as the characteristic resembles the one of a diode quite well (somewhat steep increase of the current beyond a certain threshold voltage). This is shown in Figure 17. Note that for negative V_{GS} the drain current is essentially zero, as the MOSFET is off, confirming the diode-like behavior.

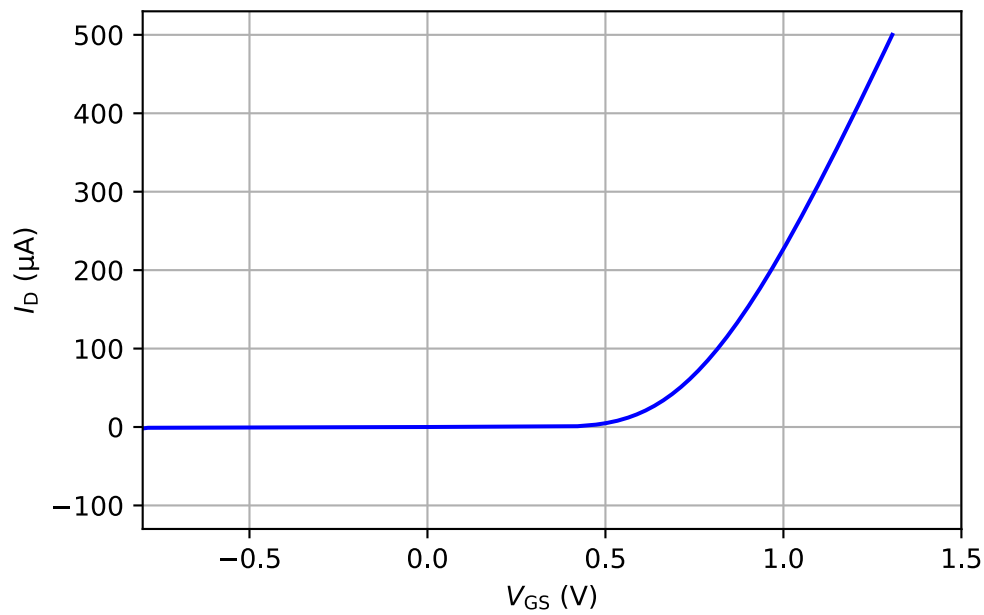


Figure 17: Drain current of a MOSFET diode with $W=1\mu m$ and $L=0.13\mu m$ showing the drain current as a function of the gate-source voltage.

i Feedback in the MOSFET Diode

It is important to realize that this configuration employs a feedback loop for operation. The voltage at the drain of the MOSFET is sensed by the gate, and the gate voltage changes until I_D is exactly equal to I_{bias} . In this sense this is probably the smallest feedback circuit one can build.

4.1 MOSFET Diode Sizing

We will now build this circuit in Xschem. For sizing the MOSFET we will use the g_m/I_D methodology introduced in Section 3.

💡 Exercise: MOSFET Diode Sizing

Please build a MOSFET diode circuit in Xschem where you use an LV NMOS, set $I_{bias} = 20 \mu A$, $L = 0.13 \mu m$, and we want to use $g_m/I_D = 10$ (often a suitable compromise between transistor speed and g_m efficiency).

1. Use the figures in Section 3.2 to find out the proper value for W .
2. What is the f_T for this MOSFET? What is the value for g_m and g_{ds} ?
3. Draw the circuit in Xschem, and simulate the operating point. Do the values match to the values found out before during circuit sizing?

Before continuing, please finish the previous exercise. Once you are done, compare with the below provided solution.

💡 Solution: MOSFET Diode Sizing

1. Using the fact that $I_{\text{bias}} = I_D = 20 \mu\text{A}$ and $g_m/I_D = 10$ directly provides $g_m = 0.2 \text{ mS}$.
2. Using the self-gain plot, we see that $g_m/g_{ds} \approx 18.4$, so $g_{ds} \approx 10.9 \mu\text{S}$. The f_T can easily be found in the respective plot to be $f_T = 23 \text{ GHz}$. Note that the self-gain has to be read at $V_{DS} = V_{GS} \approx 0.59 \text{ V}$, **not** at the $V_{DS} = V_{DD}/2$ used for the characterization plots in Section 3.2: in a MOSFET diode the drain is tied to the gate, and g_{ds} is a strong function of V_{DS} . The linked notebook does this self-consistently.
3. The W of the MOSFET we find using the drain current density plot and the given bias current. Rounding to half-microns results in $W = 1 \mu\text{m}$.
4. Since we are looking at the graphs, we further find $\gamma = 0.81$, $V_{ds,\text{sat}} = 0.18 \text{ V}$, and $f_{co} \approx 16 \text{ MHz}$.
5. In addition, we expect $V_{GS} \approx 0.6 \text{ V}$.

You can find an example Jupyter notebook to accurately extract these values here. An Xschem schematic for this exercise is provided as well.

4.2 MOSFET Diode Large-Signal Behavior

As discussed above, the MOSFET diode configuration is essentially a feedback loop. Before we will analyze this loop in small-signal, we want to investigate how this loop settles in the time domain, and by doing this we can observe the large-signal settling behavior. To simulate this, we change the dc bias source from the previous example to a transient current source, which we will turn on after some picoseconds. The resulting Xschem testbench is shown in Figure 18.

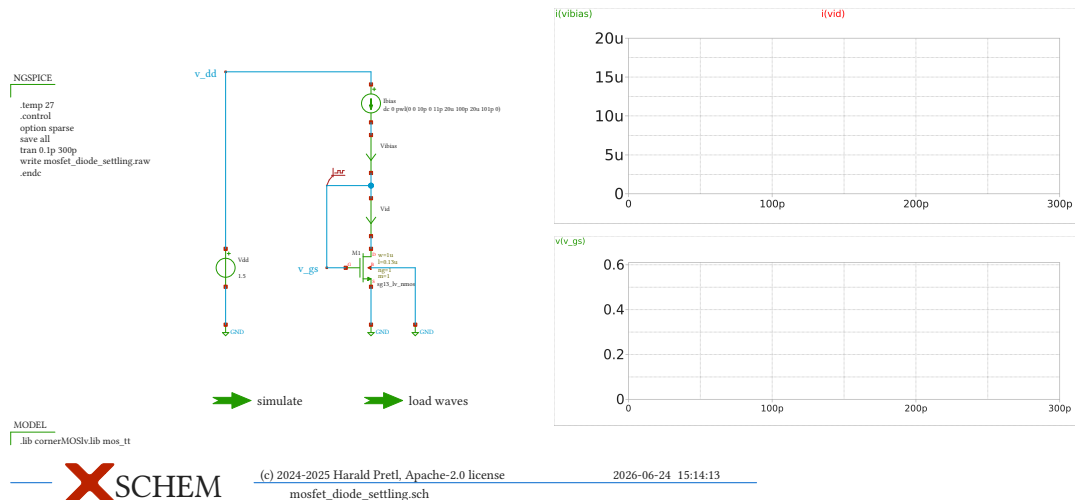


Figure 18: Testbench for MOSFET diode transient settling.

When simulating the circuit in Figure 18 another interesting effect can be observed: While the turn-on happens quite rapidly (essentially the bias current source charges the gate capacitance, until the gate-source voltage is large enough that the drain current counteracts the bias current), the turn-off shows a very long settling tail. This is due to the fact that as the gate capacitance is discharged by the drain current, the V_{GS} drops, which in turn reduces the drain current, which will make the discharge even slower. We have an effect similar to a capacitor discharge by a diode [15].

! Power-Down Switches

It is thus generally a good idea to add power-down switches to the circuits to disable the circuit quickly by pulling floating nodes to a defined potential (usually V_{DD} or V_{SS}) and to avoid long intermediate states during power down. This will also allow a turn-on from a well-defined off-state.

Exemplary implementations of power-down switches are shown in the Xschem implementation of the improved OTA in Figure 78. Which W/L ratio should these transistors have? Well, in general, switches often have minimum length to be fast and to have low R_{on} . However, if there are no critical specifications (e.g., like power-down time), then these transistors are often used as dummy transistors for other circuit parts and are sized to fit the layout best.

4.3 MOSFET Diode Small-Signal Analysis

We now want to investigate the small-signal behavior of the MOSFET diode. Based on the small-signal model of the MOSFET in Figure 6 we realize that gate and drain are shorted, and we also connect bulk to source. We can thus simplify the circuit to the one shown in Figure 19.

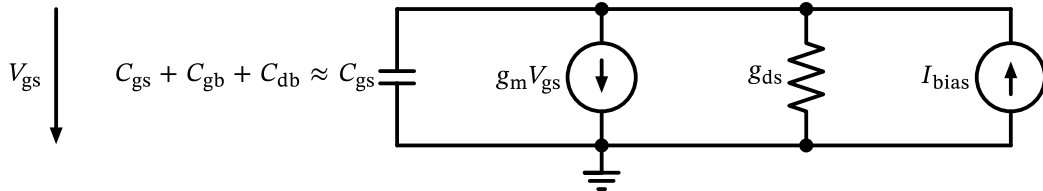


Figure 19: The MOSFET diode small-signal model (drain and gate are shorted, as well as source and bulk).

i Ground Node Selection

For small-signal analysis we would not need to declare one node as the ground potential. However, when doing so, and selecting the ground node strategically, we can simplify the analysis, as we usually do not formulate KCL for the ground node (as we have only $N - 1$ independent KCL equations, N being the number of nodes in the circuit), and the potential difference equations are simpler if one node is at $0 V$.

For calculating the small-signal impedance of the MOSFET diode we formulate Kirchhoff's current law (KCL, also Kirchhoff's first law or Kirchhoff's junction rule) at the top node to get

$$I_{\text{bias}} - sC_{\text{gs}} V_{\text{gs}} - g_{\text{m}} V_{\text{gs}} - g_{\text{ds}} V_{\text{gs}} = 0.$$

It follows that

$$Z_{\text{diode}}(s) = \frac{V_{\text{gs}}}{I_{\text{bias}}} = \frac{1}{g_{\text{m}} + g_{\text{ds}} + sC_{\text{gs}}}. \quad (5)$$

When neglecting g_{ds} , at dc we get $Z_{\text{diode}} = 1/g_{\text{m}}$, which is an important result and should be memorized.

! The Admittance is Your Friend

In circuit analysis it is often algebraically easier to work with admittance instead of impedance, so please remember that Ohm's law for a conductance is $I = G \cdot V$, and for a capacitance is $I = sC \cdot V$. When writing equations, it is also practical to keep sC together, so we will strive to sort terms accordingly.

Looking at Equation 5 we see that for low frequencies, the diode impedance is resistive, and for high frequencies it becomes capacitive as the gate-source capacitance starts to dominate. The corner frequency of this low-pass can be calculated as

$$\omega_c = \frac{g_{\text{m}} + g_{\text{ds}}}{C_{\text{gs}}} \approx \omega_{\text{T}}$$

which is pretty much the transit frequency of the MOSFET!

4.4 MOSFET Diode Stability Analysis

i Open-Loop Gain, Closed-Loop Gain, and Loop-Gain—A Short Recap

Figure 20 shows a generic negative feedback system with input $X(s)$ and output $Y(s)$, where $H_{ol}(s)$ is the transfer function of the feed-forward path (also called **open-loop gain**) and $G(s)$ is the transfer function of the feedback network. The **loop-gain** is the product of both transfer functions $T(s) = H_{ol}(s)G(s)$ and is used for the stability analysis. The **closed-loop** gain is defined as $H_{cl}(s) = Y(s)/X(s)$ can be derived with $Y(s) = H_{ol}(s)[X(s) - Y(s)G(s)]$ to be

$$H_{cl}(s) = \frac{Y(s)}{X(s)} = \frac{H_{ol}(s)}{1 + H_{ol}(s)G(s)} = \frac{H_{ol}(s)}{1 + T(s)} \quad (6)$$

If the open-loop gain is sufficiently large $H_{ol}(s) \gg 1$, then the closed-loop gain simplifies to $H_{cl}(s) \approx 1/G(s)$. This result is convenient, since it is independent of $H_{ol}(s)$. Therefore, the overall gain is only set with the feedback gain $G(s)$ in operational amplifier circuits.

In the case of the MOSFET diode, $G(s) = 1$ and therefore $T(s) = H_{ol}(s)$ and $H_{cl}(s) \approx 1$.

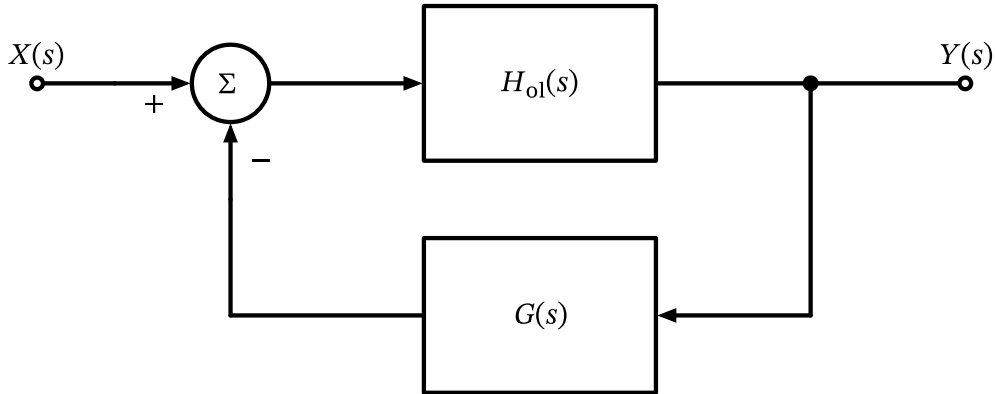


Figure 20: The block diagram of a negative feedback system.

Note that the feedback system depicted above shows an inversion in the feedback path. Sometimes this inversion is also included in the definition of $G(s)$. Please be aware of this when reading literature, as different conventions exist.

i Gain-Bandwidth Product in Feedback Systems

The gain-bandwidth product (GBP or GBWP) or transit frequency f_T of a first-order open-loop system is the product of the open-loop dc gain $H_{ol,dc} = H_{ol}(f = 0 \text{ Hz})$ and the open-loop -3 dB cut-off frequency $f_{c,ol}$ of $H_{ol}(s)$.

$$\text{GBWP} = f_{T,ol} = H_{ol,dc} f_{c,ol}$$

If a frequency-independent negative feedback G (e.g., a resistive divider) is applied to this open-loop system, the closed-loop -3 dB cut-off frequency $f_{c,cl}$ follows from the open-loop transit frequency and the feedback gain as

$$f_{c,cl} = H_{ol,dc} f_{c,ol} G = f_{T,ol} G$$

i.e. the bandwidth is extended by exactly the factor by which the gain is reduced. The **gain-bandwidth product is therefore preserved** by the feedback,

$$H_{cl,dc} f_{c,cl} \approx \frac{1}{G} f_{T,ol} G = f_{T,ol},$$

which is the reason the GBWP is such a useful figure of merit.

What *does* change is the frequency at which the closed-loop gain itself crosses unity:

$$f_{T,cl} = f_{T,ol} \sqrt{1 - G^2}$$

Note that this is **not** the same quantity as the GBWP, even though the two coincide in the open-loop case — this distinction is a common source of confusion. For weak feedback ($G \ll 1$) the closed-loop unity-gain frequency is only slightly lower than $f_{T,ol}$, but for strong feedback it drops sharply, and for the unity-gain case $G = 1$ it vanishes altogether, simply because the closed-loop gain $H_{cl} = H_{ol}/(1 + H_{ol}) < 1$ never reaches unity in the first place. Keep this in mind for the MOSFET diode, where exactly this case $G = 1$ applies.

This theory might be interesting when Middlebrook's and Tian's methods for loop gain analysis are later compared in the MOSFET diode testbench (see Figure 22).

The diode-connected MOSFET forms a feedback loop. What is the loop gain? For calculating it, we are breaking the loop, and apply a dummy C_{gs}^* at the right side to keep the impedances correct. A circuit diagram is shown in Figure 21, we break the loop at the red crosses. As we can see in this example, it is critically important when breaking up a loop for analysis (also for simulation!) to keep the terminal impedances the same. Only in special cases where the load impedance is very high or the driving impedance is very low is it acceptable to disregard loading effects!

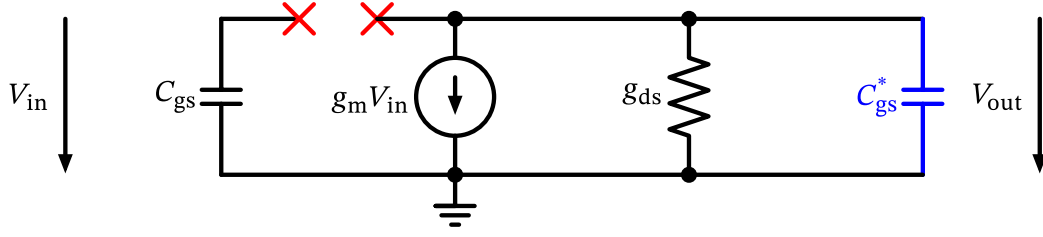


Figure 21: The MOSFET diode small-signal circuit for open-loop analysis.

We are now driving (with a voltage source) V_{in} and record the output voltage V_{out} to find the loop gain $T(s)$. By inspecting Figure 21 we see that

$$V_{out} = -g_m V_{in} \frac{1}{g_{ds} + sC_{gs}}.$$

The loop gain $T(s)$ is thus

$$T(s) = (-1) \cdot \frac{V_{out}}{V_{in}} = \frac{g_m}{g_{ds} + sC_{gs}} = \frac{g_m}{g_{ds}} \frac{1}{1 + sC_{gs}g_{ds}^{-1}}. \quad (7)$$

Inspecting Equation 7 we realize that:

1. The dc gain g_m/g_{ds} is the self-gain of the MOSFET, so $20 \log_{10}(0.2 \cdot 10^{-3}/10.9 \cdot 10^{-6}) = 25.3$ dB.
2. There is a pole at $s_p = -g_{ds}/C_{gs}$, i.e. at a frequency of $f_p = 10.9 \cdot 10^{-6}/(2\pi \cdot 1.4 \cdot 10^{-15}) = 1.25$ GHz.

With this single pole location in $T(s)$ this loop is perfectly stable under all conditions (remember that a single pole results in a maximum phase shift of -90°).

The question is now how to simulate this loop gain, i.e., how to break the loop open in simulation? In general there are various methods, as we can use artificially large (ideal) inductors and capacitors to break loops open and still establish the correct dc operating points for the ac loop analysis. This is called **Rosenstark's method** [16]. However, mimicking the correct loading can be an issue, and requires a lot of careful consideration.

There is an alternative method which breaks the loop open only by adding an ac voltage source in series (thus keeps the dc operating point intact), or injects current using an ac current source. Based on both measurements the loop gain can be calculated. This is called **Middlebrook's method** [17] and is based on double injection, and we will use it for our loop simulations. This method is detailed in Section 16.

There are several other methods like Tian's method [18], for example. A comprehensive overview can be found in [19] which describes ten different simulation-based loop gain analysis methods.

We now want to simulate the loop transfer function $T(s)$ by using Middlebrook's and Tian's method and confirm our analysis above.

Exercise: MOSFET Diode Loop Analysis

Please build a simulation testbench in Xschem to simulate the open-loop transfer function of the MOSFET diode. Confirm the dc gain and pole location as given by Equation 7.

If you are getting stuck you can look at this Xschem testbench, shown in Figure 22.

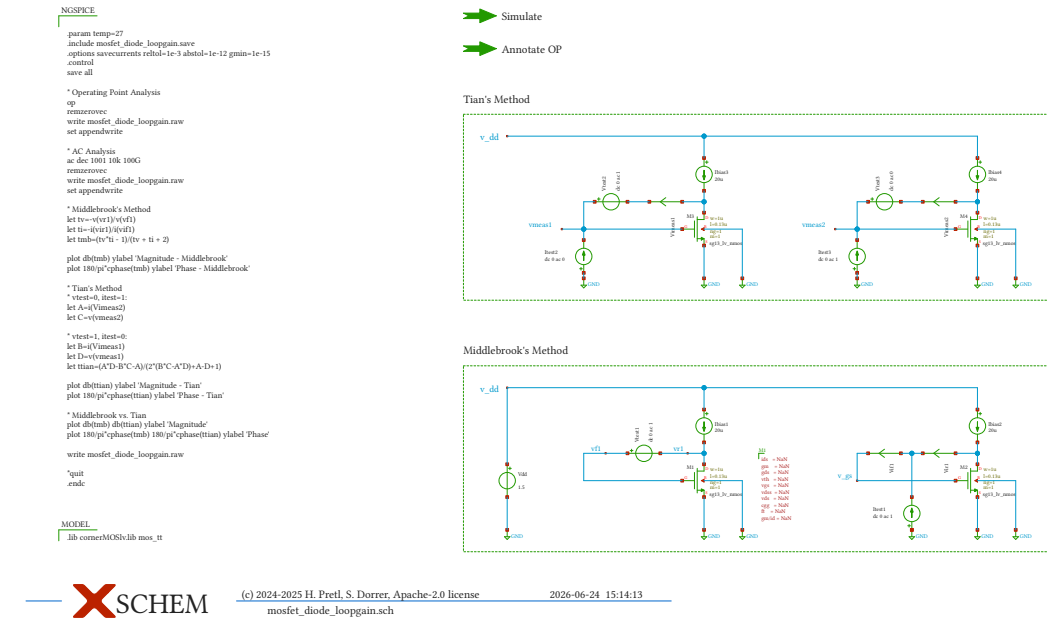


Figure 22: Testbench for MOSFET diode stability analysis.

From simulation we see that the open-loop gain is 24.9 dB at low frequencies, which matches our prediction of 25.3 dB very well. In the Bode plot we see a low-pass with a -3 dB corner frequency of 1.4 GHz, which again is close to our prediction of 1.25 GHz.

! What About Large-Signal Stability?

Keep in mind that the above simulation only verifies the small-signal stability in one certain operating point. If we later look at the stability of an OTA it might be a good idea to verify the small-signal stability in different operating points.

Furthermore, one can apply a step response to the closed-loop system input and estimate the phase margin from the overshoot at the output (see “Automatic Control” lecture). One could also use a step-wise step response to simulate different operating points for a certain time (see “Introduction in Integrated Circuit Design” lecture).

4.5 MOSFET Diode Noise Calculation

As a final exercise on the MOSFET diode circuit we want to calculate the output noise when we consider V_{GS} the output reference voltage which is created when passing a bias current through the MOSFET diode. The bias current we will assume noiseless.

We are going to use the small-signal circuit shown in Figure 23.

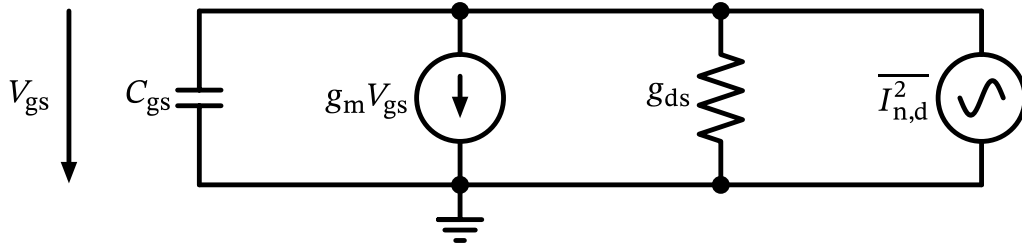


Figure 23: The MOSFET diode small-signal model with drain noise source.

As we have already calculated the small-signal diode impedance in Equation 5 we will use this result, and just note that the drain current noise of the MOSFET flows through this impedance. The noise voltage at V_{gs} is thus given as

$$\overline{V_n^2} = |Z_{\text{diode}}|^2 \overline{I_{n,d}^2}.$$

The drain current noise of the MOSFET is given as (introduced in Section 2.1.2)

$$\overline{I_{n,d}^2} = 4kT\gamma g_m.$$

For low frequencies (ignoring g_{ds} and C_{gs}) we get

$$\overline{V_n^2} = |Z_{\text{diode}}|^2 \overline{I_{n,d}^2} = \frac{1}{g_m^2} 4kT\gamma g_m = \frac{4kT\gamma}{g_m}$$

which is the thermal noise of a resistor of value $1/g_m$ enhanced by the factor γ .

We now calculate the full equation, and after a bit of algebra arrive at

$$\overline{V_n^2}(f) = \frac{4kT\gamma g_m}{(g_m + g_{ds})^2 + (2\pi f C_{gs})^2}. \quad (8)$$

If we are interested in the PSD of the noise then Equation 8 gives us the result. If we are interested in the rms value (the total noise) we need to integrate this equation, using the following identity:

i Useful Integral for Noise Calculations

$$\int_0^\infty \frac{a}{b^2 + c^2 f^2} df = \frac{\pi}{2} \frac{a}{b \cdot c} \quad (9)$$

Using the integral help in Equation 9, we can easily transform Equation 8 to

$$V_{n,\text{rms}}^2 = \int_0^\infty \overline{V_n^2}(f) df = \frac{kT\gamma g_m}{(g_m + g_{ds}) C_{gs}}. \quad (10)$$

The form of Equation 10 is the exact solution, but we gain additional insight if we assume that $g_m + g_{ds} \approx g_m$ and then

$$V_{n,\text{rms}}^2 = \frac{kT\gamma}{C_{\text{gs}}}. \quad (11)$$

Inspecting Equation 11 we see our familiar kT/C noise multiplied by the factor γ !

💡 Exercise: Total Output Noise of RC-Lowpass

If you have never calculated this before then you should work through the following: Calculate the total output noise of an RC -lowpass filter. Formulate the transfer function in the Laplace domain, and put the equivalent resistor noise voltage source at the input, calculate the transfer to the output, and then integrate the output PSD (like we did for the MOSFET diode noise).

You will find that the output noise is

$$V_{n,\text{rms}}^2 = \frac{kT}{C}$$

which is independent of R ! This is a surprising result, and is the well-known kT/C noise. Intuitively, we could argue that the noise increases with larger R , but at the same time, the bandwidth decreases and therefore R does not add additional noise. More detailed information and an intuitive explanation of kT/C noise can be found in [20].

Side note: The shortest derivation of this formula involves the equipartition theorem: Any system in thermal equilibrium with a reservoir of temperature T has a fluctuation energy of $kT/2$ per degree of freedom. This RC system has one degree of freedom in the voltage on the capacitor, and the stored energy in the capacitor is $CV_{\text{rms}}^2/2$. Equating both energies we find that $V_{\text{rms}}^2 = kT/C$ [21].

To calculate the total output noise of a generalized passive network Bode's noise theorem is quite practical (see Section 17.2).

Calculating the rms noise voltage for our MOSFET diode we get

$$\sqrt{V_{n,\text{rms}}^2} = \sqrt{\frac{1.38 \cdot 10^{-23} \cdot 300 \cdot 0.81}{1.4 \cdot 10^{-15}}} = 1.56 \text{ mV},$$

which is a sizeable value! Think about it, can this rms noise voltage be measured with an oscilloscope? If not, why? We run circuits in this technology at $V_{\text{DD}} = 1.5 \text{ V}$, which leaves us with a signal swing of ca. $1.1 \text{ V}_{\text{pp}}$ (single-ended), resulting in a dynamic range in this case of $20 \log_{10}(0.39/1.56 \cdot 10^{-3}) \approx 48 \text{ dB}$ assuming a sinusoidal signal. In order to get a feeling which dynamic range is “good”, we can calculate the required dynamic range of a 16-bit audio ADC to be $6.02 \cdot 16 + 1.76 \text{ dB} = 98.08 \text{ dB} \approx 100 \text{ dB}$. This calculation should make clear that, for example, the correct sizing of the sample&hold capacitor is crucial for low rms noise voltage.

! Be Careful with Parasitic Capacitances in IC Design

In general, in integrated circuit design, we often have only small parasitic capacitances on many nodes that could sum up to unwanted high noise according to Equation 11. If one wants to lower the noise an increased capacitance could limit the bandwidth (and thus the kT/C noise).

! Large Bandwidth and Noise

Remember: Large bandwidth circuits integrate noise over a wide bandwidth resulting in (potentially) considerable rms noise. The way to lower the total noise is to lower the PSD of the noise contributions, which usually requires increased power consumption. So in a nutshell:

Large bandwidth plus small noise equals large power consumption.

💡 Exercise: MOSFET Diode Noise

Please build a simulation testbench in Xschem to simulate the noise performance of the MOSFET diode, and confirm the rms noise value that we just calculated. Look at the rms value and the PSD of the noise, and play around with the integration limits. What is the effect? Can you see the flicker noise in the PSD? How much is its contribution to the rms noise? What is the value of f_{co} , and does it correspond to the above calculated one?

If you are getting stuck you can look at this Xschem testbench, shown in Figure 24.

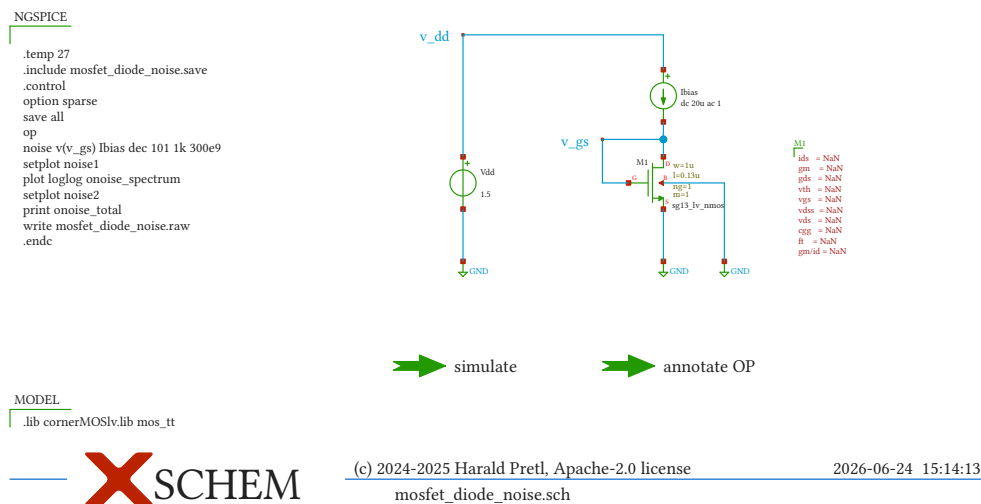


Figure 24: Testbench for MOSFET diode noise analysis.

4.6 Conclusion

In this section we investigated the simple MOSFET-diode circuit. We learned important skills like how to derive a small-signal model and how to calculate important features like noise and open-loop gain for stability analysis. We introduced Middlebrook's method to have a mechanism to open up loops in simulation (and calculation) without disturbing dc operating points or introduce errors by changing loading conditions.

If you feel that you have not yet mastered these topics or are uncertain in the operation of Xschem or ngspice, please go back to the beginning of the section and read through the theory and redo the exercises.

5 Common-Source Amplifier

We now want to step up our game, and use more components to design something useful. We will use a basic circuit structure, namely a single-ended common-source amplifier. The structure of this circuit, using a resistor as a load, is shown in Figure 25.

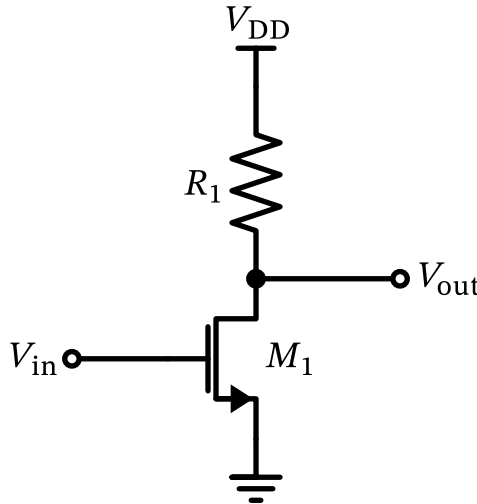


Figure 25: A MOSFET common-source amplifier with resistive load.

The function of this circuit is as follows: Assuming the MOSFET M_1 is kept in saturation, then a small-signal voltage V_{in} applied at the gate is converted into a drain current I_d by the MOSFET's transconductance g_m . Then, this current is converted into a voltage again in the resistor R_1 . Ultimately, we have a dc voltage gain A_v of

$$A_v = \frac{V_{out}}{V_{in}} \approx -\frac{g_m V_{in} R_1}{V_{in}} = -g_m R_1.$$

As explained above, it is a good approach to see electronic circuit components as

- **voltage-to-current** converter (MOSFET as common-source or common-gate; resistor),
- **current-to-voltage** converter (resistor),
- **current-to-current** converter (MOSFET as common-gate), and
- **voltage-to-voltage** converter (MOSFET as common-drain)

for better understanding.

5.1 Sense Amplifier Driving 50 Ohm Matched Load

Let us now size and design an exemplary implementation of this amplifier (of course using the g_m/I_D method). In order to have useful real-life specifications, we want to build an amplifier which can be used to sense an on-chip voltage and drive off-chip measurement equipment. Often, this equipment has an input impedance of 50Ω , and we want to have an impedance-matched output. The voltage gain shall be set to 1 (essentially, we want to sense a voltage and drive the measurement equipment).

The resulting circuit is shown in Figure 26. As the load is usually ground-referred, and we want to avoid a dc-block at the output, we use a PMOS amplifier stage (compare with Figure 25).

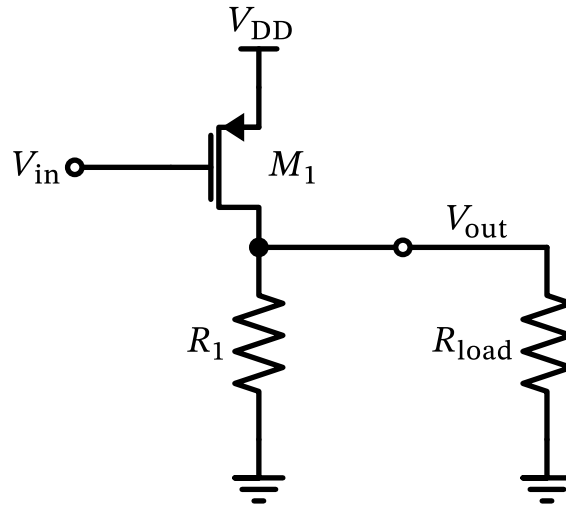


Figure 26: A MOSFET common-source amplifier with 50 Ohm load.

💡 Exercise: PMOS-Based Measurement Amplifier

Please think about why exactly we want this measurement amplifier to be based on a PMOS instead of an NMOS.

The power matching requirement at the output mandates that $R_1 = R_{\text{load}}$, so $R'_1 = R_{\text{load}} \parallel R_1 = 25\Omega$. The voltage gain requirement of $|A_v| = 1$ results in $g_m = 1/R'_1 = 40\text{ mS}$.

We now need to find W and L of M_1 and calculate the required bias current I_D . We also need to find the proper V_{GS} to set this current. As usual, we use a Jupyter notebook to calculate these values. Since we require modest speed of this buffer, we use a $g_m/I_D = 8$ and set $L = 0.13\mu\text{ m}$. The notebook is available [here](#). The resulting circuit including all component values is shown at the end of the notebook (the red input capacitor shows the C_{gg} of the MOSFET).

! Important 1: MOSFET Parameters NG and M

When sizing the MOSFET for this example we found that we need a fairly large W , resulting in a MOSFET aspect ratio of $W/L \gg 1000$. When constructing an integrated circuit out of individual MOSFETs, we strive for an overall IC dimension that is roughly square. For MOSFET with large aspect ratios we need to get them into a comfortable shape.

In order to achieve this, we construct the MOSFET out of smaller pieces, and the size of these pieces (called “gate fingers”) is controlled by the parameter `ng`. These MOSFET gate fingers all have the same L , but their width is $W_{\text{finger}} = W/\text{ng}$. All these individual smaller MOSFETs are connected in parallel.

In order to increase the MOSFET model accuracy, often the maximum value of W_{finger} is limited. In the case of SG13G2 $W_{\text{finger}} \leq 10 \mu\text{ m}$.

In order to construct even larger MOSFETs, we can connect multiple MOSFETs in parallel. We can do this in the circuit editor by placing and connecting these MOSFETs; but since this is often used there is a more convenient way: By using the parameter `m` (“multiplier” or “multiplicity”) we instantiate m MOSFETs connected in parallel.

When to use `ng` and when to use `m`? The use of `ng` results in a more compact IC layout, and is thus generally preferable. Only in certain instances (e.g., when using a really large W) `m` should be used. Further, the thoughtful use of `ng` **allows one to construct all the NMOS and PMOS of a circuit out of the same gate finger elements**. This will result in a very compact layout!

Exercise: Measurement Amplifier Simulation

Please go through the sizing notebook of the measurement amplifier and double-check the calculations. Do you agree that the calculations are correct?

Once you agree with the circuit sizing please build an Xschem simulation testbench where you simulate the small-signal voltage gain A_v of this measurement amplifier if it is driven with an ideal voltage source. Keep in mind that the maximum MOSFET finger width is $10\mu\text{m}$ in this technology, so you need to set the parameter `ng` accordingly (see Important 1).

- What is the dc gain of this amplifier when loaded with 50Ω ?
- The dc gain is likely not exactly 0 dB. Why is this so?
- Increase the width W of the PMOS until the gain is correct. What is the W that you had to set, and how much is I_D now?
- What is the bandwidth (i.e., the -3 dB corner frequency) of the output voltage, when the voltage source has a source resistance of $1\text{k}\Omega$?

If you get stuck, here is the solution to this exercise, and it is also shown in Figure 27.

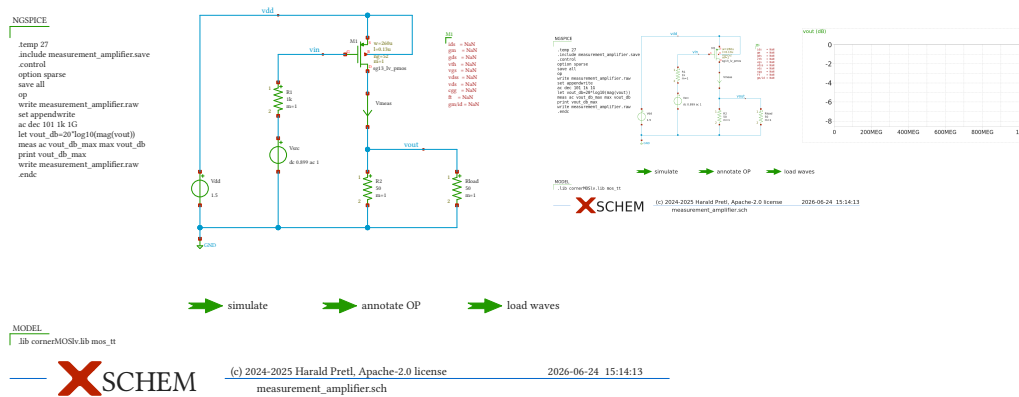


Figure 27: Simulation schematic of the common-source measurement amplifier.

By now we have designed a measurement amplifier based on a common-source stage. One problem with this stage is the relatively large input capacitance C_{GG} of approx. 0.35pF , which loads the input source. Another even more severe issue is that the bias point in this circuit is set by the dc voltage level at the input. In general, we want a setup where the bias points of the circuit are largely independent of the dc input voltages. This is why in integrated circuit design we often design **differential circuits** where the input and output signals are given by the differential voltages, and are largely independent from the common-mode voltages. This is usually an advantage.

6 Current Mirror

In this section we will look into a fundamental building block which is often used in integrated circuit design, the **current mirror** [22]. A diagram is shown in Figure 28 with a MOSFET diode converting the incoming bias current into a voltage $V_{GS} = f(I_{D1}) = f(I_{\text{bias}})$, and two output MOSFETs working as current sources, which are biased from the diode. By properly selecting all W and L the input current can be scaled, and multiple copies can be created at once. Shown in the figure are two output currents I_{out1} and I_{out2} , but any number of parallel branches can be realized (note that this is true for MOSFETs as no gate current flows; for the case of BJTs, the base current flowing into the various transistors is subtracted from I_{bias} , so usually a compensation circuit is added).

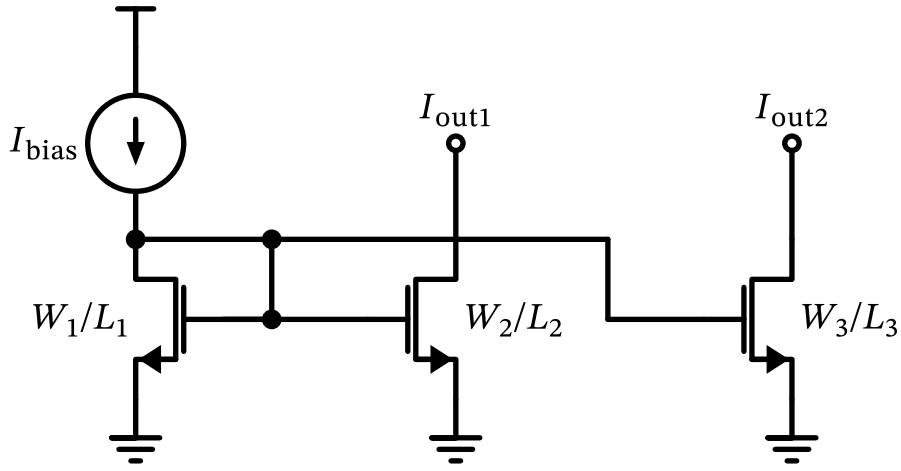


Figure 28: A current mirror with two output branches.

Neglecting the impact of g_{ds1} and g_{ds2} , the output current I_{out1} is then given by

$$I_{\text{out1}} \approx I_{\text{bias}} \frac{W_2}{L_2} \frac{L_1}{W_1}$$

and the output current I_{out2} is given by

$$I_{\text{out2}} \approx I_{\text{bias}} \frac{W_3}{L_3} \frac{L_1}{W_1}.$$

For good matching, care has to be taken that the MOSFET widths and lengths are constructed out of **unit elements** of identical size, where an appropriate number of these single units are then arranged in series or parallel configuration to arrive at the target W and L (remember MOSFET parameters n_g and m , see Important 1).

As we know from earlier investigations of the MOSFET performance in Section 3 the drain current of a MOSFET is a function of V_{GS} and V_{DS} . As long as the MOSFET stays in saturation (i.e., $V_{DS} > V_{ds,\text{sat}}$) the drain current is just a mild function of V_{DS} (essentially the effect of g_{ds} , which is the output conductance of the MOSFET). A fundamental flaw/limitation of the basic current mirror shown in Figure 28 is the mismatch of the V_{DS} of the MOSFETs. The input-side diode has $V_{GS} = V_{DS1}$, whereas the output current sources have a $V_{DS2,3}$ depending on the

connected circuitry. Improved current mirrors exist (fixing this flaw); however, when a current mirror is required with mediocre performance requirements, this structure can be used for its simplicity.

💡 Exercise: Current Mirror

Please construct a current mirror based on the MOSFET-diode which we sized in Section 4. The input current $I_{\text{bias}} = 20 \mu\text{ A}$, and we want three output currents of size $10 \mu\text{ A}$, $20 \mu\text{ A}$, and $40 \mu\text{ A}$.

Sweep the output voltage of all three current branches and see over which voltage range an acceptable current is created. For which output voltage range is the current departing from its ideal value, and why?

You see that the slope of the output current is poor, as g_{ds} is too large. We can improve this by changing the length to $L = 5 \mu\text{ m}$ (for motivation, please look at the graphs in Section 3). In addition, for a current mirror we are not interested in a high $g_{\text{m}}/I_{\text{D}}$ value, so we can use $g_{\text{m}}/I_{\text{D}} = 5$ in this case. Please size the current mirror MOSFETs accordingly (please round the W to half micron, to keep sizes a bit more practical). Compare this result to the previous one. What changed?

In case you get stuck, here are Xschem schematics for the original and the improved current mirrors.

7 Differential Pair

Like the current mirror in Section 6, the **differential pair** is a ubiquitous building block often used in integrated circuit design [23]. The fundamental structure is given in Figure 29.

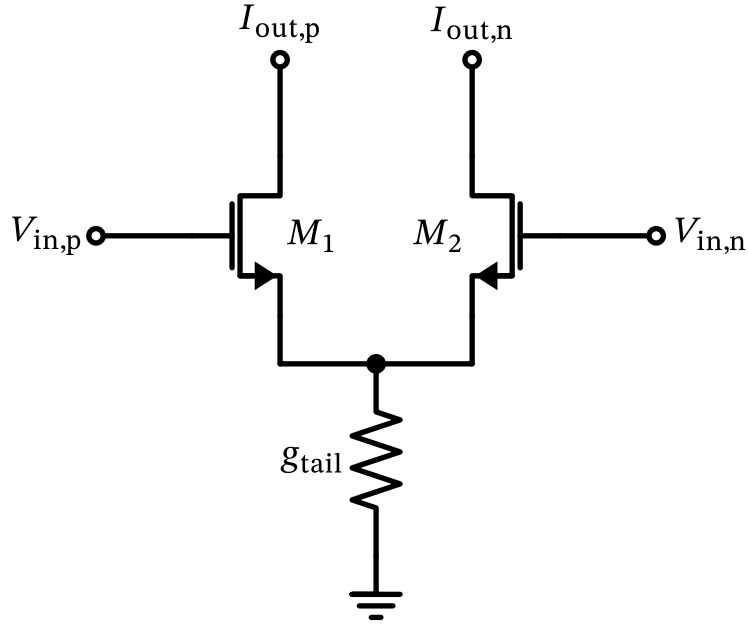


Figure 29: A differential pair.

In order to understand its operation it is instructive to separate the input condition into

1. a purely differential voltage, and
2. a common-mode voltage,

and see what the impact on the output currents is.

7.1 Differential Operation of the Diffpair

For a differential mode of operation we assume that the input common-mode voltage is constant, i.e., $(V_{in,p} + V_{in,n})/2 = V_{CM}$. The differential input voltage $V_{in} = V_{in,p} - V_{in,n}$, so that

$$V_{in,p} = V_{CM} + \frac{V_{in}}{2}$$

and

$$V_{in,n} = V_{CM} - \frac{V_{in}}{2}.$$

For a small-signal differential drive the potential at the tail point stays constant and we can treat it as a virtual ground. The output current on each side is then given by (neglecting g_{ds} and g_{mb} of M_1 and M_2)

$$I_{out,p} = g_{m1} \left(\frac{V_{in}}{2} \right)$$

and

$$I_{\text{out},n} = g_{m2} \left(-\frac{V_{\text{in}}}{2} \right).$$

Usually we assume symmetry in the differential pair, so $g_{m1} = g_{m2} = g_m$. The differential output current I_{out} is then given by

$$I_{\text{out}} = I_{\text{out},p} - I_{\text{out},n} = g_m V_{\text{in}} \quad (12)$$

We see in Equation 12 that the differential output current is simply the differential input voltage multiplied by the g_m of the individual transistor. We also note that the bottom conductance g_{tail} plays no role for the small-signal differential operation.

7.2 Common-Mode Operation of the Diffpair

Usually, the source conductance g_{tail} is realized by a current source and ideally should be $g_{\text{tail}} = 0$. If this is the case, then the output currents are not a function of the common-mode input voltage (I_{tail} is set by the tail current source), and

$$I_{\text{out},p} = I_{\text{out},n} = I_{\text{out}} = \frac{I_{\text{tail}}}{2}.$$

However, if we assume a realistic tail current source then $g_{\text{tail}} > 0$. For analysis we can simply look at a half circuit since the circuit operation is symmetric. In order to simplify the analysis a bit we remove all capacitors from the MOSFET small-signal model and set $g_{\text{ds}} = g_{\text{mb}} = 0$. We then arrive at the small-signal equivalent circuit shown in Figure 30 (note that we set $V_{\text{in},p} = V_{\text{in},n} = V_{\text{in}}$ and $I_{\text{out},p} = I_{\text{out},n} = I_{\text{out}}$ under symmetry considerations). As both transistors inject their drain current into the shared tail node, the half circuit sees an effective tail conductance of $g_{\text{tail}}/2$.

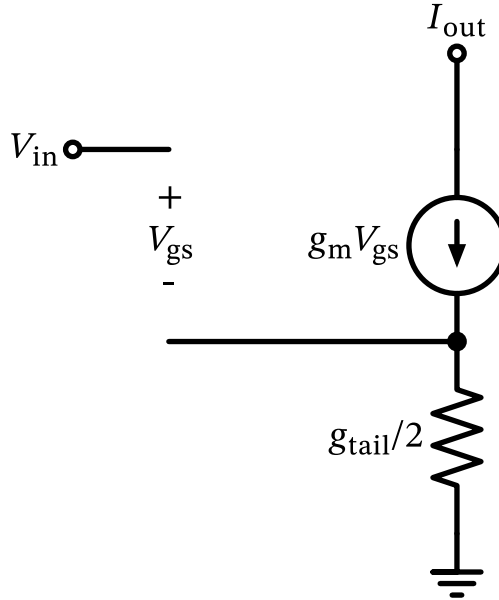


Figure 30: Small-signal model of the differential pair half-circuit in common-mode operation.

Formulating KVL for the input-side loop we get

$$V_{\text{in}} = V_{\text{gs}} + \frac{2I_{\text{d}}}{g_{\text{tail}}}.$$

With $I_{\text{out}} = I_{\text{d}} = g_{\text{m}} V_{\text{gs}}$ we arrive at

$$I_{\text{out}} = \frac{g_{\text{m}} \cdot g_{\text{tail}}}{2g_{\text{m}} + g_{\text{tail}}} V_{\text{in}} \quad (13)$$

Interpreting Equation 13 we can distinguish the following extreme cases:

1. If $g_{\text{tail}} = 0$ (ideal tail current source) then $I_{\text{out}} = 0$, the common-mode voltage variation from the input is suppressed and does not show up at the common-mode output current (which is constant due to the ideal tail current source). This is usually the case that we want to achieve.
2. If $g_{\text{tail}} \rightarrow \infty$ then $I_{\text{out}} = g_{\text{m}} V_{\text{in}}$, which means the output current is a function of the MOSFET g_{m} . If everything is perfectly matched, then the differential output current is zero, but the common-mode output current changes according to the common-mode input voltage. In special cases this can be a wanted behavior, this configuration is called a “pseudo-differential pair.”
3. For the typical case that $g_{\text{m}} \gg g_{\text{tail}}$ then $I_{\text{out}} \approx (g_{\text{tail}}/2) V_{\text{in}}$.

Note that Equation 13 is closely related to the general case of a degenerated common-source transistor stage (see Figure 31). The effective transconductance g'_{m} of a degenerated CS stage is given by

$$g'_{\text{m}} = \frac{I_{\text{out}}}{V_{\text{in}}} = \frac{1}{g_{\text{m}}^{-1} + R_{\text{degen}}}.$$

For the differential-pair half circuit in common-mode operation, the effective source degeneration is $R_{\text{degen}} = 2/g_{\text{tail}}$, yielding Equation 13.

When no degeneration resistor is used, then $g'_{\text{m}} = g_{\text{m}}$. If a degeneration of $R_{\text{degen}} \gg g_{\text{m}}^{-1}$ is used then $g'_{\text{m}} = 1/R_{\text{degen}}$. This result is worth memorizing.

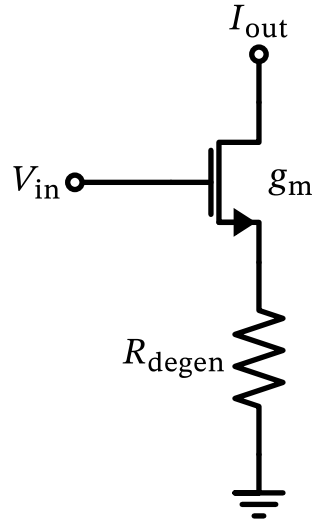


Figure 31: A MOSFET common-source amplifier with resistive degeneration.

8 A Basic 5-Transistor OTA

Armed with the insights of basic transistor operation (Section 2 and Section 3) and the working knowledge of the current mirror (Section 4 and Section 6) as well as the differential pair (Section 7), we can now start to design our first real circuit. A fundamental (simple) circuit that is often used for basic tasks is the 5-transistor operational transconductance amplifier (OTA). A circuit diagram of this 5T-OTA is shown in Figure 32.

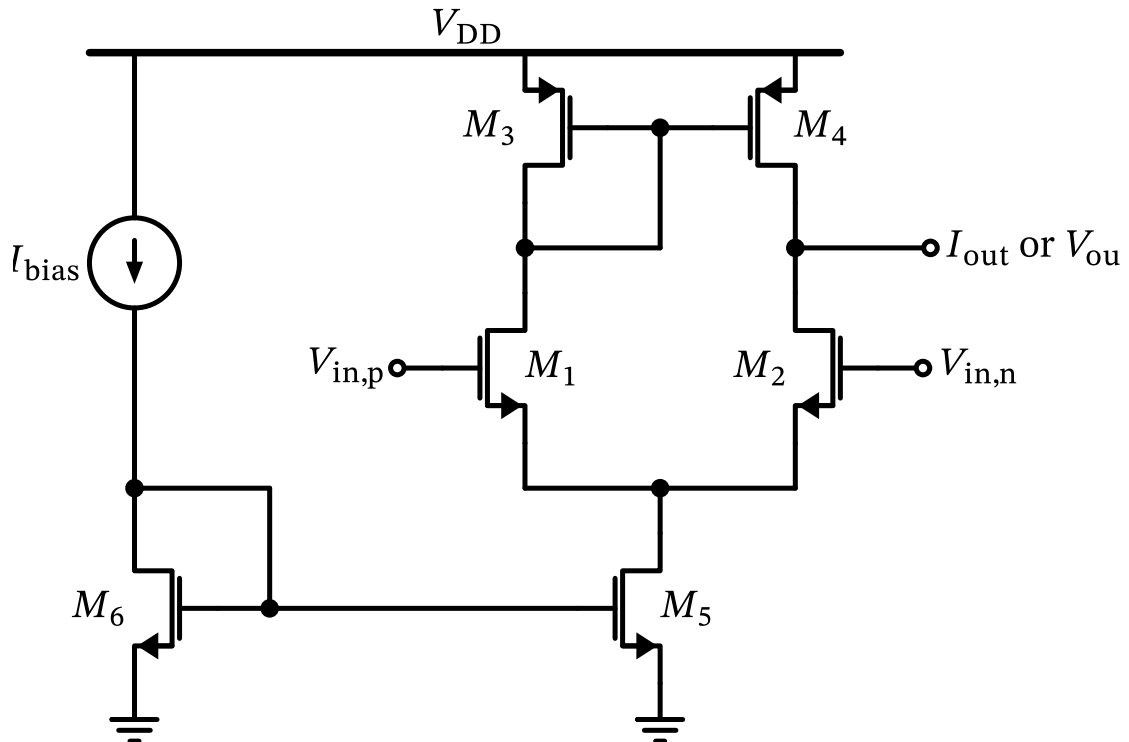


Figure 32: The 5-transistor OTA.

⚠ Refresh MOSFET Basic Circuits

While we repeat the basics of elementary MOSFET amplifier stages (like common-source stage, common-gate stage, and current mirror) in this course material, the following compendium [24] is recommended for review. It is freely available at <https://github.com/bmurmman/Book-on-MOS-stages>.

In addition, we can highly recommend these references [1], [2] for further study.

The operation is as follows: $M_{1,2}$ form a differential pair which is biased by the current source M_5 . $M_{5,6}$ form a current mirror, thus the input bias current I_{bias} sets the bias current in the OTA. The differential pair $M_{1,2}$ is loaded by the current mirror $M_{3,4}$ which mirrors the drain current of M_1 to the right side. Here, the currents from M_4 and M_2 are summed, and together with the conductance effective at the output node, a voltage builds up.

i Operational Amplifier (op-amp, OPA) vs. Operational Transconductance Amplifier (OTA)

An operational amplifier is a universal electronic building block characterized by (in the ideal case):

- infinite input impedance at the input ports ($R_{\text{in}} \rightarrow \infty$)
- zero output resistance, i.e., a voltage output ($R_{\text{out}} = 0$)
- infinite voltage gain ($A_v = V_{\text{out}}/V_{\text{in}} \rightarrow \infty$)

An operational transconductance amplifier is a building block characterized by (again in the ideal case):

- infinite input impedance at the input ports ($R_{\text{in}} \rightarrow \infty$)
- infinite output resistance, i.e., a current output ($R_{\text{out}} \rightarrow \infty$)
- infinite transconductance ($G = I_{\text{out}}/V_{\text{in}} \rightarrow \infty$)

In integrated circuits, we very often load an OPA/OTA high-ohmic, i.e., with a capacitive load. Hence, an OTA can be used to create a voltage-mode amplifier with high gain, approaching the properties of the OPA. If an OTA is used to drive a low-ohmic load, the voltage gain will be low, and we have to use this block as a transconductance amplifier. Since the output changes behavior depending on high- or low-ohmic loading, we label the output in Figure 32 accordingly.

Why then implement an OTA instead of an OPA? Usually, an OTA is a simpler structure than an OPA. As a general rule, the simplest circuit that can do a job is usually the best choice.

We note that $M_{1,2}$ and $M_{3,4}$ need to be symmetric, thus will have the same W and L dimensioning. $M_{5,6}$ we scale accordingly to set the correct bias current in the OTA.

8.1 Voltage Buffer with OTA

In order to design an OTA we need an application, and from this we need to derive the circuit specifications. We want to use this OTA to realize a voltage buffer which lightly loads an input

voltage source and can drive a large capacitive load. Such a configuration is often used to, e.g., buffer a reference voltage that is needed (and thus loaded) by another circuit. The block diagram of this configuration is shown in Figure 33.

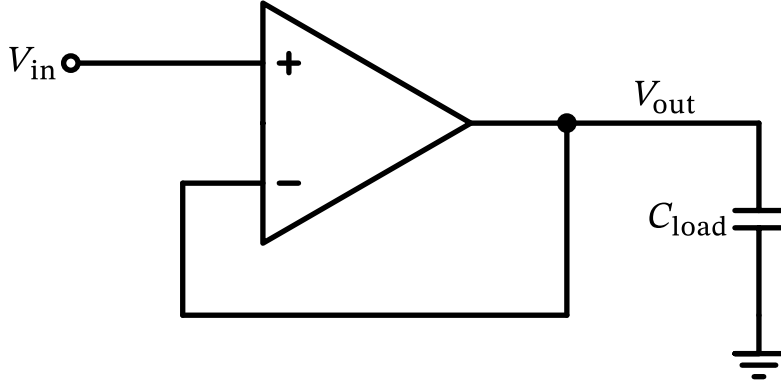


Figure 33: A voltage buffer (based on OTA) driving a capacitive load.

If the voltage gain of the OTA in Figure 33 is high, then $V_{\text{out}} \approx V_{\text{in}}$. We now want to design an OTA for this application, fitting the following specification values (see Table 2). These values are rather typical of what could be expected for such a buffer design.

Table 2: Voltage buffer specification

Specification	Value	Unit
Supply voltage	$1.45 < \underline{1.5} < 1.55$	V
Temperature range (industrial)	$-40 < \underline{27} < 125$	degC
Load capacitance C_{load}	50	fF
Input voltage range (for buffering 2/3 bandgap voltage)	$0.7 < \underline{0.8} < 0.9$	V
Signal bandwidth (3 dB)	> 10	MHz
Output voltage error	< 3	%
Total output noise (rms)	< 1	mV _{rms}
Supply current (as low as possible)	< 10	μA
Stability	stable for rated C_{load}	
Turn-on time (settled to with 1%)	< 10	μs
Externally provided bias current (nominal)	20	μA

8.2 Large-Signal Analysis of the OTA

The first step when receiving a design task is to look at the specifications and see whether they make sense. The detailed performance of the design will be the result of the circuit simulation, but before we step into sizing we need to do a few simple calculations to (a) do back-of-the-

envelope gauging if the specification makes sense, and (b) use the derived analytical equations as guide for the sizing procedure.

In terms of large-signal operation, we will now check whether the input and output voltage range, as well as the settling time can be roughly met. Since we do not know yet the resulting V_{GS} of the transistors, we use 0.6 V as an initial guess. If we run into issues with that guess, we know how to later steer the sizing procedure. The follower configuration showing the transistor-level details including estimated operating points is shown in Figure 34.

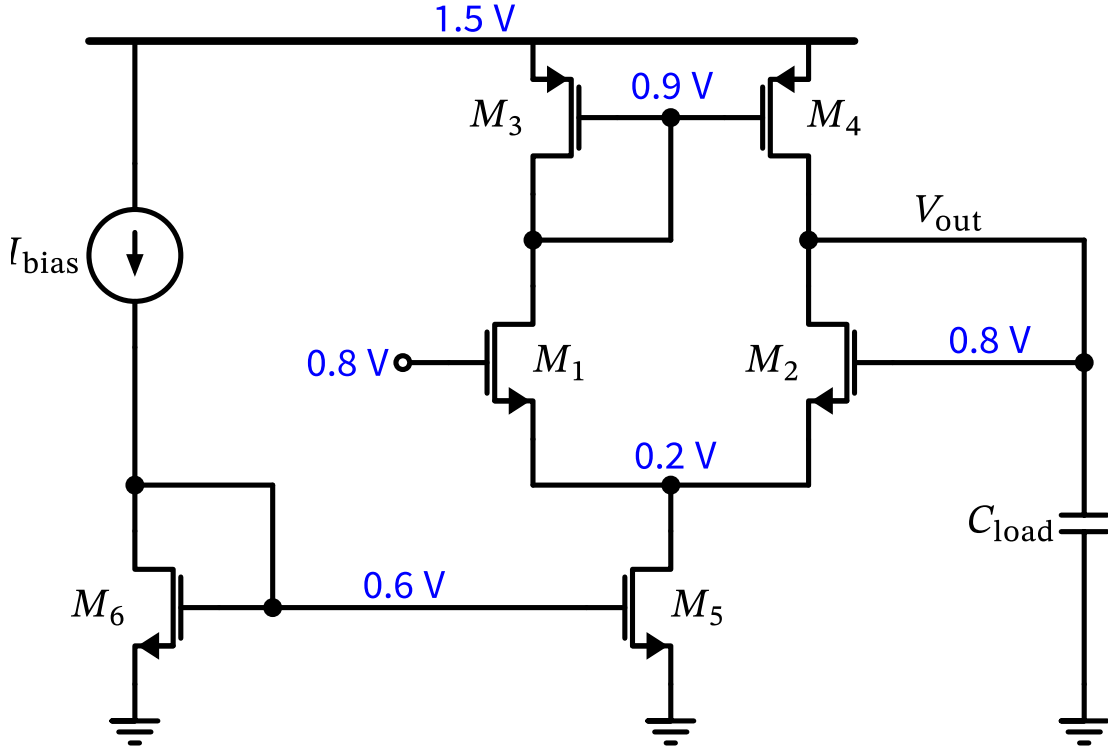


Figure 34: The 5-transistor OTA with external connections and load capacitor. Estimated dc operating points are shown in blue.

- When the input is at its maximum of 0.9 V, we see that we need to keep M_1 in saturation. We can calculate that $V_{DS1} = V_{DD} - |V_{GS3}| + V_{GS1} - V_{in} = 1.45 - 0.6 + 0.6 - 0.9 = 0.55$ V, which leaves enough margin.
- When the input is at its minimum of 0.7 V, we see that the V_{DS5} of M_5 is calculated as $V_{DS5} = V_{in} - V_{GS1} = 0.7 - 0.6 = 0.1$ V, so this leaves little margin, but we can make V_{GS1} smaller, so it should work out.
- For the output voltage, when the output voltage is on the high side, it leaves $|V_{DS4}| = V_{DD} - V_{out} = 1.45 - 0.9 = 0.55$ V, which is enough margin.

In summary, we think that we can make an NMOS-input OTA like the one in Figure 32 (and in Figure 34) work for the required supply and input and output voltages. If this would not work out, we need to look for further options, like a PMOS-input OTA or an NMOS/PMOS-input OTA.

Another large-signal specification item that we can quickly check is the settling time. Under slewing conditions, the complete bias current in the OTA is steered toward the output (try

to understand why this is the case), so when the output capacitor is fully discharged and we assume just a linear ramp due to constant-current charging of the output capacitor, the settling time is

$$T_{\text{slew}} \approx \frac{C_{\text{load}} \cdot V_{\text{out,max}}}{I_{\text{tail}}} = \frac{50 \cdot 10^{-15} \cdot 0.9}{10 \cdot 10^{-6}} = 4.5 \text{ ns} .$$

Note that we have optimistically inserted the *total* supply current budget of $10 \mu\text{ A}$ for I_{tail} here; the actual tail current will be smaller, since the bias branch M_6 also draws current. This is fine for a first sanity check, as it tells us the slewing contribution is negligible even if the real value turns out several times larger.

This leaves plenty of margin for additional small-signal settling due to the limited bandwidth, as well as for reducing the supply current.

The small-signal settling (assuming one pole at the bandwidth corner frequency) leads to an approximate settling time (1% error corresponds to $\approx 5\tau$) of

$$T_{\text{settle}} \approx \frac{5}{2\pi f_c} = \frac{5}{2\pi \cdot 10 \times 10^6} = 0.08 \mu\text{ s} .$$

This also checks out.

8.3 Small-Signal Analysis of the OTA

In order to size the OTA components we need to derive how the MOSFET parameters define the performance. The important small-signal metrics are

- dc voltage gain A_0
- gain-bandwidth product (GBW)
- output noise

The specification for GBW is directly given in Table 2, while the dc gain we have to calculate from the voltage accuracy specification. For a voltage follower in the configuration shown in Figure 33 the voltage gain is given by (see Figure 33)

$$(V_{\text{in}} - V_{\text{out}}) \cdot A_0 = V_{\text{out}} \rightarrow \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{A_0}{1 + A_0} . \quad (14)$$

So in order to reach an output voltage accuracy of at least 3% we need a dc gain of $A_0 > 30.2 \text{ dB}$. To allow for process and temperature variation we need to add a bit of extra gain as margin.

! Small-Signal vs. Large-Signal Operation

In order to get the correct dc voltage per the specification we require the large-signal gain calculated with Equation 14. However, calculating the large-signal gain of a circuit is quite involved (usually mandating the use of a large-signal nonlinear model for the used components), so we typically resort to do a simpler small-signal calculation instead, like in Section 8.3. We deliberately introduce this error, but we should not get confused about the difference between large- and small-signal operation!

8.3.1 OTA Small-Signal Transfer Function

In order to derive the governing small-signal equations for the OTA we will make a few simplifications:

- We assume that $g_{m1,2} = g_{m1} = g_{m2}$, $g_{m3,4} = g_{m3} = g_{m4}$, and $C_{gs3,4} = C_{gs3} = C_{gs4}$ for symmetry reasons (as M_1 and M_2 will have to be equally sized, as well as M_3 and M_4).
- We will set $g_{mb} = 0$ for all MOSFETs.
- We will further set $C_{gd} = 0$ for all MOSFETs except for M_4 where we expect a Miller effect on this capacitor, and we could add its effect by increasing the capacitance at the gate node of $M_{3,4}$ (for background please see Section 17.1). However, as this does not create a dominant pole in this circuit, we consider this a minor effect (see Equation 17). Thus, only $2C_{gs3,4}$ is considered at the gate node of the current mirror load.
- We assume $g_m \gg g_{ds}$, so we set $g_{ds1} = g_{ds3} = 0$ as this node is dominated by g_{m3}^{-1} .
- The drain capacitance of M_2 and M_4 , as well as the gate capacitance of M_2 , we could add to the load capacitance C_{load} (see Figure 34). Do not dismiss this as a second-order correction: with the small $C_{load} = 50$ fF specified here, the sizing procedure will show that these device parasitics contribute roughly as much again as the specified load itself, so they effectively halve the achievable bandwidth if ignored.

The resulting small-signal equivalent circuit is shown in Figure 35.

⚠ Refresh MOSFET Small-Signal Model

Please review the MOSFET small-signal equivalent model in Figure 6 at this point. For the PMOS just flip the model upside-down.

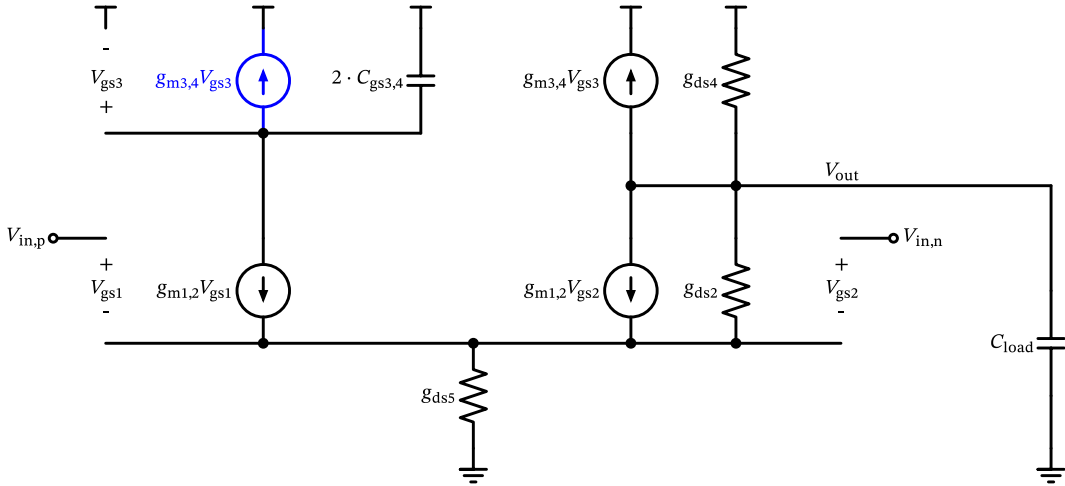


Figure 35: 5-transistor OTA open-loop small-signal model. For the closed-loop model, the input voltage $V_{in,n}$ is connected to the output voltage V_{out} . Note that the blue current source can be replaced by a conductance of $g_{m3,4}$.

We can further simplify Figure 35 by realizing that we operate the circuit purely differential and thus the tail point of M_1 and M_2 can be treated like a virtual ground, we thus short g_{ds5} . Therefore, we can move $g_{ds2} + g_{ds4}$ in parallel to C_{load} . The current source $g_{m3,4}V_{gs3}$ is

replaced with the equivalent conductance $g_{m3,4}$. All the previous steps result in the further simplified equivalent circuit shown in Figure 36.

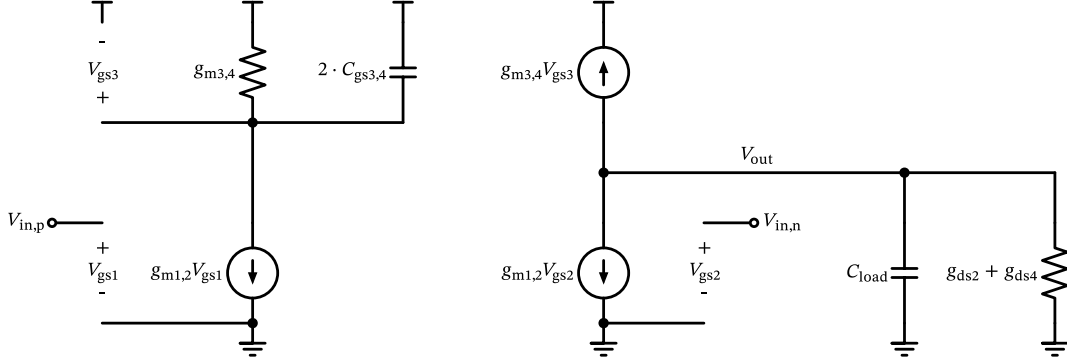


Figure 36: 5-transistor OTA small-signal model with further simplifications.

In the simplified circuit model in Figure 36, we can see that we have two poles in the circuit, one at the gate node of $M_{3,4}$ and one at the output. Realizing that $V_{gs1} = V_{in,p} = V_{in}/2$ and $V_{gs2} = V_{in,n} = -V_{in}/2$ we can formulate KCL at the output node to

$$-g_{m3,4} V_{gs3} - g_{m1,2} \left(-\frac{V_{in}}{2} \right) - V_{out} (g_{ds2} + g_{ds4} + sC_{load}) = 0. \quad (15)$$

We further realize that

$$V_{gs3} = -g_{m1,2} \frac{V_{in}}{2} \frac{1}{g_{m3,4} + 2 \cdot sC_{gs3,4}}. \quad (16)$$

By combining Equation 15 and Equation 16 and after a bit of algebraic manipulation we arrive at

$$A(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{g_{m1,2}}{2} \frac{2 \cdot g_{m3,4} + 2 \cdot sC_{gs3,4}}{(g_{m3,4} + 2 \cdot sC_{gs3,4})(g_{ds2} + g_{ds4} + sC_{load})}. \quad (17)$$

When we inspect Equation 17 we can see that for low frequencies the (open-loop) gain is

$$A(s \rightarrow 0) = A_0 = \frac{g_{m1,2}}{g_{ds2} + g_{ds4}} \quad (18)$$

which is plausible, and confirms the requirement of a high impedance at the output node.

Above the dominant pole, but still well below the current-mirror doublet, the numerator of Equation 17 is still dominated by the term $2g_{m3,4}$, and the gain becomes

$$A(s) \approx \frac{g_{m1,2}}{2} \frac{2g_{m3,4}}{g_{m3,4} \cdot sC_{load}} = \frac{g_{m1,2}}{sC_{load}} \quad (19)$$

which is essentially the behavior of an integrator. This is the frequency range in which the amplifier is actually operated, so we use Equation 19 to calculate the frequency where the gain drops to $|A(s_{ug})| = 1 = g_{m1,2}/|j\omega_{ug}C_{load}|$:

$$f_{\text{ug}} = \frac{g_{\text{m1},2}}{2\pi C_{\text{load}}} \quad (20)$$

Note that this is exactly the dc gain Equation 18 multiplied by the dominant-pole frequency Equation 22, i.e. the gain-bandwidth product, as it has to be for a system that behaves like a single-pole system up to f_{ug} . The output conductances cancel, so the achievable GBW is set by $g_{\text{m1},2}$ and C_{load} alone.

i Watch the Asymptote You Use

It is tempting to obtain f_{ug} from the asymptote of Equation 17 for $s \rightarrow \infty$, where both numerator and denominator are dominated by their $sC_{\text{gs3},4}$ terms:

$$A(s \rightarrow \infty) = \frac{g_{\text{m1},2}}{2 \cdot sC_{\text{load}}} \quad (21)$$

This differs from Equation 19 by a factor of two, and would predict a unity-gain frequency only half as large. The reason for the discrepancy is physical: Equation 21 describes the behavior *above* the doublet, where $C_{\text{gs3},4}$ shorts out the current mirror so that the signal path through $M_{3,4}$ is lost and only the direct path through M_2 remains — hence half the transconductance. In a sensible design the doublet sits far above f_{ug} , so Equation 19 is the asymptote to use.

Looking at Equation 17, we see that we have a dominant pole at s_{p} and a pole-zero doublet with $s_{\text{pd}}/s_{\text{zd}}$:

$$s_{\text{p}} = -\frac{g_{\text{ds2}} + g_{\text{ds4}}}{C_{\text{load}}} \quad (22)$$

$$s_{\text{pd}} = -\frac{g_{\text{m3},4}}{2 \cdot C_{\text{gs3},4}} \quad (23)$$

$$s_{\text{zd}} = -\frac{g_{\text{m3},4}}{C_{\text{gs3},4}} \quad (24)$$

i Why a Pole-Zero Doublet?

Looking at Equation 23 and Equation 24 we see that this pair is intimately linked by the same parameters and can only move together. Hence we call it a “doublet”. The effects of pole-zero doublets on the frequency response and settling time of OTAs can be found in [25]. This paper shows that doublets may cause severe degradation of settling time while only causing minor changes in the frequency response of the amplifier.

8.3.2 OTA Noise

For the noise analysis we ignore the pole-zero doublet due to $C_{\text{gs3},4}$ (we assume minor impact due to this, hence we set $C_{\text{gs3},4} = 0$) and just consider the dominant pole given by Equation 22 due to the load capacitance. For the noise analysis at the output we set the positive input signal

to ground and connect the output to the negative input, and thus starting from Figure 36 we arrive at the adapted small-signal circuit shown in Figure 37.

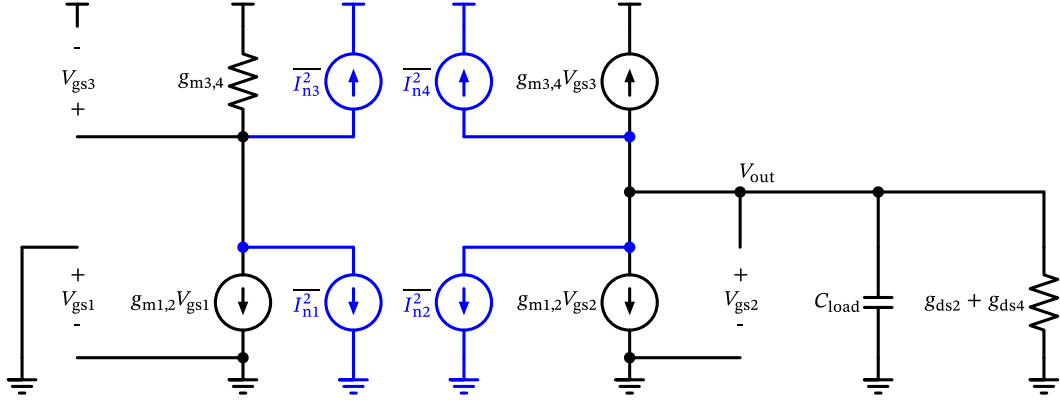


Figure 37: 5-transistor OTA small-signal model for noise calculation (added noise sources shown in blue).

For symmetry reasons we can set $\overline{I_{n1,2}^2} = \overline{I_{n1}^2} = \overline{I_{n2}^2}$ and $\overline{I_{n3,4}^2} = \overline{I_{n3}^2} = \overline{I_{n4}^2}$. We see that we can replace the current source $g_{m1,2}V_{gs2}$ with its equivalent conductance of $g_{m1,2}$, and this conductance is in parallel to $g_{ds2} + g_{ds4}$, hence $g_{m1,2} + g_{ds2} + g_{ds4} \approx g_{m1,2}$. The resulting simplified small-signal noise equivalent circuit is shown in Figure 38.

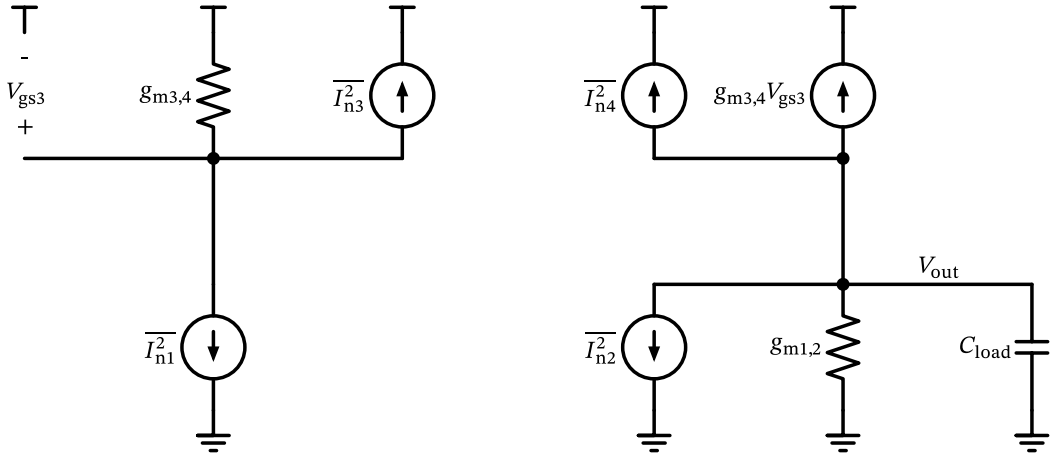


Figure 38: 5-transistor OTA simplified small-signal model for noise calculation.

We see that

$$\overline{V_{gs3}^2} = \frac{1}{g_{m3,4}^2} (\overline{I_{n1}^2} + \overline{I_{n3}^2}).$$

! Noise Addition

Remember that **uncorrelated** noise quantities need to be power-summed (i.e., $I^2 = I_1^2 + I_2^2$)!

We can then sum the total output noise current $\overline{I_n}$ as

$$\overline{I_n^2} = \overline{I_{n2}^2} + \overline{I_{n4}^2} + g_{m3,4}^2 \frac{1}{g_{m3,4}^2} (\overline{I_{n1}^2} + \overline{I_{n3}^2}) = 2(\overline{I_{n1,2}^2} + \overline{I_{n3,4}^2}).$$

The output noise voltage is then (using Equation 1)

$$\begin{aligned} \overline{V_{n,out}^2}(f) &= \frac{\overline{I_n^2}}{|g_{m1,2} + sC_{load}|^2} = \frac{\overline{I_n^2}}{g_{m1,2}^2 + (2\pi f C_{load})^2} \\ &= \frac{8kT(\gamma_{1,2}g_{m1,2} + \gamma_{3,4}g_{m3,4})}{g_{m1,2}^2 + (2\pi f C_{load})^2}. \end{aligned}$$

We can use the identity Equation 9 to calculate the rms output noise to

$$V_{n,out,rms}^2 = \int_0^\infty \overline{V_{n,out}^2}(f) \cdot df = \frac{kT}{C_{load}} \left(2\gamma_{1,2} + 2\gamma_{3,4} \frac{g_{m3,4}}{g_{m1,2}} \right). \quad (25)$$

Inspecting Equation 25 we can see that the integrated output noise is the kT/C noise of the output load capacitor, enhanced by the γ_{12} of the input differential pair, plus a (smaller) contribution of the current mirror load $M_{3,4}$. Intuitively, this result makes sense. We learn that to reduce the output noise we should set $g_{m3,4} < g_{m1,2}$.

💡 Exercise: Derivation of 5T-OTA Performance

Please take your time and carefully go through the explanations and derivations for the 5-transistor-OTA in Section 8.2 and Section 8.3. Try to do the calculations yourself; if you get stuck, review the previous chapters. There are additional useful derivations in Section 18.

8.4 5T-OTA Sizing

Armed with the governing equations derived in Section 8.3, we can now size the MOSFETs in the OTA. We remember that we have to size $M_{1,2}$ and $M_{3,4}$ equally.

First, we need to select a proper g_m/I_D for the MOSFET. Remembering Section 3, we see that for the input differential pair we should go for a large g_m , thus we select a $g_m/I_D = 10$. As g_{ds} of M_2 could limit the dc gain (Equation 18), we go with a rather long $L = 5 \mu\text{m}$. For current sources, a small g_m/I_D is a good idea, so we start with $g_m/I_D = 5$ (because we cannot go too low because of $V_{ds,sat}$) and also an $L = 5 \mu\text{m}$. The g_m/I_D is also useful to estimate the required drain-source voltage to keep a MOSFET in saturation (i.e., keep the g_{ds} small) with this approximate relationship:

$$V_{ds,sat} = \frac{2}{g_m/I_D} \quad (26)$$

💡 Exercise: 5T-OTA Sizing

Please size the 5T-OTA according to the previous g_m/I_D and L suggestions. Please calculate the W of M_{1-6} and the total supply current. Please check whether gain error, total output noise, and turn-on settling are met with the calculated devices sizes and bias currents.

The sizing procedure and its calculation are best performed in a Jupyter notebook, as we can easily look up the exact data from the pre-computed tables:

💡 Solution: 5T-OTA Sizing

Sizing for Basic 5T-OTA

Copyright 2024-2025 Harald Pretl

Licensed under the Apache License, Version 2.0 (the “License”); you may not use this file except in compliance with the License. You may obtain a copy of the License at <http://www.apache.org/licenses/LICENSE-2.0>

```
# read table data
from pygmid import Lookup as lk
import numpy as np
lv_nmos = lk('sg13_lv_nmos.mat')
lv_pmos = lk('sg13_lv_pmos.mat')
# list of parameters: VGS, VDS, VSB, L, W, NFING, ID, VT, GM, GMB, GDS,
CGG, CGB, CGD, CGS, CDD, CSS, STH, SFL
# if not specified, minimum L, VDS=max(vgs)/2=0.9 and VSB=0 are used
```

```
# define the given parameters as taken from the specification table or
initial guesses
c_load = 50e-15
gm_id_m12 = 10
gm_id_m34 = 5
gm_id_m56 = 5
l_12 = 5
l_34 = 5
l_56 = 5
f_bw = 10e6 # -3dB bandwidth of the voltage buffer
i_total_limit = 10e-6
i_bias_in = 20e-6
output_voltage = 1.3
vin_min = 0.7
vin_max = 0.9
vdd_min = 1.45
vdd_max = 1.55
```

```
# we get the required gm of M1/2 from the -3dB bandwidth requirement of
the voltage buffer specification
# note that the -3dB bandwidth of the voltage buffer with gain Av=1 is
equal to the unity gain bandwidth
# of the ota, hence we set them equal here
# the unity-gain frequency of the 5T-OTA is f Ug = gm12 / (2*pi*C_load)
# on top of the bare specification we apply a design margin of:
#   3x for PVT variation plus the additional MOSFET parasitic loading
#   2x of reserve on dc gain and settling (the power budget allows for it)
bw_margin = 3 * 2
```

[illegible]

8.5 5T-OTA Simulation

With the initial sizing of the MOSFETs of the 5T-OTA done, we can design the 5T-OTA circuit and set up a simulation testbench to check the performance parameters. Since this is the first time we draw a more complex schematic, and use a hierarchical design, we should note that drawing a schematic is an art, and there exists a set of rules and recommendations how to name pins, how to use annotations, and so on. Please read Section 22 before you start into your design work.

Exercise: 5T-OTA Design and Testbench

Please design the circuit of the 5T-OTA. Put the OTA circuit in a separate schematic, create a symbol for it, and use this symbol in a testbench you create in Xschem for this 5T-OTA used as a voltage buffer as shown in Figure 33. Use typical conditions for the simulation and check how well the specification in Table 2 is met and how well the derivations in Section 8.2 and Section 8.3 fit to the simulation results.

If you get stuck, you can find the testbench and 5T-OTA schematic here (for the small-signal analysis) and here (for the large-signal settling simulation). For interested students, the loop gain analysis with Middlebrook's and Tian's method of the 5T-OTA can be found here. A comprehensive technical white paper by Texas Instruments about operational amplifier stability theory and compensation methods can be found in [26].

8.6 Component Mismatch

8.6.1 MOSFET Mismatch

So far, we have assumed that implemented MOSFETs show no difference from device to device, which means that two transistors behave completely identical, and the resulting differential circuits are fully symmetric. However, due to manufacturing tolerances, this is not the case in reality. MOSFETs will show **mismatch** due to tiny random fluctuations in manufacturing, and we have to account for this. The mismatch parameters for various components are summarized in Table 4.

For a typical MOSFET, we usually consider two main mismatch effects [27]:

- A variation of the threshold voltage (mainly due to variations in doping levels).
- A variation of the critical dimensions of the MOSFET (W and L as well as vertical dimensions).

Both effects influence the drain current of the MOSFET, and they are indirectly proportional to the size of the MOSFET. So, if we want to reduce the mismatch, we have to increase the size of the MOSFET by increasing its gate area $W \cdot L$.

If we formulate the drain current mismatch standard deviation $\sigma\{\Delta I_D/I_D\}$ of two nominally identical MOSFET we get

$$\sigma\left\{\frac{\Delta I_D}{I_D}\right\} = \frac{A_{\text{mosfet}}}{\sqrt{WL}} \quad (27)$$

with A_{mosfet} being a mismatch parameter for a given CMOS technology and $\sigma\{\cdot\}$ being the standard deviation of the parameter in parentheses.

i MOSFET Mismatch

Usually, the mismatch in MOSFETs is characterized via two mismatch parameters [27]:

- The threshold voltage mismatch standard deviation

$$\sigma\{\Delta V_{th}\} = \frac{A_{vth}}{\sqrt{WL}} \quad (28)$$

- and standard deviation of the size mismatch

$$\sigma\left\{\frac{\Delta(W/L)}{(W/L)}\right\} = \frac{A_k}{\sqrt{WL}}. \quad (29)$$

The resulting standard deviation of the input offset voltage V_{offs} of a differential pair with small g_m/I_D is then given by [2]

$$\sigma\{V_{offs}\} = \sqrt{\left(\frac{V_{GS} - V_{th}}{2}\right)^2 \cdot \sigma^2\left\{\frac{\Delta(W/L)}{(W/L)}\right\} + \sigma^2\{\Delta V_{th}\}}. \quad (30)$$

The mismatch in the drain current of two current-mirror transistors, characterized as the standard deviation and for small g_m/I_D , is given by [2]

$$\sigma^2\left\{\frac{\Delta I_D}{I_D}\right\} = \sigma^2\left\{\frac{\Delta(W/L)}{(W/L)}\right\} + 4 \cdot \sigma^2\left\{\frac{\Delta V_{th}}{V_{GS} - V_{th}}\right\}. \quad (31)$$

To minimize the input offset voltage in a differential pair we should strive to minimize the overdrive voltage $V_{GS} - V_{th}$ (i.e., to maximize g_m/I_D , see Equation 30) and to minimize the mismatch in current mirrors we should target a large overdrive voltage (i.e., to minimize g_m/I_D , see Equation 31). In both cases the MOSFET area $W \cdot L$ needs to be large enough (see Equation 28 and Equation 29).

How can we now cope with mismatch in design and simulation? We can account for the transistor mismatch according to Equation 28 and Equation 29 in circuit analysis and quantify its effect. We can then take this into account when performing the circuit sizing procedure.

We can also simulate the effects of MOSFET mismatch on circuit performance by doing a **Monte Carlo** simulation. Here, a random realization of the variations of all circuit components (where mismatch is modelled) is taken and the circuit is simulated. Then, another random realization is simulated, and so on. In summary, we run the same simulation for different realizations N times and evaluate the resulting variations of the circuit parameters. If N is large enough, then the distributions should approach a Gaussian distribution, and we can then estimate the variances of the circuit parameters. Using statistical analysis we can then assess the **yield** of a circuit, i.e., how many circuit realizations will meet the specification.

i Number of Monte Carlo Simulation Runs

The number of Monte Carlo simulation runs N has to be large enough to approach Gaussian distributions to allow estimation of the variances. However, this comes at the cost of a large simulation time, so a balance has to be found. Often, $N = 250$ is a good compromise between simulation time and well-behaved parameter distributions.

As you can see in the previous discussion, running Monte Carlo simulations is a tedious process due to the large number of involved simulations and the required data processing of the heaps of simulation data. Luckily, CACE supports this type of simulation, and we will use it in Section 8.7.

8.6.2 Resistor Mismatch

Similar to the MOSFET mismatch discussed in Section 8.6.1, resistors will also show mismatch. Equivalently to Equation 27 the standard deviation of the resistor mismatch $\sigma\{\Delta R/R\}$ can be characterized by

$$\sigma\left\{\frac{\Delta R}{R}\right\} = \frac{A_{\text{res}}}{\sqrt{WL}} \quad (32)$$

with A_{res} being a mismatch parameter for a given CMOS technology.

With Equation 32 we now have two criteria for how to select the width W of a specific resistor (the length L is then derived from the required resistance value with $R = R_s \cdot L/W$):

1. The current handling capability (the larger the W , the more dc current a resistor can carry), and
2. the resistor mismatch (the larger the W , the larger the WL for a given L/W).

If a resistor's dimensions are not limited by the two criteria above then we usually choose the minimum width that is allowed for a given resistor in a specific technology (for SG13G2 it is $W_{\text{min}} = 0.5 \mu\text{m}$) to save area and to minimize the parasitic capacitance of the resistor to substrate.

8.6.3 Capacitor Mismatch

Similar to the resistor matching discussed in Section 8.6.2, capacitors will also show mismatch. Equivalently to Equation 27 the standard deviation of the capacitor mismatch $\sigma\{\Delta C/C\}$ can be characterized by

$$\sigma\left\{\frac{\Delta C}{C}\right\} = \frac{A_{\text{cap}}}{\sqrt{WL}} \quad (33)$$

8.7 5T-OTA Simulation versus PVT and MC

As you have seen in Section 8.5 running simulations by hand is tedious. When we want to check the overall performance, we have to run many simulations over various conditions:

1. The supply voltage of the circuit has tolerances, and thus we need to check the performance against this variation.
2. The temperature at which the circuit is operated is likely changing. Also the performance against this has to be verified.

3. When manufacturing the wafers random variations in various process parameters lead to changed parameters of the integrated circuit components. In order to check for this effect, wafer foundries provide model files which shall cover these manufacturing excursions. Simplified, this leads to a slower or faster MOSFET, and usually NMOS and PMOS are not correlated, so we have the process corners **SS**, **SF**, **TT**, **FS**, and **FF**. So far, we have only used the **TT** models in our simulations.

The variations listed in the previous list are abbreviated as **PVT** (process, voltage, temperature) variations. In order to finalize a circuit all combinations of these (plus the variations in operating conditions like input voltage) have to be simulated. As you can imagine, this leads to a huge number of simulations and simulation results that have to be evaluated for pass/fail.

There are two options how to tackle this efficiently:

1. As an experienced designer you have a very solid understanding of the circuit, plus based on the analytic equations you can identify which combination of operating conditions will lead to a worst case performance. Thus, you can drastically reduce the number of corners to simulate, and you run them by hand.
2. You are using a framework which highly automates this task of running a plethora of different simulations and evaluating the outcome. These frameworks are called simulation runners.

Luckily, there are open-source versions of simulation runners available, and we will use CACE in this lecture. CACE is written in Python and allows one to set up a datasheet in YAML that defines the simulation problem and the performance parameters to evaluate against specified limits. The resulting simulations are then run in parallel and the simulation data is evaluated and summarized in various forms.

There is a CACE setup available for our 5T-OTA. The datasheet describes the operating conditions and the simulations tasks. For each simulation a testbench template is needed, this one is used for ac simulations, this one is used for noise simulation, and this one is used for transient simulation.

⚠ Running CACE Simulation

The CACE simulation run can be started with

```
cace cace/voltage-buffer-ota.yaml
```

The simulation results are then placed into the `cace/_docs` folder. If in addition to the default Markdown report an HTML output is needed for easier review then using Pandoc it can be easily converted and viewed with

```
cace/cace_view.sh cace/_docs/ota-5t_schematic.md
```

After a successful run, a documentation is automatically generated. The result of a full run of this OTA design is presented here:

Note 2: CACE Summary for 5T-OTA


CACE Summary for ota-5t

netlist source: schematic

Parameter	Tool	Result	Min Limit	Min Value	Typ Ta	Typ Value	Max Limit	Max Value	Status
Output voltage ratio	ngspice	gain	0.97	0.987	any	1.000	1.03	1.007	Pass ✓
Bandwidth	ngspice	bw	15550	400.000	26012	100.000	34052	200.000	Pass ✓
Output voltage ratio (MC)	ngspice	gain_mc	any	0.998	any	0.999	any	1.001	Pass ✓
Bandwidth (MC)	ngspice	bw_mc	24012	600.000	26012	900.000	28104	300.000	Pass ✓
Output noise	ngspice	noise	any	0.308	any	0.371	1	0.454	Pass ✓
Settling time	ngspice	tsettle	any	0.137	any	0.144	10	0.156	Pass ✓

Plots

gain_vs_temp

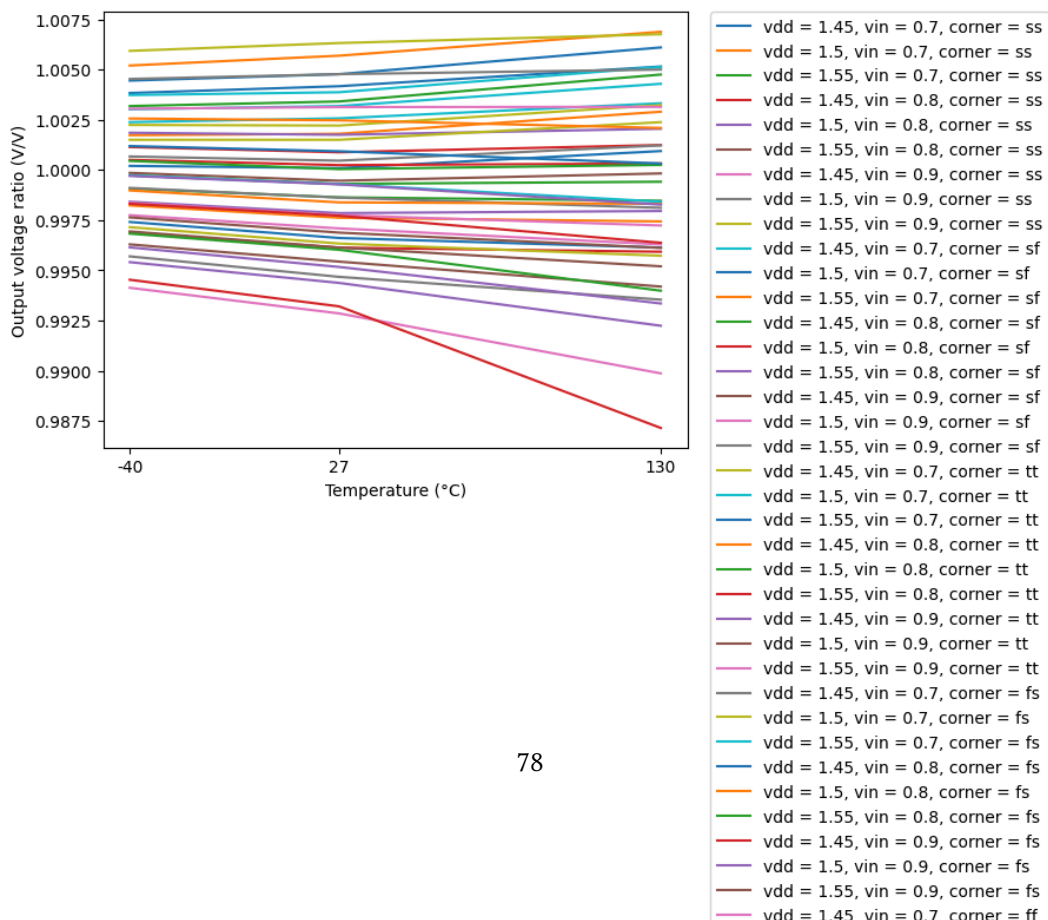

8.7.1 PVT Simulation Analysis

Looking at the CACE report in Note 2, we see that (luckily) the specification is met across all **PVT corners**. This is great news! We now have a design that we carefully simulated across PVT and other corners and that is ready for layout. Once we have the layout ready, we can extract the wiring parasitics (R and C) as well as other layout-dependent effects like well proximity. Using this augmented netlist, we can then again use CACE to check performance across conditions and parameter variations, and if we still pass all specification points, then our design is finished.

8.7.2 Monte Carlo Simulation Analysis

The **Monte Carlo** run in the same CACE report in Note 2 tells a different story: here the output voltage specification is not met, due to MOSFET mismatch! Note that this is not a contradiction to the PVT result above — PVT corners shift all devices together, whereas mismatch makes nominally identical devices differ, and it is exactly this asymmetry that the voltage buffer is sensitive to. We have not considered transistor mismatch in the circuit sizing procedure, and as a result the selected MOSFET dimensions prove to be too small. We should now go back and change the transistor sizing (increasing L significantly while keeping the g_m/I_D values). Likely we will find that some performance parameters are now deteriorating due to the increased MOSFET dimensions, and we need to iterate until all performance metrics are met in the presence of transistor mismatch.

It is not unusual that the power consumption now increases, as we have to increase the size of the MOSFETs for matching, and these larger MOSFETs increase the parasitic capacitances which in turn lead to larger power consumption to keep the required bandwidth by increasing the g_m .

Exercise: Re-Sizing of 5T-OTA for Mismatch

Go back to Section 8.4 and repeat the sizing procedure of the 5T-OTA by increasing the L of the MOSFETs significantly. Focus first on the differential pair as it will likely have the biggest impact (see Equation 30). Then, tune the size of the output current mirror if necessary (see Equation 31).

Once you are happy with the sizing result, repeat the PVT simulations in CACE to confirm the performance of the voltage buffer including mismatch.

8.8 OTA Variants

Following, we are going to discuss two popular variants of the simple 5T-OTA. The first version provides an almost rail-to-rail single-ended output and can thus be used for a variety of applications requiring this range. The arrangement is shown in Figure 57. It is a single-stage amplifier, as the only high-impedance point is at the output where significant voltage-gain is produced. The current mirrors can be used to scale up the current generated in the input differential pair to some extent in the output stage (or can be used to lower the current compared to the bias current in the diffpair); i.e., the bias currents of the input stage and the output stage can be set independently.

Being a single-stage amplifier stability is usually not an issue, as only the output node is high-ohmic; all other nodes feature a MOSFET diode so the node impedance is $\approx g_m^{-1}$ and thus the according poles are located at high frequencies.

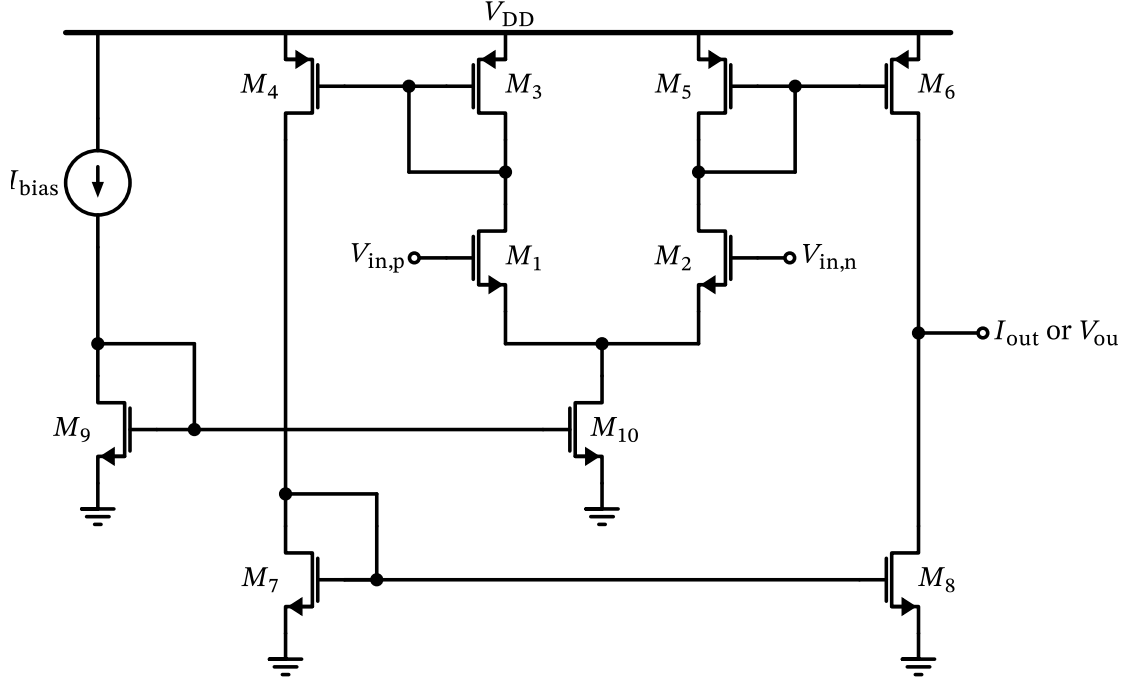


Figure 57: Single-ended OTA with rail-to-rail output stage.

Another popular version is shown in Figure 58. Here, we have a two-stage amplifier able to provide higher voltage gain. The first stage (the diffpair loaded by a current mirror) is followed by a single-stage common-source amplifier with current-source load. Being a two-stage amplifier with two high-ohmic nodes, stability is a concern, so usually we need some form of compensation. Figure 58 shows a very simplistic Miller-compensation (see Section 13.1) using C_M . Often, we would want to implement a more advanced scheme. Some examples can be found in [28]. An interesting technique is the indirect compensation with cascoded input differential pairs (see Figure 76) for higher power supply rejection. An advantage of this two-stage amplifier (compared with the simple 5T-OTA) is that both output nodes of the input stage are dc-balanced: each of them sits one V_{GS} below V_{DD} — on the left set by the diode-connected V_{GS3} , on the right set by the gate of the second-stage device M_5 , i.e. by V_{GS5} . In the plain 5T-OTA the right-hand node is instead the output node, whose dc level is imposed by the external feedback, so the two sides of the differential pair are generally *not* balanced.

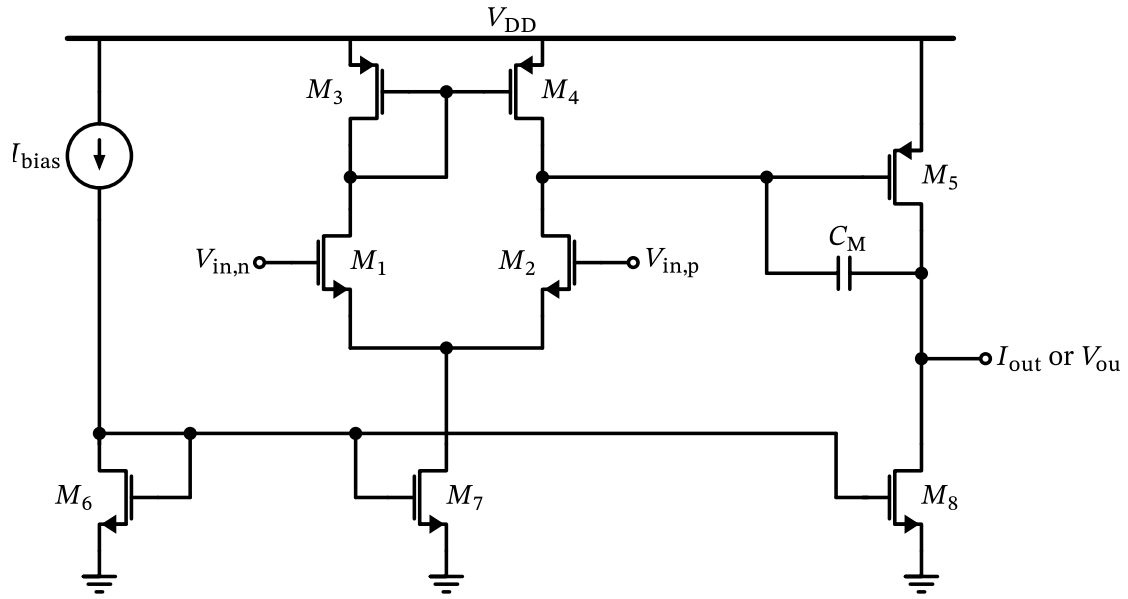


Figure 58: Single-ended two-stage OTA with rail-to-rail output.

Note that the circuit of Figure 58 can be easily modified into a low-dropout voltage regulator (LDO). This simple yet often effective circuit is shown in Figure 59. The pass transistor M_{pass} has to be sized according to the load current and the dropout voltage.

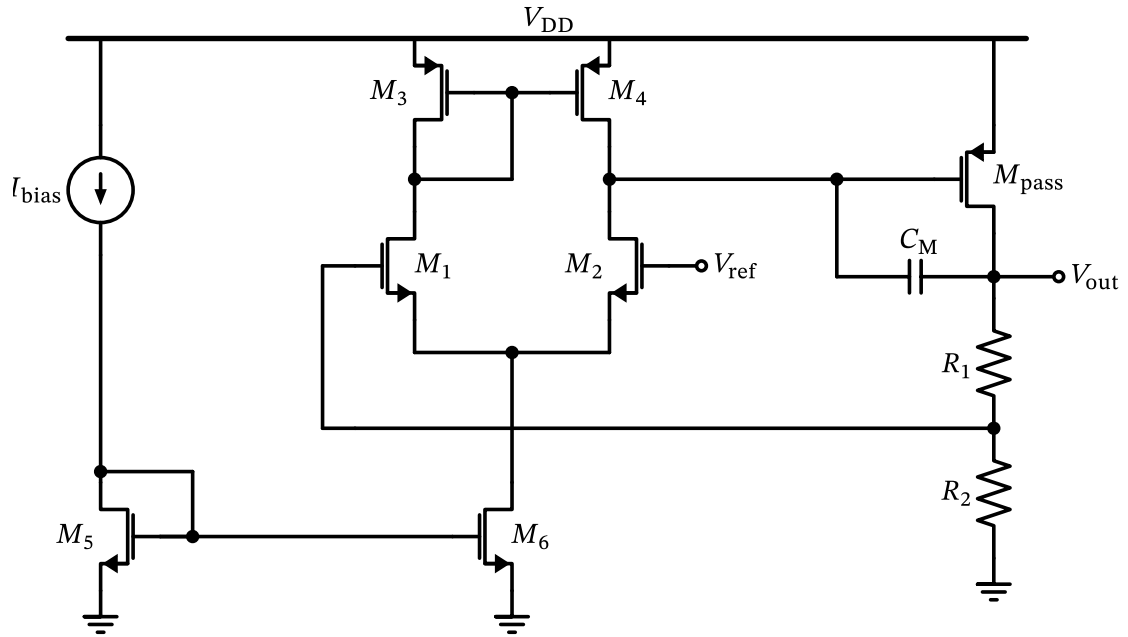


Figure 59: A basic low-dropout voltage regulator (LDO) with Miller compensation.

The reference voltage V_{ref} is scaled by R_1 and R_2 so that the output voltage V_{out} is given by

$$V_{\text{out}} \approx V_{\text{ref}} \left(1 + \frac{R_1}{R_2} \right)$$

if the gain of the OTA is sufficiently high. The quiescent current through $R_{1,2}$ establishes a minimum load current for the LDO, which is often good for stability. More information on LDOs can be found in [29].

9 Cascode Stage

As we have seen in Section 8, the performance of the OTA is generally quite acceptable (see Table 2), but we might want to aim for better output voltage accuracy. As our analysis has shown the output voltage tolerance is limited by the open-loop dc gain A_0 of the OTA (see Equation 14), which in turn is limited by the output conductance of M_2 and M_4 in Figure 32, which is also confirmed by the analytical result in Equation 18.

During the sizing procedure, we have seen that the achievable g_m/g_{ds} ratio of a single MOSFET is limited, even if we increase L . We are thus searching for a better option, and here (local) feedback in form of a **cascode** comes to help.

For analysis of a cascode, we use the following single-transistor stage shown in Figure 60.

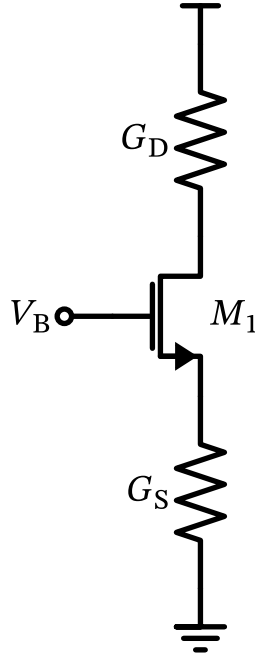


Figure 60: A MOSFET cascode circuit.

In order to derive the operation of the cascode analytically, we draw the small-signal equivalent circuit in Figure 61. We assume that V_B is a low-ohmic bias voltage, thus we replace it with ac ground. We further set $g_{mb} = 0$ (and ignore a couple of capacitances for now).

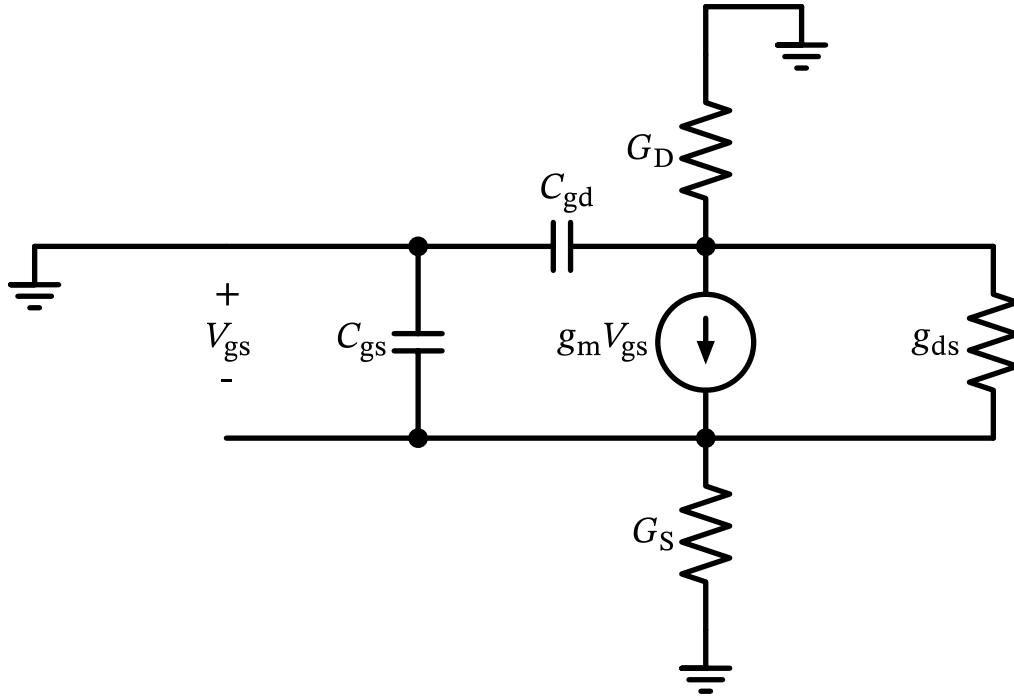


Figure 61: The MOSFET cascode small-signal model.

Since the gate is assumed at a fixed potential, we can put C_{gs} in parallel with G_S as $G_S^* = G_S + sC_{gs}$, and we can put C_{gd} in parallel with G_D as $G_D^* = G_D + sC_{gd}$. As a result, we will disregard these capacitors for now, and just consider G_S and G_D , which leads to the simplified small-signal circuit shown in Figure 62.

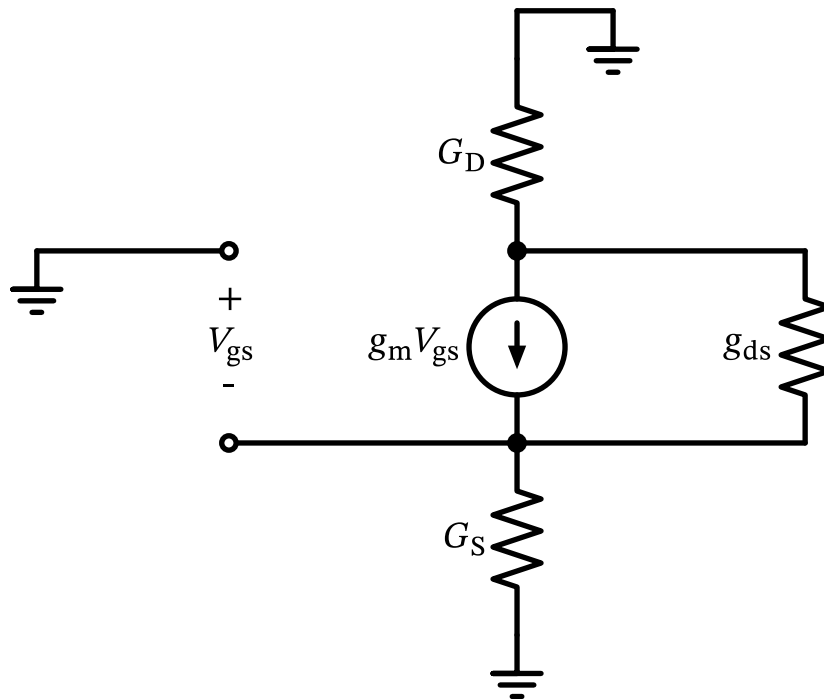


Figure 62: The simplified MOSFET cascode small-signal model.

9.1 Cascode Output Impedance

As a first step, we want to calculate the output impedance at the drain of the MOSFET (i.e., looking into the drain). For this, we replace G_D with a current source. The resulting small-signal equivalent circuit is shown in Figure 63.

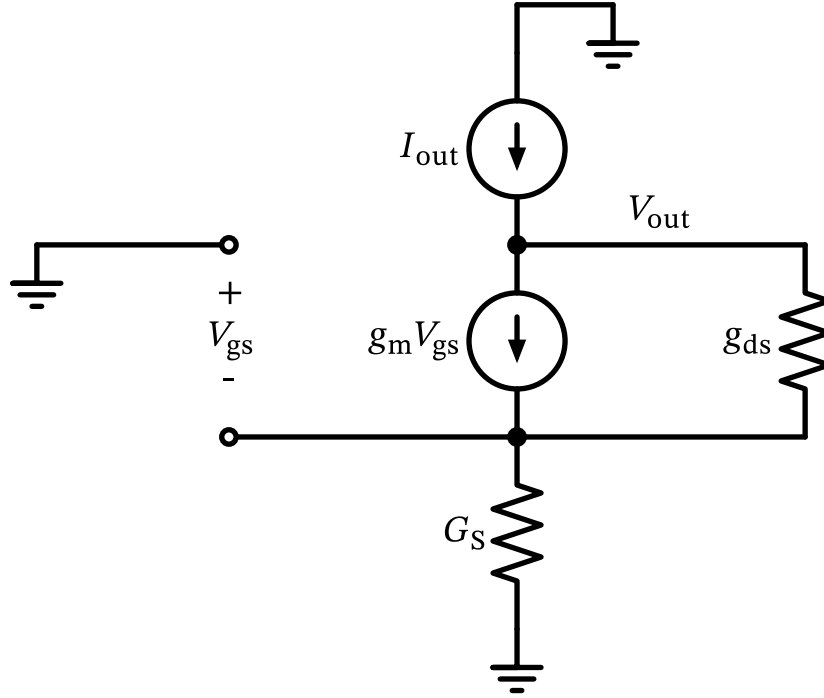


Figure 63: The simplified MOSFET cascode small-signal model for calculation of the output impedance.

We realize that I_{out} flows through G_S (as there is no other way to go) and drops V_{gs} (note the sign):

$$V_{\text{gs}} = -\frac{I_{\text{out}}}{G_S}$$

Further, $V_{\text{out}} = -V_{\text{gs}} + V_{\text{ds}}$. Calculating KCL at the output node results in

$$I_{\text{out}} - g_m V_{\text{gs}} - g_{\text{ds}} V_{\text{ds}} = 0.$$

Using the previously found identities, and after a bit of algebraic manipulations we arrive at

$$g_{\text{out}} = \frac{I_{\text{out}}}{V_{\text{out}}} = \frac{g_{\text{ds}}}{1 + \frac{g_m + g_{\text{ds}}}{G_S}} = \frac{g_{\text{ds}} \cdot G_S}{G_S + g_m + g_{\text{ds}}} \quad (34)$$

We find that if $G_S = 0$ ($R_S \rightarrow \infty$) then $g_{\text{out}} = 0$ ($r_{\text{out}} \rightarrow \infty$), and if $G_S \rightarrow \infty$ ($R_S = 0$) then $g_{\text{out}} = g_{\text{ds}}$.

We can further calculate the benefits of a cascode if we assume we put a cascode on top of a common-source transistor stage (thus $G_S = g'_{\text{ds}}$) and get

$$g_{\text{out}} = \frac{g_{\text{ds}} \cdot g'_{\text{ds}}}{g'_{\text{ds}} + g_m + g_{\text{ds}}} \approx g'_{\text{ds}} \frac{g_{\text{ds}}}{g_m} \quad (35)$$

! Benefit of Cascode (Output)

The output impedance of the lower MOSFET ($r_{\text{out}} = 1/g'_{\text{ds}}$) is **increased** by the self-gain (g_m/g_{ds}) of the cascode transistor! This is a powerful technique to increase the output impedance of a transistor stage by cascoding, much better than increasing L !

9.2 Cascode Input Impedance

To calculate the input impedance of a cascode (i.e., looking into the source) we replace G_S with a current source. The resulting small-signal equivalent circuit is shown in Figure 64.

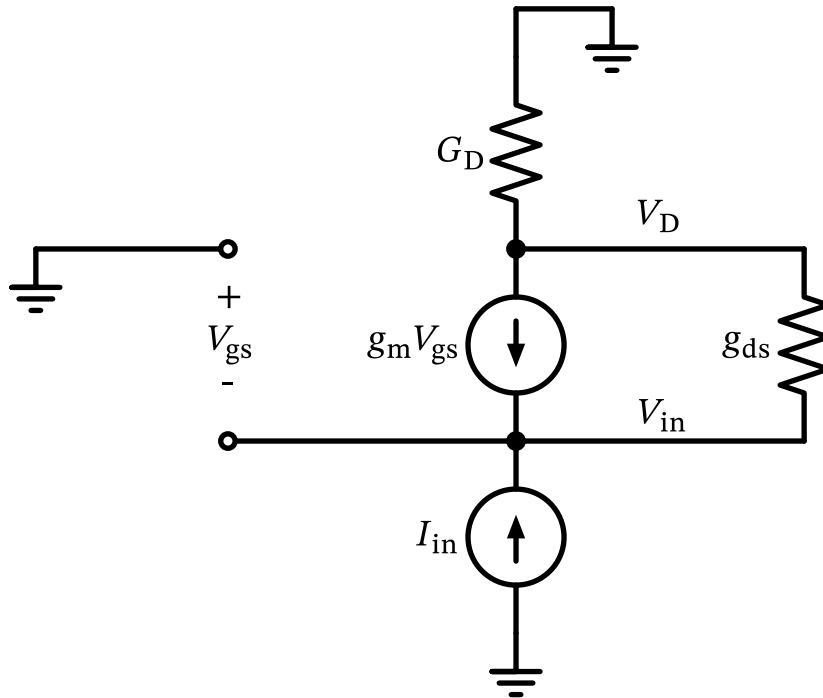


Figure 64: The simplified MOSFET cascode small-signal model for calculation of the input impedance.

We note that $V_{\text{gs}} = -V_{\text{in}}$ and that I_{in} flows through G_D (again, there is no other way to go), resulting in $V_D = I_{\text{in}}/G_D$. Note that $V_{\text{ds}} = V_D - V_{\text{in}}$. Formulating KCL at the input node results in

$$I_{\text{in}} + g_{\text{ds}} V_{\text{ds}} + g_m V_{\text{gs}} = 0.$$

After some manipulation we find that

$$g_{\text{in}} = \frac{I_{\text{in}}}{V_{\text{in}}} = \frac{(g_m + g_{\text{ds}}) \cdot G_D}{g_{\text{ds}} + G_D}. \quad (36)$$

Setting $G_D = 0$ ($R_D \rightarrow \infty$) results in $g_{\text{in}} = 0$ ($r_{\text{in}} \rightarrow \infty$) as well, so the input impedance of the cascode becomes very large when the drain impedance is large.

However, setting $G_D = \infty$ ($R_D = 0$) results in the well-known result of

$$g_{in} = g_m + g_{ds} \approx g_m,$$

which means that the input impedance looking into a cascode is $r_{in} \approx g_m^{-1}$.

! Benefit of Cascode (Input)

This has the practical benefit that a capacitance connected at this node results in a high-frequency pole, which is often not critical in terms of stability. Further, the voltage swing at a cascode input node is small due to the often small impedance, and this minimizes the Miller effect at connected inter-node capacitors (see Section 17.1).

10 Improved Current Mirrors

In Section 6, we looked into the operation of the basic current mirror. While it is a useful structure and easy to implement, its output resistance is limited by the MOSFET's output conductance to $r_{out} = g_{ds}^{-1}$, and its current mirroring accuracy is also limited by channel-length modulation effects since the V_{DS} of the output transistor varies with load conditions, and is thus different from the V_{DS} of the reference transistor.

Using the cascode principle introduced in Section 9, we can improve both the output resistance and the current mirroring accuracy of the current mirror by adding a cascode stage (shown in blue). The improved current mirror structure is shown in Figure 65.

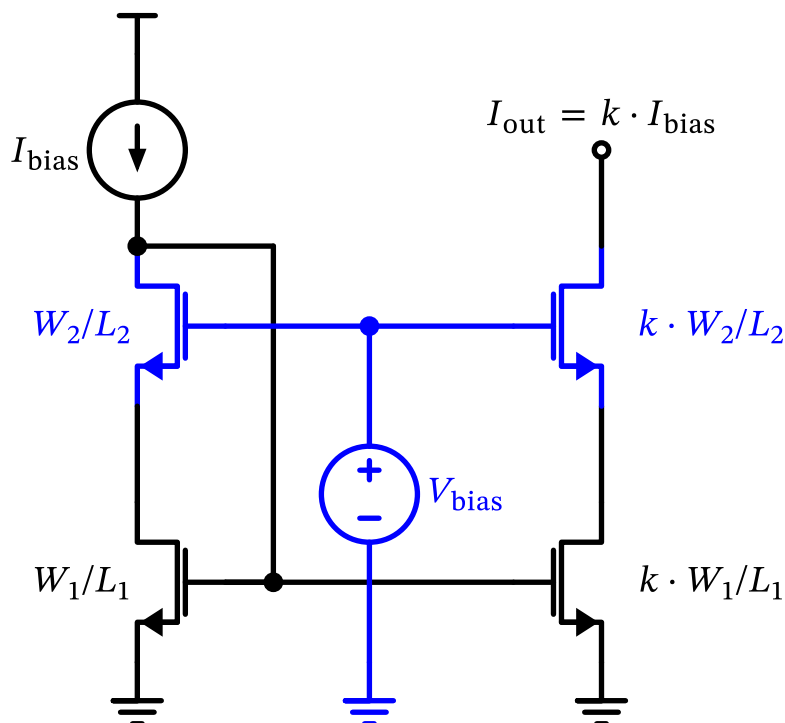


Figure 65: A cascoded current mirror using a biasing voltage to set the cascode gate potential.

We can see that by introducing the cascode transistors we achieve the following benefits:

1. Increased output resistance, as we have seen in Equation 34.
2. Improved current mirroring accuracy, since the cascode transistors help to keep the drain-source voltage of the output transistor nearly constant and equal to that of the reference transistor.

There are several ways to implement the bias voltage V_{bias} for setting the cascode transistors' gate potential. One simple option is to use a biasing resistor R_{bias} (highlighted in blue) as shown in Figure 66, which is called a “high-swing” cascode structure.

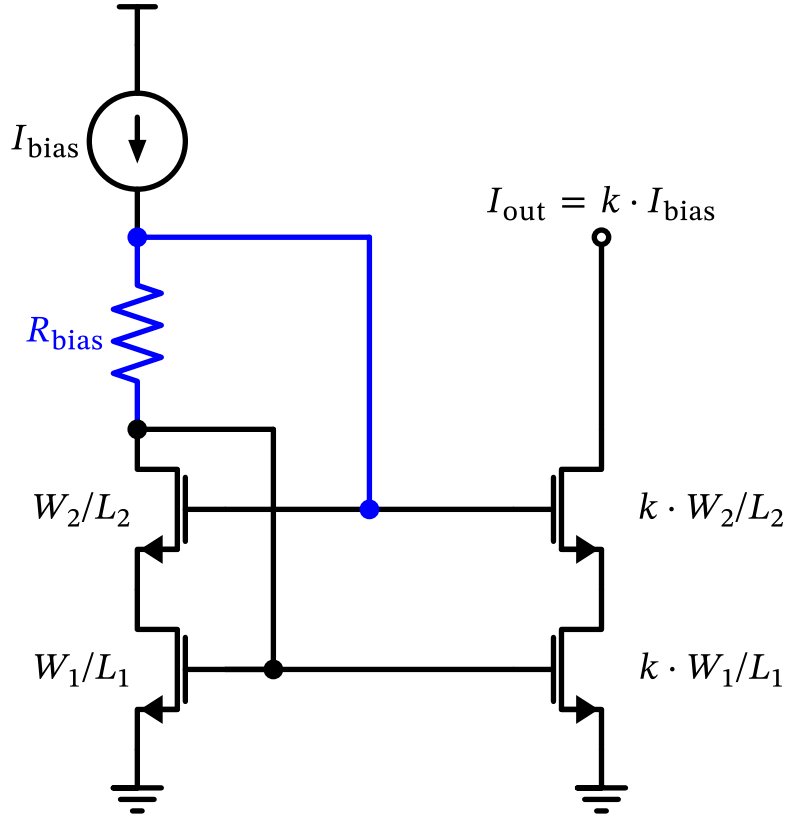


Figure 66: A high-swing cascoded current mirror. The voltage drop across the resistor R_{bias} sets the drain-source voltage of the lower transistors (together with the sizing of the MOSFETs).

The output impedance according to Equation 35 of the improved current mirror is approximately given by ($r_{\text{ds,casc}} = g_{\text{ds,casc}}^{-1}$ and $g_{\text{m,casc}}$ are the parameters of the cascode transistor, and $r_{\text{ds}} = g_{\text{ds}}^{-1}$ is the parameter of the bottom transistor):

$$r_{\text{out}} = r_{\text{ds,casc}} + r_{\text{ds}} \cdot (1 + g_{\text{m,casc}} \cdot r_{\text{ds,casc}}). \quad (37)$$

We can bias the gate voltages of the cascode transistors with any suitable bias circuit, but a simple way is to use a resistor R_{bias} as shown in the figure. The voltage drop across this resistor sets the drain-source voltage of the lower transistors (together with the sizing of the MOSFETs). By choosing a sufficiently large value for R_{bias} , we can ensure that both transistors

remain in saturation for the desired range of output currents. The cascode transistors make sure that the drain-source voltage of the output transistor remains nearly constant and equal to the drain-source voltage of the reference transistor, thus improving the current mirroring accuracy.

Another option for an improved current mirror is to use source degeneration with a resistor. This configuration is shown in Figure 67. Here, the source degeneration resistors R_{deg} help to stabilize the operating point of the current mirror using series feedback.

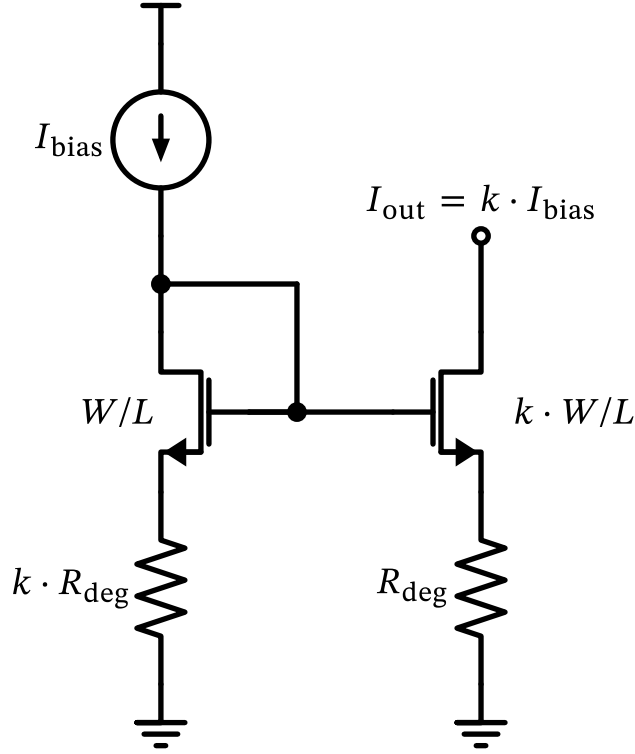


Figure 67: A current mirror with resistive degeneration.

Here, similar to Equation 37, the output resistance can be approximated by

$$r_{\text{out}} = r_{\text{ds}} + R_{\text{deg}} \cdot (1 + g_m \cdot r_{\text{ds}}). \quad (38)$$

A third popular option to implement an improved current mirror is to use the so-called regulated current mirror, which uses an additional amplifier to sense the drain potential of the bottom transistor and keep it constant [30]. Note that the output current will not change if the V_{DS} of the bottom transistor is kept constant. We can use any suitable amplifier for this purpose, e.g., a simple OTA as introduced in Section 8. In the most basic form, we use a common-source stage with a current mirror load as shown in blue in Figure 68.

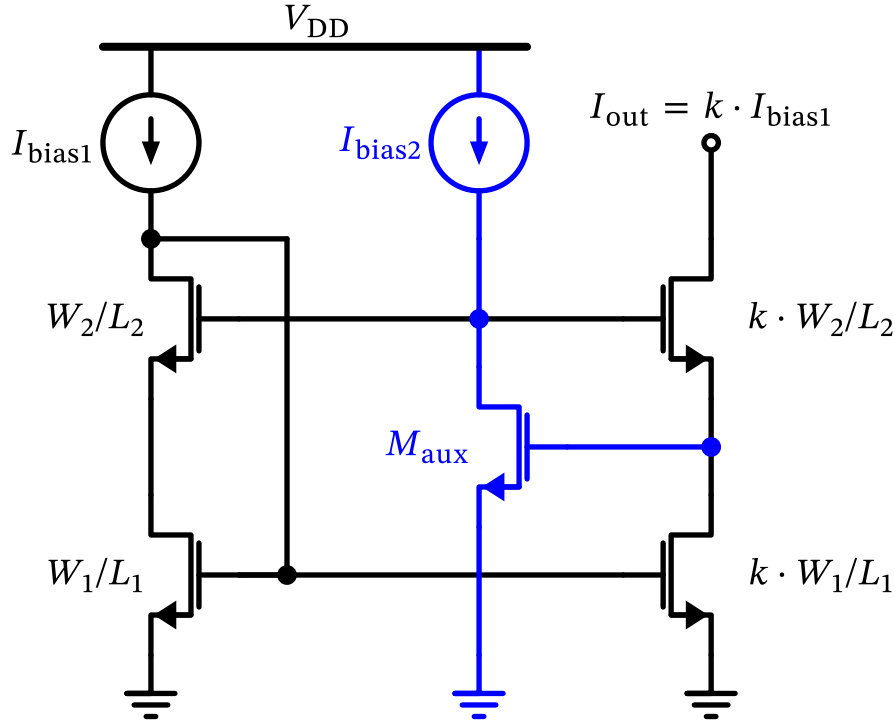


Figure 68: A regulated-cascode current mirror. The simple common-source amplifier is used to keep the drain voltage of the bottom transistor constant, thus improving the current mirroring accuracy and output resistance.

We assume the voltage gain of the auxiliary amplifier to be $A_v = g_{\text{maux}}/g_{\text{dsaux}}$, where g_{maux} and g_{dsaux} are the transconductance and output conductance of the auxiliary amplifier, respectively. The output resistance of the regulated cascode current mirror can then be approximated by

$$\begin{aligned} r_{\text{out}} &= r_{\text{ds,casc}} + r_{\text{ds}} \cdot [1 + g_{\text{m,casc}} \cdot r_{\text{ds,casc}} \cdot (1 + g_{\text{maux}}/g_{\text{dsaux}})] \\ &\approx r_{\text{ds}} \cdot g_{\text{m,casc}} \cdot r_{\text{ds,casc}} \cdot g_{\text{m,aux}} \cdot r_{\text{ds,aux}} \end{aligned} \quad (39)$$

which, compared to Equation 37, is further improved by the gain of the auxiliary amplifier.

We now want to size all these current mirror structures and simulate their performance. We try to size them for similar chip area in order to get a fair comparison. We assume a reference current of $I_{\text{bias}} = 50 \mu\text{A}$ and a mirror ratio of 1:1. We size for a minimum voltage headroom for the current sources of $V_{\text{DS,min}} = 0.4\text{V}$. The calculations are summarized in this sizing notebook.

One structure cannot honor that number, and it is worth seeing why before we look at the simulation results. In the regulated cascode the auxiliary amplifier holds the drain of the bottom device at its own gate-source voltage, so $V_{\text{DS1}} = V_{\text{GSaux}} \approx 0.37\text{V}$, and the cascode transistor stacked on top still needs its own $V_{\text{ds,sat}} \approx 0.2\text{V}$. Its compliance voltage is therefore about 0.57V , not 0.4V – forcing it to 0.4V would simply leave the cascode device in triode, where it does no cascoding at all. This is the drawback we will address in Section 10.1, and it is clearly visible in the simulated output resistance below.

The source-degenerated mirror, in contrast, improves the output resistance only mildly (by about a factor of 1.4), since the degeneration factor $1 + g_m R_{\text{deg}}$ of Equation 38 stays modest for a practical voltage drop across R_{deg} . Its strength lies elsewhere, as we will see next.

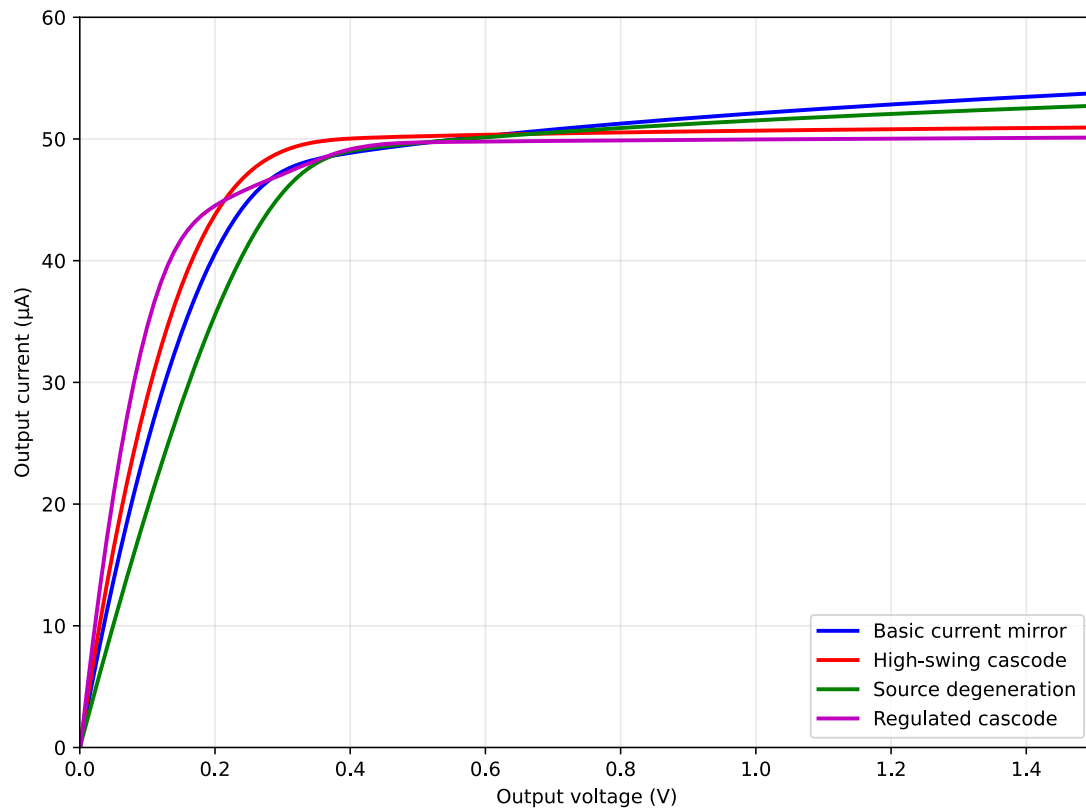


Figure 70: Output characteristics of the four current mirror structures.

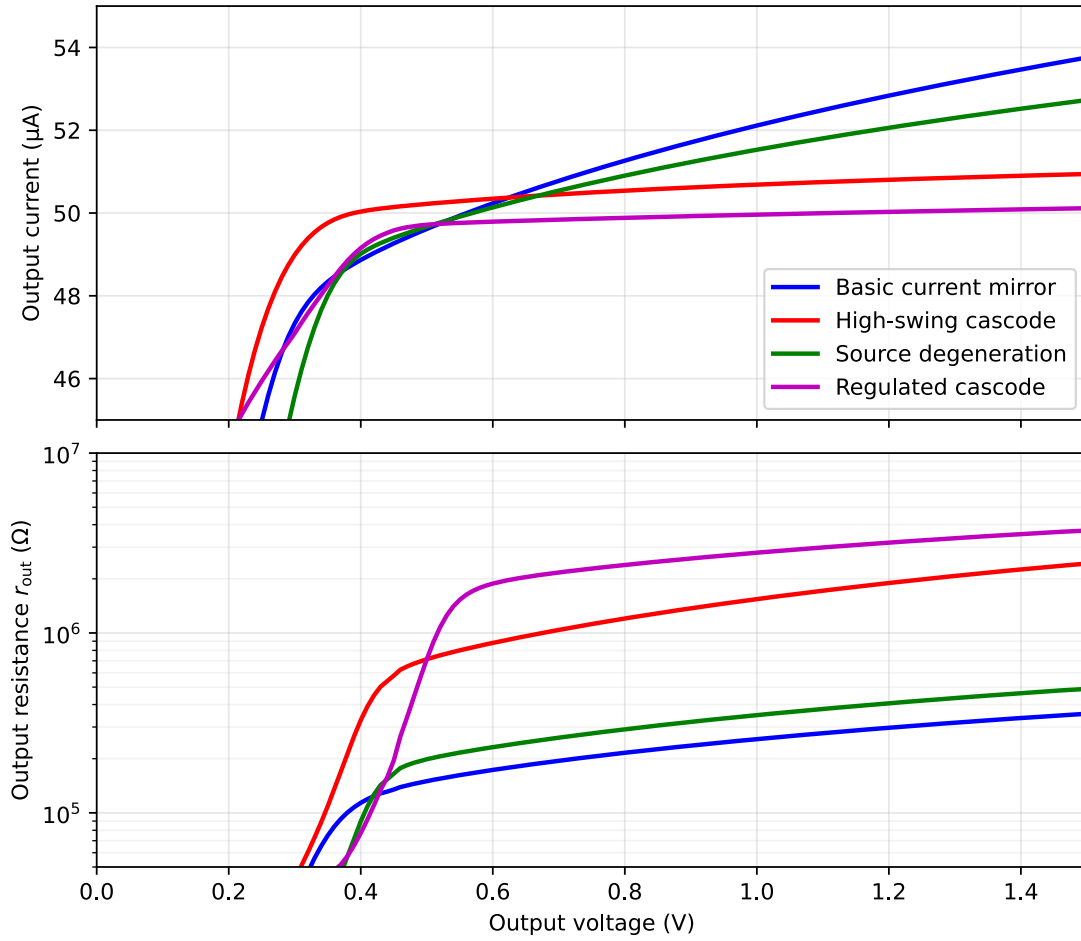


Figure 71: Output characteristics of the four current mirror structures (zoom in, upper panel) and the resulting small-signal output resistance $r_{\text{out}} = dV_{\text{out}}/dI_{\text{out}}$ obtained as the reciprocal slope of these curves (lower panel, logarithmic). The high-swing cascode and the regulated cascode achieve significantly higher output resistance compared to the basic and degenerated current mirror. Note the steep collapse of r_{out} below the compliance voltage, where the output transistors leave saturation, and that r_{out} keeps rising with V_{out} well inside the useful range.

We now look into the results of the Monte-Carlo simulation to evaluate the current mirroring accuracy under device mismatch using 500 runs and a compliance voltage of 0.4 V. The results are summarized in Figure 72. We can see that the high-swing cascode and the regulated cascode achieve a very precise nominal current accuracy of almost 50 μA . However, the source-degenerated current mirror shows a significantly reduced spread of the output current, indicating a reduced mismatch of the poly-silicon resistors compared to the MOSFETs.

It is instructive to also look at the reverse side of the coin. The relative spread comes out as 0.42 % for the basic mirror, 0.24 % for the source-degenerated one, but 0.83 % for the high-swing cascode and 1.79 % for the regulated cascode. The two cascoded structures thus match **worse** than the plain current mirror, because the cascode devices (and, in the regulated case, the auxiliary amplifier with its own bias current sources) contribute their own mismatch on top of that of the bottom transistor pair. Output resistance and current accuracy are therefore not improved by the same measure: a cascode buys you the former and can cost you the latter. This is a good example of why a structure should never be selected on a single figure of merit.

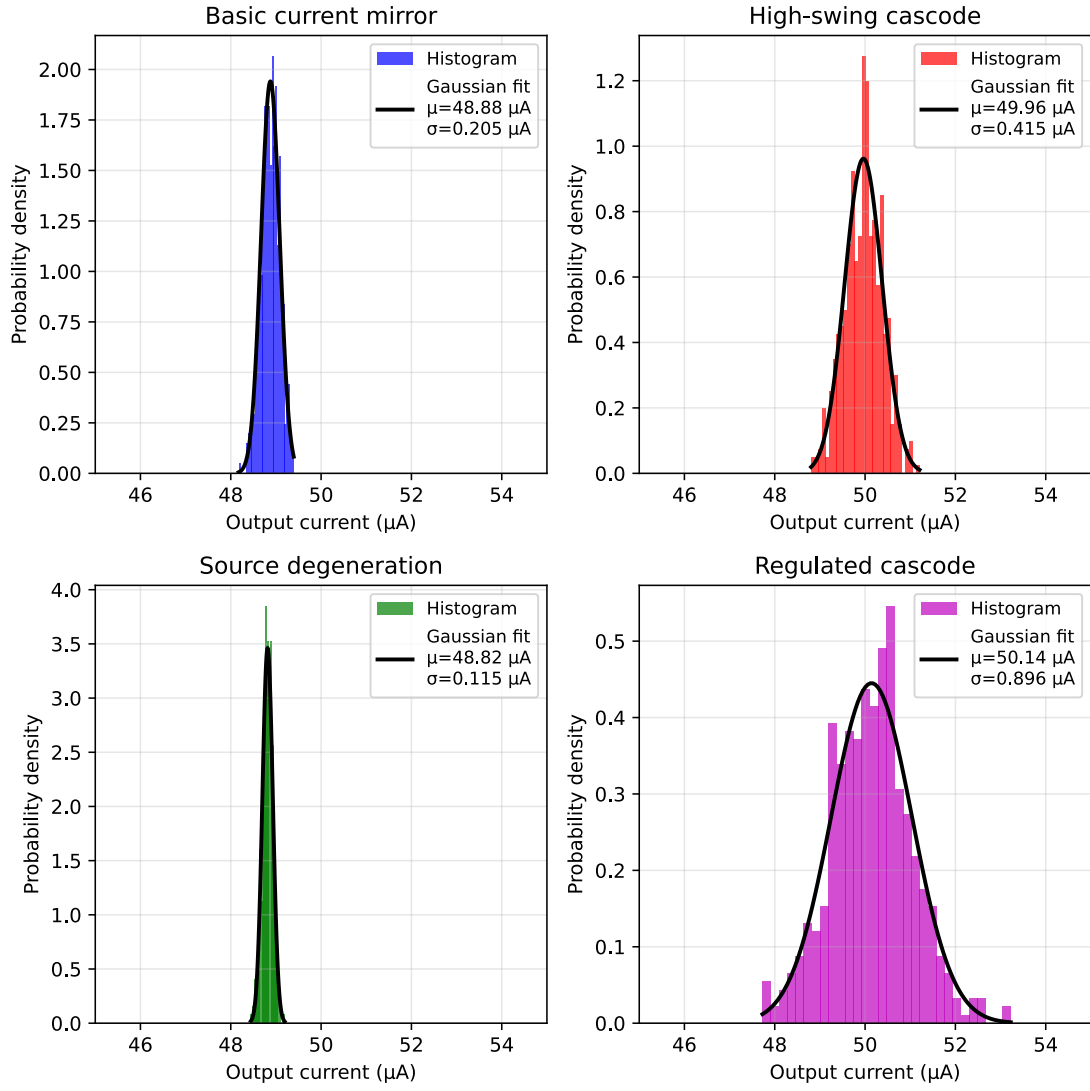


Figure 72: Monte Carlo analysis of the four current mirror structures showing current distribution and fitted Gaussian curves.

Finally, we compare the output noise of the four different current mirror structures in Figure 73. We can see that the regulated cascode has the highest output noise due to the additional auxiliary amplifier, while the source-degenerated mirror has the lowest output noise.

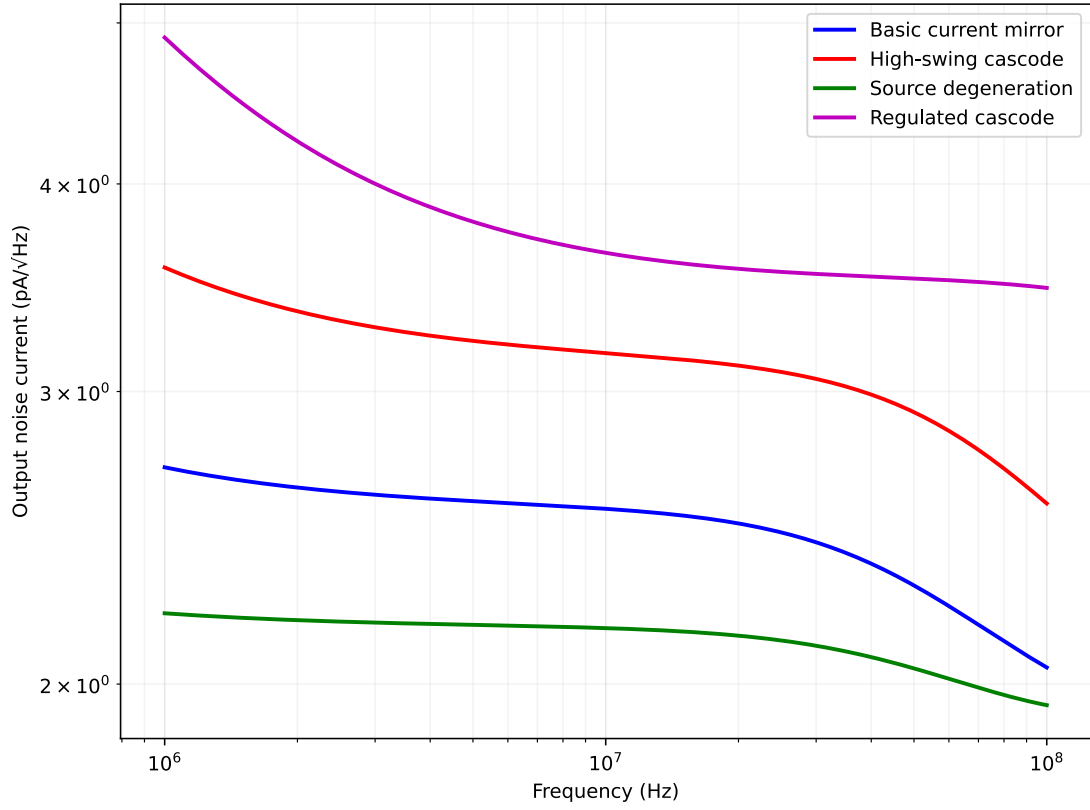


Figure 73: Output noise current vs. frequency for the four current mirror structures.

10.1 Low-Voltage Regulated Current Mirror

The one drawback of the regulated cascode current mirror shown in Figure 68 is its relatively high compliance voltage, which is due to the fact that $V_{DS1} = V_{GSaux}$. One alternative implementation that reduces the compliance voltage is shown in Figure 74. Here, we use a differential common-gate stage (essentially a current mirror with inputs at the sources of the transistors) as an auxiliary amplifier, which significantly reduces the required voltage headroom, at the expense of a slightly increased circuit complexity [31]. However, the bias current sources $I_{bias2,3}$ of the auxiliary amplifier introduce some additional noise and mismatch.

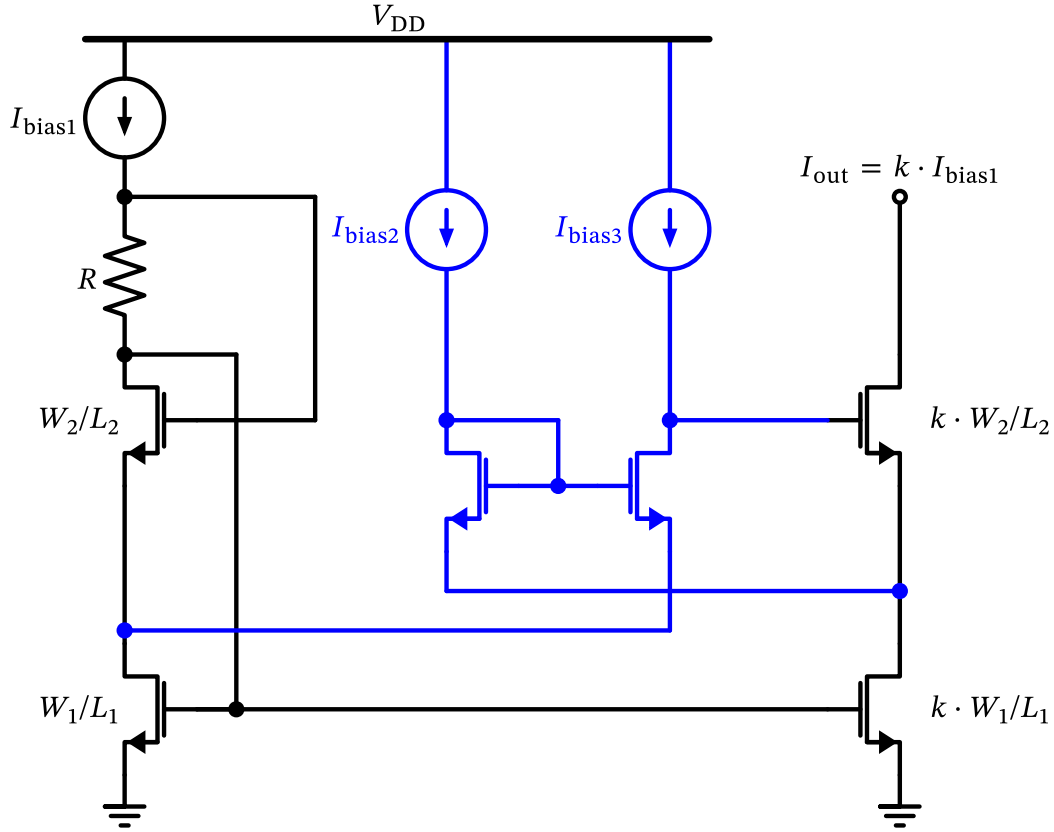


Figure 74: A low-voltage regulated-cascode current mirror. The differential common-gate error amplifier is used to keep the drain voltage of the bottom transistors constant, thus improving the current mirroring accuracy and output resistance.

10.2 Current Source Variations Summary

In summary, we can classify the usage of the different current mirror structures as follows:

- For general applications where output resistance and current accuracy are not critical, the **basic current mirror** can be used. It also has the lowest compliance voltage since only one transistor is stacked.
- The **high-swing cascode current mirror** is a good choice when higher output resistance is needed, while still keeping the circuit relatively simple. Be aware that the added cascode devices roughly double the current spread under mismatch compared to the basic mirror.
- The **source-degenerated current mirror** is a good choice when the best current matching and low output noise are required. The additional voltage headroom that is dropped across the source degeneration can be adapted (higher is better), but a minimum value of 0.1 V should be used. Note that its output resistance is only mildly improved.
- The **regulated cascode current mirror** is the best choice when the highest output resistance is required, and the additional complexity, output noise, and a roughly four-fold larger current spread under mismatch are acceptable.
- The **low-voltage regulated cascode current mirror** is a good alternative to the regulated cascode when a low compliance voltage is required.

Please note that the absolute performance can be tweaked by proper sizing. The examples shown here are sized for similar chip area and a fair comparison.

10.3 Current Mirror Matching

Looking at the different current mirror architectures in Section 10, we can see that the current mirror matching is dominated by the bottom transistor pair (assuming equal V_{DS}), with the exception of the resistively degenerated current mirror. We asserted that the matching of the resistively-degenerated current mirror is improved due to the lower impact of MOSFET mismatch compared to resistor mismatch. We will now substantiate this claim.

We will derive the current mirror matching of a pair of resistively-degenerated current mirror transistors shown in Figure 67.

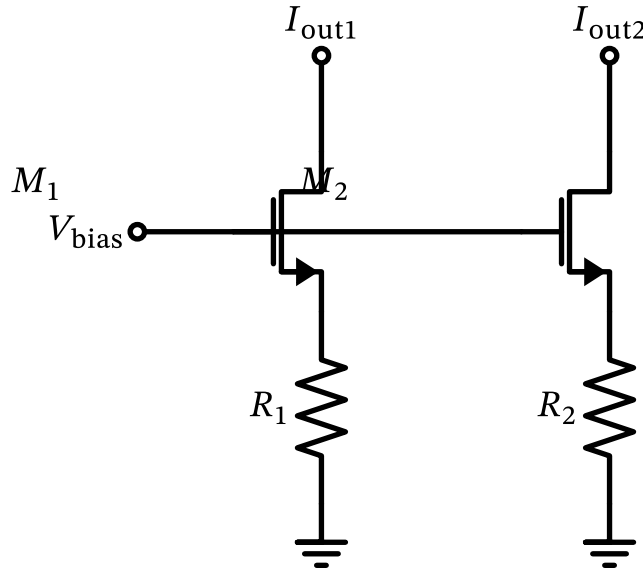


Figure 75: A current mirror pair with resistive degeneration.

The variance σ^2 of the output current difference, normalized to the current, is given by [1]

$$\begin{aligned} \sigma^2 \left\{ \frac{\Delta I_D}{I_D} \right\} &= \frac{\sigma^2 \{ \Delta V_{th} \}}{(V_{drv} + V_{deg})^2} + \left(\frac{V_{drv}}{V_{drv} + V_{deg}} \right)^2 \cdot \sigma^2 \left\{ \frac{\Delta K}{K} \right\} \\ &+ \left(\frac{V_{deg}}{V_{drv} + V_{deg}} \right)^2 \cdot \sigma^2 \left\{ \frac{\Delta R}{R} \right\}. \end{aligned} \quad (40)$$

The definition of V_{drv} is adapted here and understood as half of the V_{DS} saturation voltage, i.e., $V_{drv} = V_{DS,sat}/2 \approx I_D/g_m$. The degeneration voltage is the voltage drop across the degeneration resistors and given by $V_{deg} = I_D \cdot R$.

The standard deviation of the resistor $\sigma \{ \Delta R/R \}$ can be calculated using Equation 32. Further, the threshold voltage mismatch $\sigma \{ \Delta V_{th} \}$ can be calculated using Equation 28.

By using the approximation of Equation 4, we can express Equation 40 in terms of our preferred sizing parameter g_m/I_D :

$$\sigma^2\left\{\frac{\Delta I_D}{I_D}\right\} = \frac{\sigma^2\{\Delta V_{th}\}}{[(g_m/I_D)^{-1} + V_{deg}]^2} + \left(\frac{1}{1 + V_{deg} \cdot g_m/I_D}\right)^2 \cdot \sigma^2\left\{\frac{\Delta K}{K}\right\} + \left(\frac{V_{deg} \cdot g_m/I_D}{1 + V_{deg} \cdot g_m/I_D}\right)^2 \cdot \sigma^2\left\{\frac{\Delta R}{R}\right\}. \quad (41)$$

The standard deviation of the transconductance parameter mismatch $\sigma\{\Delta K/K\}$ can be calculated similarly as (which is an alternative form to Equation 29)

$$\sigma^2\left\{\frac{\Delta K}{K}\right\} = \sigma^2\{\Delta W\} \cdot \frac{1}{W^2} + \sigma^2\{\Delta L\} \cdot \frac{1}{L^2} + A_\mu^2 \cdot \frac{1}{WL}, \quad (42)$$

where $\sigma\{\Delta W\}$ and $\sigma\{\Delta L\}$ are the process-dependent absolute mismatch parameters for the width W and length L , respectively. The mobility mismatch follows Pelgrom's law like the threshold voltage, so it is described by an area-scaled constant $A_\mu = \sigma\{\Delta\mu/\mu\} \cdot \sqrt{WL}$, which is the quantity listed in Table 4.

The standard deviations of the components of the SG13G2 process are summarized in Table 4. For mismatch calculations we can assume them to be uncorrelated.

Table 4: IHP SG13G2 device mismatch

Component	Matching Parameter	Value
Resistor <i>rsil</i>	$\sigma\{\Delta R/R\} \cdot \sqrt{WL}$	1.2 % μm
Resistor <i>rppd</i>	$\sigma\{\Delta R/R\} \cdot \sqrt{WL}$	1.5 % μm
Resistor <i>rhigh</i>	$\sigma\{\Delta R/R\} \cdot \sqrt{WL}$	5 % μm
MIM <i>cap_cmim</i>	$\sigma\{\Delta C/C\} \cdot \sqrt{WL}$	1 % μm (estimated)
MOSFET <i>sg13_lv_nmos</i>	$\sigma\{\Delta V_{th}\} \cdot \sqrt{WL}$	3.9 mV μm
MOSFET <i>sg13_lv_nmos</i>	$\sigma\{\Delta W\}$	4 nm
MOSFET <i>sg13_lv_nmos</i>	$\sigma\{\Delta L\}$	2 nm
MOSFET <i>sg13_lv_nmos</i>	$\sigma\{\Delta\mu/\mu\} \cdot \sqrt{WL}$	0.5 % μm
MOSFET <i>sg13_lv_pmos</i>	$\sigma\{\Delta V_{th}\} \cdot \sqrt{WL}$	2.2 mV μm
MOSFET <i>sg13_lv_pmos</i>	$\sigma\{\Delta W\}$	4 nm
MOSFET <i>sg13_lv_pmos</i>	$\sigma\{\Delta L\}$	2 nm
MOSFET <i>sg13_lv_pmos</i>	$\sigma\{\Delta\mu/\mu\} \cdot \sqrt{WL}$	0.33 % μm

Inspecting Equation 40 we can see that by implementing a common-source transistor without source degeneration (i.e., $V_{\text{deg}} = 0$), the current mirror matching is dominated by the threshold voltage mismatch and the transconductance parameter mismatch of the MOSFETs:

$$\sigma^2 \left\{ \frac{\Delta I_D}{I_D} \right\} = \sigma^2 \{ \Delta V_{\text{th}} \} \left(\frac{g_m}{I_D} \right)^2 + \sigma^2 \left\{ \frac{\Delta K}{K} \right\} \quad (43)$$

The first term in Equation 43 can be minimized by choosing a low g_m/I_D ratio, while the latter term is minimized by increasing the device area (i.e., increasing W and L).

Looking at the resistively-degenerated current mirror, and using a large degeneration voltage V_{deg} , we can simplify Equation 41 to

$$\sigma^2 \left\{ \frac{\Delta I_D}{I_D} \right\} = \sigma^2 \left\{ \frac{\Delta R}{R} \right\} \quad (44)$$

indicating that now the current matching of the degenerated current mirror is defined by the resistor matching only. Since resistors can be matched considerably better than MOSFETs, this can lead to a significant improvement in current mirror accuracy, but only if the resistor is given enough area, as the worked example below will show.

i Current Mirror Matching Calculation

Let us now calculate the current mirror matching of the simple current mirror. Using Equation 43, and using the sizing values of $g_m/I_D = 5 \text{ V}^{-1}$, $W = 10 \mu \text{ m}$, and $L = 5 \mu \text{ m}$, we can calculate the standard deviation of the transconductance parameter mismatch using Equation 42 and Table 4:

$$\sigma\left\{\frac{\Delta K}{K}\right\} = \sqrt{\left(\frac{4 \text{ nm}}{10 \mu \text{ m}}\right)^2 + \left(\frac{2 \text{ nm}}{5 \mu \text{ m}}\right)^2 + \left(\frac{0.5 \% \mu \text{ m}}{\sqrt{10 \mu \text{ m} \cdot 5 \mu \text{ m}}}\right)^2} = 0.09 \%.$$

The standard deviation of the threshold voltage mismatch can be calculated using Equation 28 and Table 4:

$$\sigma\{\Delta V_{\text{th}}\} = \frac{3.9 \text{ mV } \mu \text{ m}}{\sqrt{10 \mu \text{ m} \cdot 5 \mu \text{ m}}} = 0.55 \text{ mV}.$$

Bringing both results into Equation 43, we get

$$\sigma\left\{\frac{\Delta I_D}{I_D}\right\} = \sqrt{(0.55 \text{ mV} \cdot 5 \text{ V}^{-1})^2 + (0.09 \%)^2} \approx 0.29 \%.$$

Comparing with the simulation results in Figure 72 for the basic current mirror, we can see that this gives a reasonable estimate compared to the standard deviation of about $0.21 \mu \text{ A} / 48.9 \mu \text{ A} = 0.43 \%$ obtained from the Monte-Carlo simulation. The remaining discrepancy is due to simplifications in the analytical model (e.g., the square-law approximation).

Let us now calculate the current mirror matching of the resistively-degenerated current mirror. We can use Equation 41 to analyze this configuration. We use the sizing values of $g_m/I_D = 10 \text{ V}^{-1}$, $W = 20 \mu \text{ m}$, and $L = 3 \mu \text{ m}$, for the MOSFET, and $V_{\text{deg}} = 0.2 \text{ V}$, and $W = 3 \mu \text{ m} / L = 45 \mu \text{ m}$ for the used **rppd** resistor (which at $R_s = 260 \Omega$ gives the required $R_{\text{deg}} \approx 3.9 \text{ k } \Omega$).

The standard deviation of the transconductance parameter mismatch can be calculated as

$$\sigma\left\{\frac{\Delta K}{K}\right\} = \sqrt{\left(\frac{4 \text{ nm}}{20 \mu \text{ m}}\right)^2 + \left(\frac{2 \text{ nm}}{3 \mu \text{ m}}\right)^2 + \left(\frac{0.5 \% \mu \text{ m}}{\sqrt{20 \mu \text{ m} \cdot 3 \mu \text{ m}}}\right)^2} = 0.09 \%.$$

The standard deviation of the threshold voltage mismatch can be calculated as

$$\sigma\{\Delta V_{\text{th}}\} = \frac{3.9 \text{ mV } \mu \text{ m}}{\sqrt{20 \mu \text{ m} \cdot 3 \mu \text{ m}}} = 0.50 \text{ mV}.$$

The standard deviation of the resistor mismatch can be calculated using Equation 32 and Table 4:

$$\sigma\left\{\frac{\Delta R}{R}\right\} = \frac{1.5 \% \mu \text{ m}}{\sqrt{3 \mu \text{ m} \cdot 45 \mu \text{ m}}} = 0.13 \%.$$

Plugging these results into Equation 41, we get

$$\begin{aligned} \sigma^2\left\{\frac{\Delta I_D}{I_D}\right\} &= \underbrace{\left(\frac{0.50 \text{ mV}}{0.1 \text{ V} + 0.2 \text{ V}}\right)^2}_{(0.17 \%)^2} + \underbrace{\left(\frac{1}{1 + 0.2 \text{ V} \cdot 10 \text{ V}^{-1}} \cdot 0.09 \%\right)^2}_{(0.03 \%)^2} \\ &\quad + \underbrace{\left(\frac{0.2 \text{ V} \cdot 10 \text{ V}^{-1}}{1 + 0.2 \text{ V} \cdot 10 \text{ V}^{-1}} \cdot 0.13 \%\right)^2}_{(0.02 \%)^2} \end{aligned}$$

With the newly learned know-how of the cascode stage we can set out to improve our original basic 5T-OTA design. Essentially this means adding cascodes to M_2 and M_4 in Figure 32. For symmetry reasons we add cascodes to both sides, and the resulting schematic is shown in Figure 76. This configuration is also referred to as “**telescopic OTA**” (likely because of the stacked structure, where all the transistors are stacked in a current path like the tubes of a telescope).



! Cascode Bias Voltage Generation

101

The current mirror constructed out of $M_{3,3C}$ and $M_{4,4C}$ is a special kind of **cascode current mirror for low-voltage operation**, also referred to as high-swing cascode current mirror [12]. This type is very often used, as it forces the V_{GS} and V_{DS} of $M_{3,4}$ to be equal, so the current mirror ratio is independent of g_{ds} .

 Exercise: Cascode Current Mirror vs. High-Swing Cascode Current Mirror

Try to verify the above statement of equal drain-source voltages by deriving both, an equation for V_{DS4} assuming a high-swing cascode current mirror (Figure 76) and V_{DS4} in case of a simple cascode current mirror, where the reference branch ($M_{3,3C}$) is comprised of two MOSFET diodes.

Further, by properly selecting the bias voltages of the cascode a low-voltage operation is achieved as V_{DS} can be minimized, allowing even triode operation of the current-mirror MOSFETs (as, noted above, a large g_{ds} is not a big issue).

A simplified small-signal gain calculation of this improved OTA uses the result of Equation 18 and Equation 35 to arrive at the approximate dc gain of

$$A_0 \approx \frac{g_{m12}}{g_{ds2} \frac{g_{ds2C}}{g_{m2C}} + g_{ds4} \frac{g_{ds4C}}{g_{m4C}}} \quad (45)$$

leading to a significant boost in dc gain due to cascoding. We use this increased gain to reduce the L of all MOSFET to

1. save area (a smaller L will lead to a smaller W for a given W/L ratio) and
2. push the additional poles and zeros at the inner nodes of the cascode transistors (e.g., the connection of the drain of M_4 to the source of M_{4C}) to higher frequencies to result in stable behavior and a reasonable gain transfer function (too many poles and zeros in the pass band of the amplifier create many issues with stability margin).

11.1 Sizing the Improved OTA

Like the sizing of the 5T-OTA in Section 8.4 we again use the g_m/I_D method using a Python notebook. Instead of using $L = 5 \mu\text{m}$ we this time use a reduced $L = 0.5 \mu\text{m}$ for $M_{1/1C,2/2C,3/3C,4/4C}$ (for speed reasons) and $L = 5 \mu\text{m}$ for $M_{5,6}$ for better common-mode rejection (the tail current mirror is less critical in terms of speed and stability).

We set $g_m/I_D = 13$ across the board for a good trade-off between speed, current efficiency, and voltage headroom for the MOSFETs (this is now way more critical than in the basic 5T-OTA as we now stack twice as many MOSFETs at the same supply voltage). Please look at Section 3 to confirm this choice.

Sizing for Basic (Improved) OTA

Copyright 2024-2025 Harald Pretl

Licensed under the Apache License, Version 2.0 (the “License”); you may not use this file except in compliance with the License. You may obtain a copy of the License at <http://www.apache.org/licenses/LICENSE-2.0>

```
# read table data
from pygmid import Lookup as lk
import numpy as np
lv_nmos = lk('sg13_lv_nmos.mat')
lv_pmos = lk('sg13_lv_pmos.mat')
# list of parameters: VGS, VDS, VSB, L, W, NFING, ID, VT, GM, GMB, GDS,
CGG, CGB, CGD, CGS, CDD, CSS, STH, SFL
# if not specified, minimum L, VDS=max(vgs)/2=0.9 and VSB=0 are used
```

```
# define the given parameters as taken from the specification table or
initial guesses
c_load = 50e-15
gm_id_m12 = 13
gm_id_m12c = 13
gm_id_m34 = 13
gm_id_m34c = 13
gm_id_m56 = 13
l_12 = 0.5
l_12c = 0.5
l_34 = 0.5
l_34c = 0.5
l_56 = 5
f_bw = 10e6 # -3dB bandwidth of the voltage buffer
i_total_limit = 10e-6 # we plan 2x5uA in addition for additional bias
voltage generation
i_bias_in = 5e-6
output_voltage = 1.3
vin_min = 0.7
vin_max = 0.9
vdd_min = 1.45
vdd_max = 1.55
vds_headroom = 0.2
```

```
# we get the required gm of M1/2 from the -3dB bandwidth requirement of
the voltage buffer specification
# note that the -3dB bandwidth of the voltage buffer with gain Av=1 is
equal to the unity gain bandwidth
```

Looking at this sizing result we see that we achieve an improved $A_0 > 43$ dB while meeting also the other performance requirements of Table 2 with margin. In addition, we check the voltage headroom of the critical MOSFET to see if we can squeeze it into the available supply voltage range, and see that this is possible with our above choice selection of parameters.

💡 Exercise: Improved OTA Sizing

Please take a detailed look at the above sizing notebook and play with the numbers and calculations. Do you find a better trade-off for the input parameters? Can you understand the thinking process behind the choices and calculations?

11.2 Designing the Improved OTA

Based on the collected experience in this lecture and the result of the sizing procedure in Section 11.1 you should be able to design this OTA. If you want, please go ahead and try an implementation and check its performance with CACE. Looking at the design in Figure 76 we can see that we still have the task to create the bias voltages V_{bias1} and V_{bias2} , and we have to take care of practical issues like power-down, proper biasing, and so on.

In Figure 77 you can see a possible implementation of the bias voltage generation which we will then implement in Figure 78. The additional current mirror transistors $M_{8,9}$ create a small current flowing through M_{10} to establish $V_{\text{bias1}} = V_{\text{GS10}} + V_{\text{tail}}$. The V_{GS} of M_8 is used to create $V_{\text{bias2}} = V_{\text{DD}} - V_{\text{GS8}}$. Note that it is an important design aspect that V_{bias1} tracks variations in V_{tail} to keep the V_{DS} of $M_{1,2}$ constant with changing common-mode input voltage. Likewise, V_{bias2} has to track variations in V_{DD} to keep the V_{DS} of $M_{3,4}$ constant with changing supply voltage.

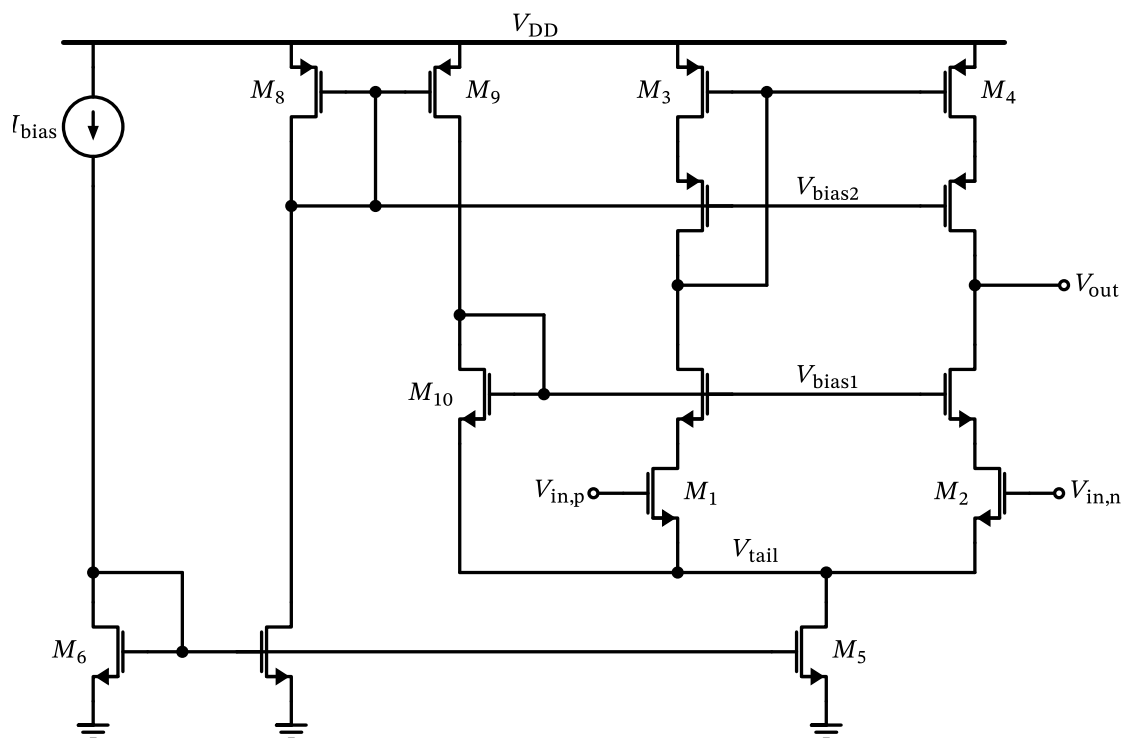


Figure 77: The improved OTA based on the 5T-OTA design with biasing details shown.

The transistor-level implementation is finally shown in Figure 78, and it also includes practical design aspects like power-down transistors, current sensing elements, and decoupling capacitors on sensitive bias nodes.

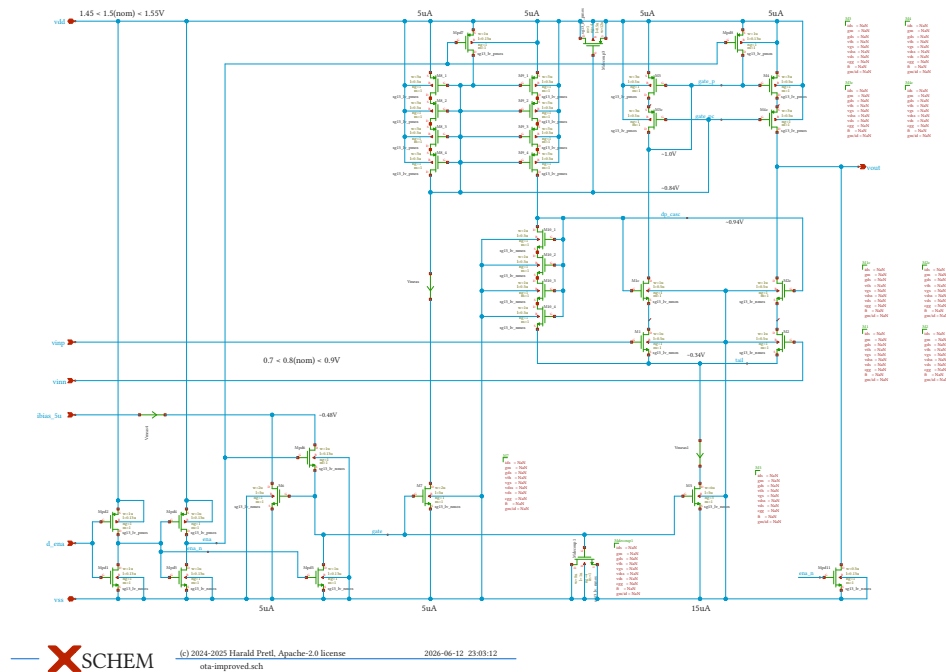


Figure 78: Improved OTA design in Xschem.

11.2.1 Discussion of the OTA Design

We now do an analysis of the circuit design of the OTA including all the complications which make this design practical.

1. For easier navigation, the device identifiers are consistent with the circuit sketch in Figure 76.
2. Some MOSFET dimensions are rounded to make a better fit in the IC layout. Please also look carefully at W , L , and ng . The parameter ng defines how the total W of a MOSFET should be split into individual MOSFET fingers with $W_f = W/ng$. This is done to arrive at a suitably sized MOSFET physical implementation. As we will not deal with IC layout in this lecture we will leave it at that.
3. In order to allow good matching in the IC layout, MOSFETs (and other components) have to be constructed from equal pieces. To that end, W/L scaling is done using unit elements (see finger width W_f). Sometimes, besides W the length L has to be scaled, and this leads to the odd-looking series stacking of some MOSFETs (easily recognizable by the connected gates). In order to increase circuit readability, a subcircuit could be constructed hiding this series stacking of MOSFET, but it is sometimes easier to avoid subcircuits. There is a fine line in this trade-off, sometimes a depth of 4 is the decision point between subcircuit use/no-use.
4. As you can (hopefully) see the circuit is carefully drawn to ease readability. Important nets are named, text comments state certain properties like nominal voltage levels, bias currents, etc. Current sensing elements are added to directly see the dc currents in the circuit simulation.

Exercise: Improved OTA Initial Simulation

Please use the above testbenches to simulate the improved OTA:

1. Check the dc bias points. Are they good? How stable are they across PVT variations?
2. What are the small-signal parameters like gain, noise and bandwidth? Are they fitting the specification?
3. What is large-signal performance? Is the settling fast enough? Is the settling well behaved, i.e., are there overshoots or other strange ringing indicating potential stability issues?
4. Try to improve the design. Change various device parameters and see what happens. Whenever you change something, check the dc operating point first. If the dc operating point is not good no further simulations make sense.

11.4 Corner Simulation of Improved OTA

Just like for the basic OTA we use the CACE system to check the performance of the improved OTA design holistically across variations like PVT and input signal variations. The results of the CACE run are shown below in Note 3.

Note 3: CACE Summary for Improved OTA


CACE Summary for ota-improved

netlist source: schematic

Parameter	Tool	Result	Min Limit	Min Value	Typ Value	Max Value	Max Limit	Status
Output voltage ratio	ngspice	gain	0.99 V/V	1.000 V/V	any	1.002 V/V	1.01 V/V	Pass ✔
Bandwidth	ngspice	bw	14660000.000 Hz	206653000.000 Hz	any	254164000.000 Hz	4000.000 Hz	Pass ✔
Output voltage ratio (MC)	ngspice	gain_mc	any V/V	1.002 V/V	any	1.002 V/V	1.002 V/V	Pass ✔
Bandwidth (MC)	ngspice	bw_mc	204156000.000 Hz	2071620500.000 Hz	any	210269000.000 Hz	4000.000 Hz	Pass ✔
Output noise	ngspice	noise	any mV	0.309 mV	any	0.391 mV	0.6 mV	Pass ✔
Settling time	ngspice	tsettle	any us	0.134 us	any	0.141 us	1 us	Pass ✔

Plots

gain_vs_temp

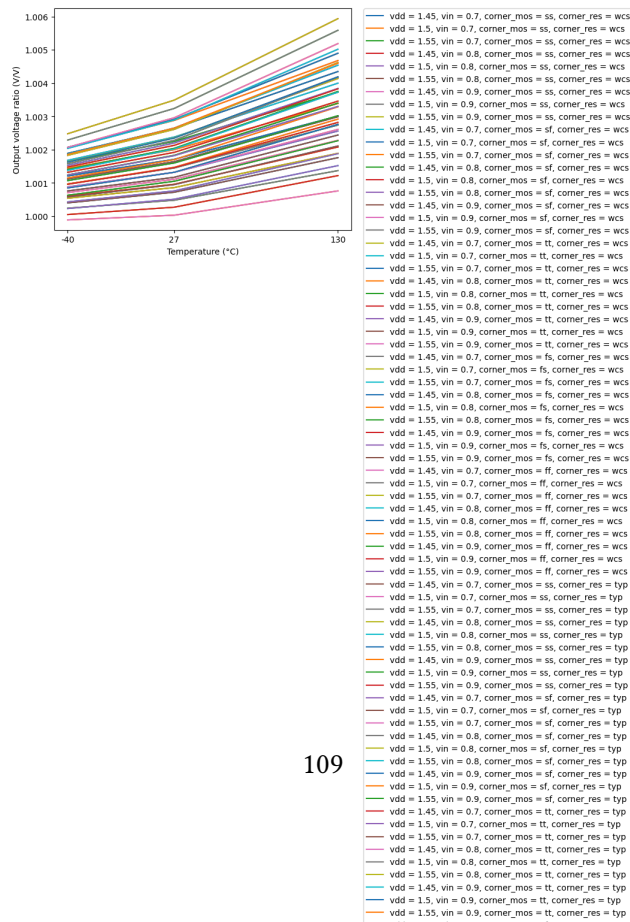

The increased performance allows to improve the specifications in a few important points, notably the output voltage tolerance which is an important metric for a reference voltage buffer. The new situation with the improved design is summarized in Table 5 (unchanged entries are not shown).

The supply current budget in that table deserves a comment, since at first glance it looks like a step backwards from $10\ \mu\text{A}$ to $20\ \mu\text{A}$. The point is that we negotiated with the chip lead designer a reduction of the externally provided bias current from $20\ \mu\text{A}$ to $5\ \mu\text{A}$ at the same time. That bias current has to be generated somewhere on the chip as well, so what counts at system level is the sum: previously $10 + 20 = 30\ \mu\text{A}$, now at most $20 + 5 = 25\ \mu\text{A}$. Overall the situation is thus slightly improved, while we have bought ourselves headroom in the OTA budget to spend on gain and settling.

Table 5: Voltage buffer specification

Specification	Basic OTA	5T- OTA	Improved OTA	Unit
Output voltage error	< 3		< 1	%
Total output noise (rms)	< 1		< 0.6	mV_{rms}
Supply current (as low as possible)	< 10		< 20	μA
Turn-on time (settled to within 1%)	< 10		< 1	μs
Externally provided bias current (nominal)	20		5	μA

12 Biasing

So far, we have deferred one unresolved issue. We have studied ways to multiply and scale bias currents using current mirrors (see Section 6) and we have also found ways to buffer (and scale) bias voltages (see Section 8.1, scaling can be readily achieved by using a resistive divider in the feedback path). We can generate bias voltages by running a current through a resistor. However, what has not been discussed so far is **how to generate one stable bias current in the first place**.

If we had a stable reference voltage, then we could use the arrangement shown in Figure 100 to generate a bias current that is given by (note the use of feedback using an error amplifier which could be a simple OTA)

$$I_{\text{bias}} = \frac{V_{\text{ref}}}{R_1}.$$

Using A_1 and M_1 the voltage V_{ref} is regulated across R_1 and available at the drain of M_1 .

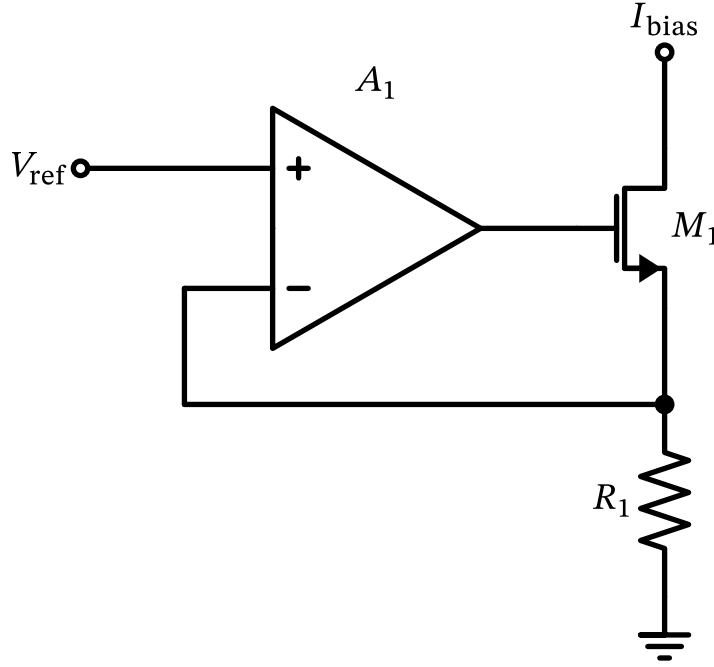


Figure 100: A constant-current generator based on OTA.

The resistor R_1 will show variation with the process tolerance, but we can either (a) use an external resistor for a precise current generation, or (b) use some sort of trimming to correct this resistor value. Depending on the further use of the bias currents a variation of the resistor might not be a bad thing. Assuming we use the resulting bias current to generate somewhere a bias voltage V_{bias} by running the current through resistor R_2 , then this voltage is given by

$$V_{\text{bias}} = R_2 I_{\text{bias}} = \frac{R_2}{R_1} V_{\text{ref}}.$$

We can see in the above equation that the absolute values of R_1 and R_2 do not play a role, only the *ratio* is important. Luckily, components in integrated circuits match very well, so we can multiply and scale one reference voltage V_{ref} across our IC.

Since all components on chip will experience manufacturing tolerances of at least $\pm 10\%$ we strive for something more accurate. We can resort to an off-chip property like an externally provided reference current or voltage, or use the power supply as a voltage reference (often, power supply rails are specified to $\pm 5\ldots 10\%$).

The only option left is to use a material property of the silicon itself for stable reference voltage generation.

12.1 Bandgap Reference

It has been realized that a bipolar junction transistor (BJT) has the wonderful property, that the base-emitter voltage V_{BE} has the following approximate relationship vs. temperature [32]

$$V_{\text{BE}} \approx V_{\text{g0}} \left(1 - \frac{T}{T_0} \right) + V_{\text{BE0}} \left(\frac{T}{T_0} \right) \quad (46)$$

where $V_{g0} = 1.205$ V is the bandgap voltage of silicon *extrapolated* to 0 K and V_{BE0} is the base-emitter voltage of a BJT at reference temperature T_0 . (Note that this is not the physical bandgap of silicon at 0 K, which is about 1.17 eV; V_{g0} is the value obtained by extrapolating the nearly linear $V_{BE}(T)$ characteristic back to $T = 0$ K.) Further, the difference in V_{BE} of two BJT operated at different emitter current densities J_1 and J_2 is given as

$$\Delta V_{BE} = \frac{kT}{q} \ln\left(\frac{J_1}{J_2}\right) \quad (47)$$

with k the Boltzmann constant, and q the elementary charge.

Adding Equation 46 and a scaled version of Equation 47 results in a reference voltage of value

$$V_{ref} = V_{g0} \left(1 - \frac{T}{T_0}\right) + V_{BE0} \left(\frac{T}{T_0}\right) + K \frac{kT}{q} \ln\left(\frac{J_1}{J_2}\right) \quad (48)$$

where K is a scaling factor that we are free to choose in the circuit implementation (we will see below that it is realized as a resistor ratio). Demanding zero temperature coefficient, $\partial V_{ref}/\partial T = 0$, fixes it to

$$K \frac{k}{q} \ln\left(\frac{J_1}{J_2}\right) = \frac{V_{g0} - V_{BE0}}{T_0}. \quad (49)$$

Substituting Equation 49 back into Equation 48 makes every term proportional to T cancel, and only

$$V_{ref} = V_{g0} \quad (50)$$

remains. We thus have created an on-chip reference (called the *bandgap voltage reference*) which is almost independent of manufacturing tolerances with a very small temperature coefficient. Of course, this is only true neglecting second-order effects, but nevertheless, reference accuracies of $\pm 1...3\%$ without trimming are perfectly possible.

The original implementation in [32] uses NPN transistors. The question is, where do we find BJT in a CMOS process? Luckily, when looking at the typical implementations, we find that there is a layer sandwich of P-N-P available. While the PNPs constructed parasitically out of these available layers are available for free without extra processing cost, they are very slow, show unusually small $\beta < 10$, and the collector is tied to V_{SS} as it is the substrate. Still, for bandgap references, they are very useful.

A simple implementation of a bandgap reference circuit is shown in Figure 101. If we scale R_1 and R_2 correctly then we can achieve Equation 50. Note that the output voltage is ca. 1.2 V, so operating this circuit on low supply voltages will be problematic.

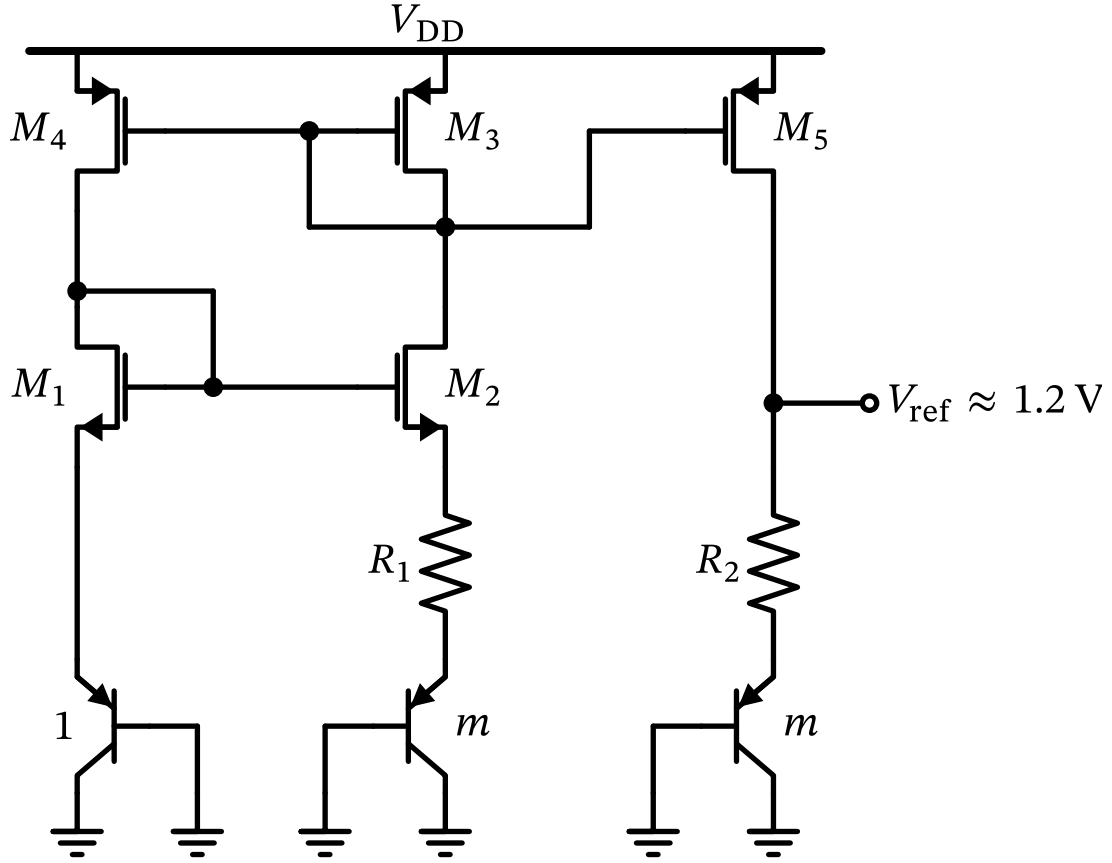


Figure 101: A simple bandgap reference.

M_1 to M_4 are scaled in a way that in both branches the same bias current is flowing. Further, M_1 and M_2 ensure that there is the same potential at their sources. Since the two PNP are scaled by the factor m , they are operated at different current densities despite carrying the same current, and consequently the following voltage develops across R_1 :

$$\Delta V_{BE} = \frac{kT}{q} \ln m$$

Hence, the bias current in all the branches is given by

$$I_{\text{bias}} = \frac{\Delta V_{BE}}{R_1} = \frac{1}{R_1} \frac{kT}{q} \ln m. \quad (51)$$

Inspecting Equation 51 we see that $I_{\text{bias}} = k_1 T$ is a linear function of temperature T , a property that is very useful and called **PTAT** (proportional to absolute temperature). Strictly, this holds only insofar as R_1 itself is temperature-independent; a real resistor has a noticeable temperature coefficient (see Table 1), which is one reason why the resistor type matters in a bandgap design. With M_5 we mirror this bias current into the output branch, and the output voltage V_{ref} is then given by

$$V_{\text{ref}} = V_{BE} + \frac{R_2}{R_1} \frac{kT}{q} \ln m.$$

Comparing with Equation 48 we see that the scaling factor K is realized here as the resistor ratio R_2/R_1 . By proper selection of R_1 , R_2 and m we can thus satisfy Equation 49 and arrive at Equation 50.

i Improved Bandgap Reference

For an improved implementation of Figure 101, the current mirrors should be cascoded, and a startup circuit should be included to guarantee proper operation after enabling it. Further, Equation 46 and Equation 47 build on the relationship $I_C = f(V_{BE})$, while we control I_E in this circuit. If β is large then $I_C \approx I_E$, but this is not the case for the used PNPs.

Many more different bandgap architectures exist, with the Kuijk [33] or the Brokaw [34] types being popular choices.

The circuit of Figure 101 has been implemented in Xschem and is shown in Figure 102. The current sources have been improved by using cascodes. We are using the low-voltage current mirror type already introduced in Section 11. The bias voltages for the cascodes are generated via the voltage drops of R_3 and R_4 , respectively.

No base current compensation for the BJTs is implemented, as it is assumed that the β of the PNP are similar although they are operated at different emitter current densities.

Note the addition of a startup branch with M_{startup} which is inactive during normal operation but will inject a startup current if no proper bias point has yet been found.

There is no circuitry added for enabling/disabling the circuit, which would also be needed for a practical implementation. As usual, the MOSFET sizing has been done in this notebook.

The resistors R_{1-4} have been implemented out of unit elements of ca. $5\text{ k}\Omega$ for optimum matching. Building a bandgap for the first time on silicon likely will show a slightly deviating temperature coefficient, which is why we keep a few dummy resistors around in R_2 to compensate the TC in a redesign.

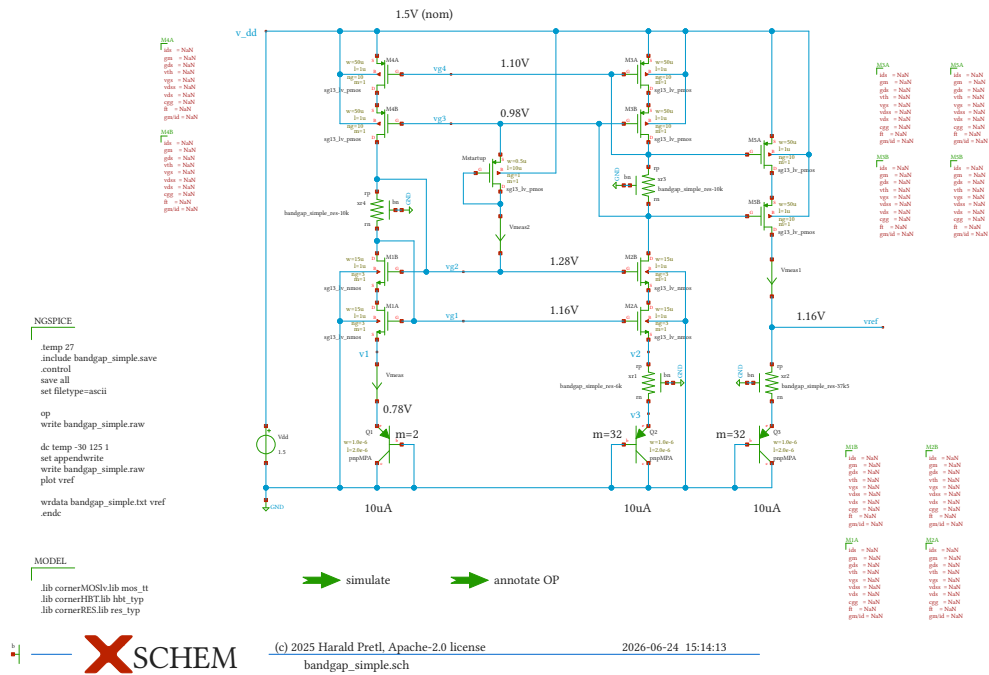


Figure 102: Simple bandgap reference circuit in Xschem.

The Xschem schematic is available [here](#) and the simulated reference voltage vs. temperature is shown in Figure 103. For a typical process we achieve a spread of the reference voltage of about $\pm 0.16\%$ over the simulated temperature range of -30 degC to 125 degC , which corresponds to an average temperature coefficient of ca. 20 ppm/K (the ppm/K figure is the one you will usually find in a datasheet).

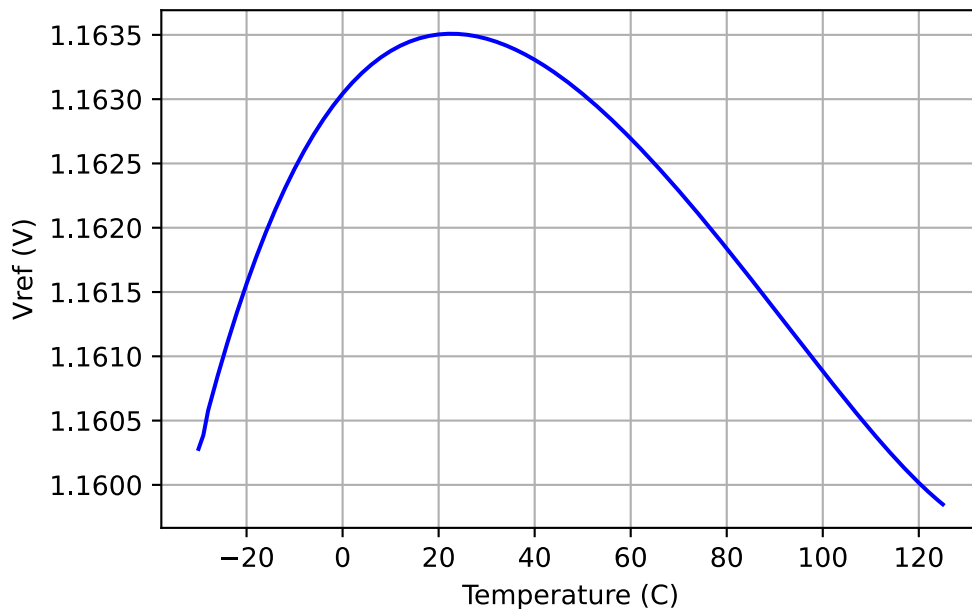


Figure 103: Reference voltage from simulated bandgap circuit.

Please note how tight the dc operating point is in this design to keep all MOSFET saturated. We only use 100 mV nominally as headroom. The circuit in Figure 102 works only marginally

at $V_{DD} = 1.5\text{ V}$, but would not work at 1.2 V or lower. Improved circuit architectures for $< 1\text{ V}$ operation exist; see [35] or [36].

12.2 Banba Bandgap Reference

The Banba reference [35] is quite a bit trickier to design than the classical bandgap shown in Figure 101. It requires the use of an error amplifier; luckily, we can use the 5T-OTA which we designed in Section 8. Since a loop is involved the startup of this circuit is not easy and requires the use of a transient simulation and a proper pre-charge of critical nodes. We can use the ngspice scripting language to (a) set the temperature for a sweep, (b) run a transient simulation, and (c) capture the final reference voltage and save it.

A first design has been implemented and is shown in Figure 104, and the testbench is shown in Figure 105. The supply voltage (which could be lower than 1.5 V) is limited by our OTA design; however, it works well at $V_{DD} = 1.5\text{ V}$. The simulated reference voltage (which is scaled to roughly $V_{\text{bandgap}}/2$) is shown in Figure 106.

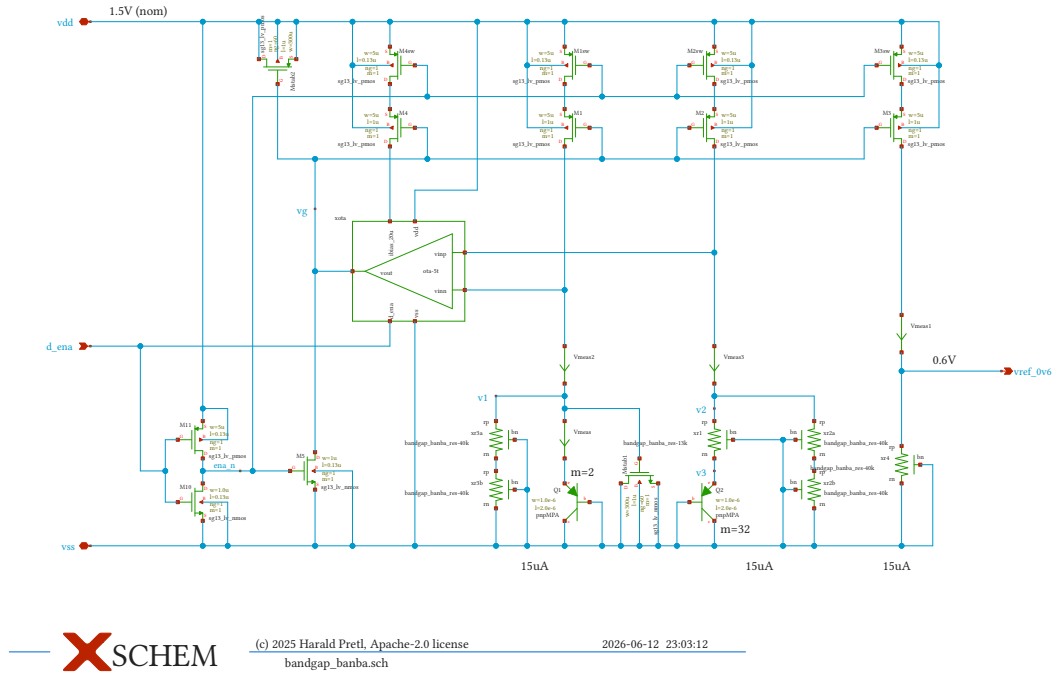


Figure 104: Banba bandgap reference circuit in Xschem.

Note the self-biasing of the OTA with the current generated in the reference branches. The feedback loop needs capacitors for stabilization, and we use area-efficient MOSFET for this task. For a detailed explanation of this circuit please refer to [35], but in brief, the operation is as follows:

The CTAT and PTAT currents required for compensating each other's TCs are built using a ΔV_{BE} cell (given the PTAT current) with parallel resistors (providing the CTAT current). Voltages are sensed using an error amplifier and current sources are controlled to achieve matching currents in both branches. This current can then also be mirrored to flow through another resistor which can be scaled to produce the output voltage.

In comparison to the classical bandgap reference shown in Figure 101 (where the developed currents in all branches are PTAT) the currents developed in the Banba reference are constant vs. temperature.

The minimum supply voltage for the Banba reference is the V_{BE} of the PNP plus the saturation voltage of one MOSFET current source, so ca. $V_{DDmin} \geq 0.8\text{ V} + 0.2\text{ V} \approx 1\text{ V}$. Of course we also need to design an OTA which can work at this low supply.

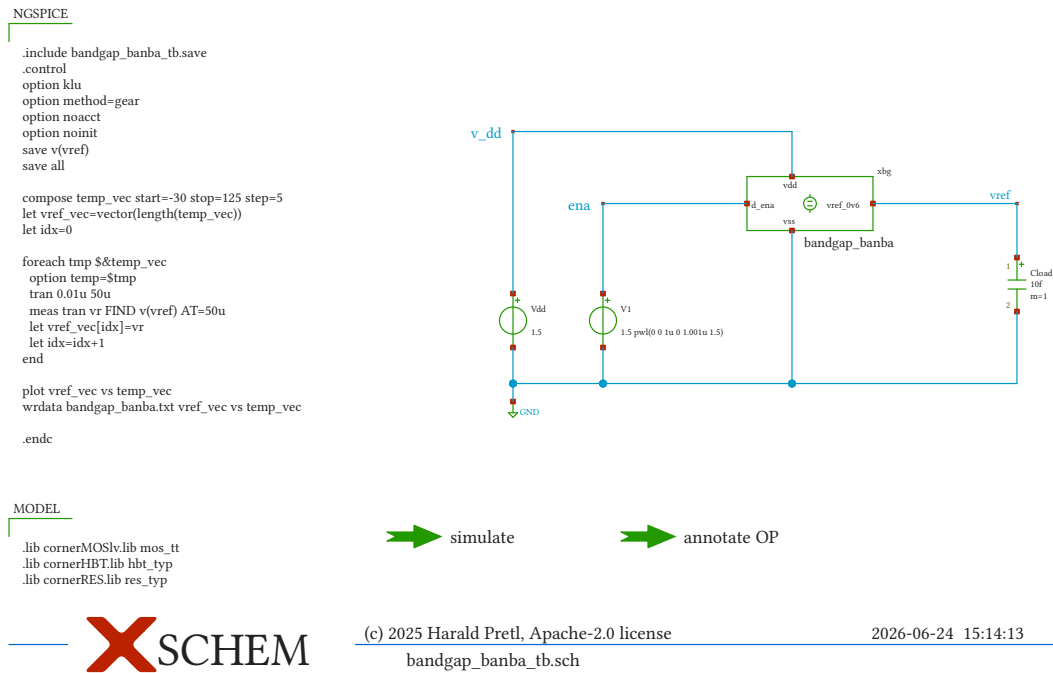


Figure 105: Banba bandgap testbench Xschem.

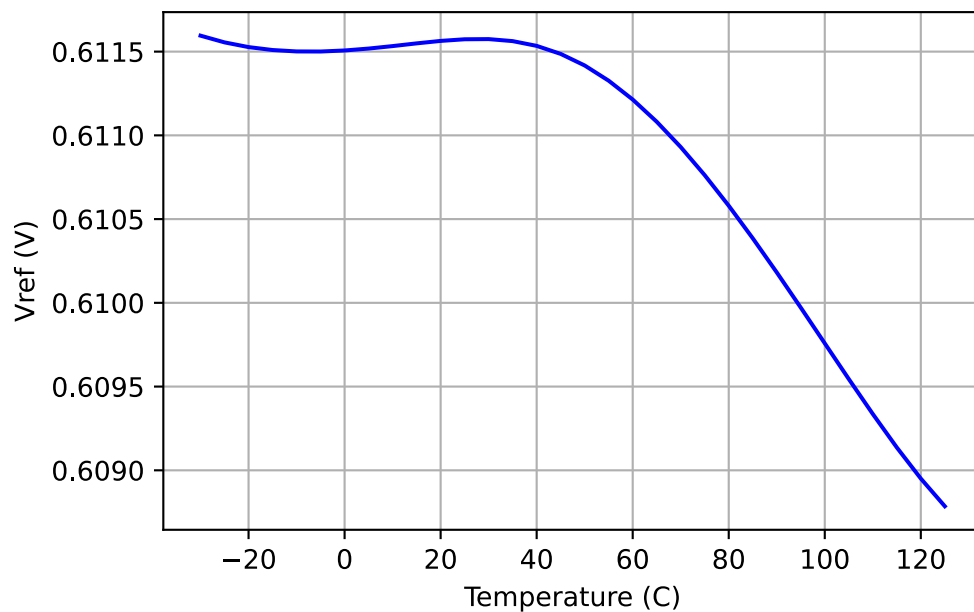


Figure 106: Reference voltage from simulated Banba bandgap circuit.

A well described design of a Banba bandgap reference (including a two-stage OTA and a regulated cascode for the output current mirror), covering much more details than discussed here, can be found in [37].

💡 Exercise: Improved Low-Voltage Bandgap

As an *optional* exercise for advanced users: Design a bandgap circuit following [37]. Implement the shown two-stage OTA and the regulated cascode.

As a starting point, the design of Section 12.2 can be used. As this design will contain more blocks, please build up a hierarchical design, with the OTAs designed in separate subcircuits.

13 Differential OTAs

So far, we have discussed the implementation of OTAs with a differential input and a single-ended output. Often, in integrated circuits, we want to implement fully differential signal chains, as this allows an almost-rail-to-rail swing around a common-mode voltage. Further, noise pickup due to limited power-supply rejection ratio (PSRR) or coupling into the differential signal routing can be suppressed by designing amplifiers with high common-mode rejection ratio (CMRR).

The OTA presented in Section 8.8 can be readily adapted for differential output. Striving for maximum utility, we are discussing a popular two-stage differential-output OTA with a special kind of load, shown in Figure 107.

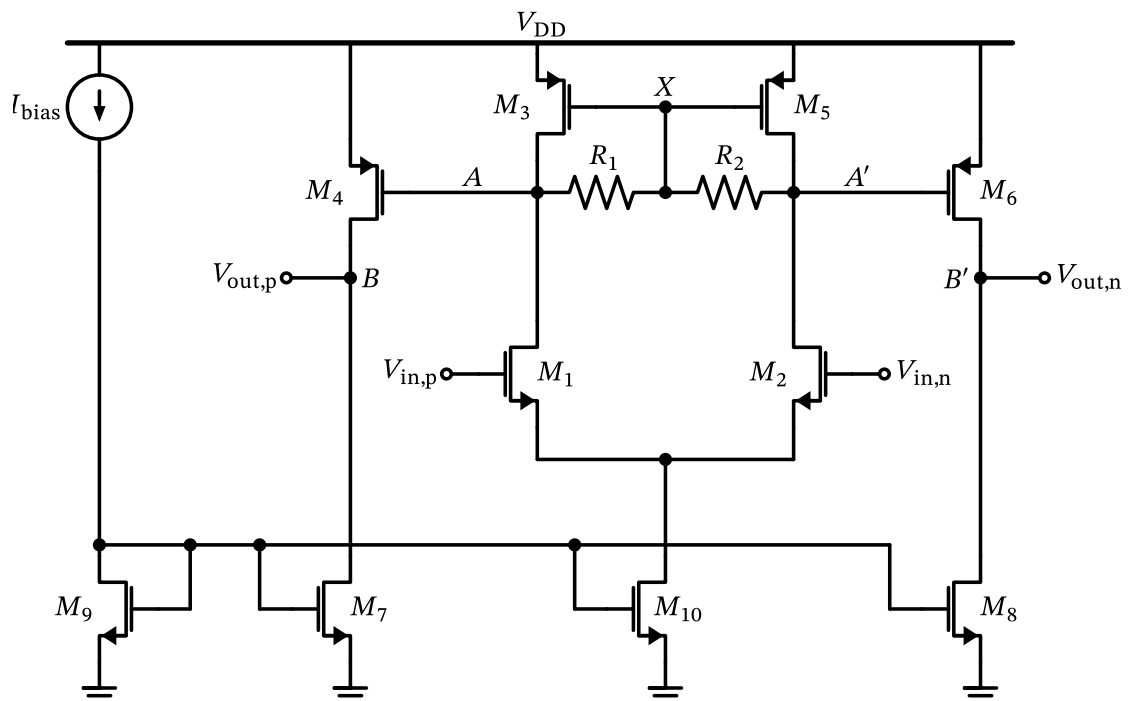


Figure 107: Differential two-stage OTA with resistive load.

This OTA shows a load on top of the differential pair that we have not yet studied. It is instructive to analyze this structure in terms of differential and common-mode operation.

For common-mode operation (i.e., injecting the same current into the drain of M_3 and M_4) we have the same voltage at the drains of $M_{3,5}$, thus $V_{DS3} = V_{DS5}$. We have thus no current flowing through $R_{1,2}$ and as a result $V_{DS3} = V_{DS5} = V_X = V_{GS3} = V_{GS5} = V_{GS3,5}$. We realize that M_3 and M_5 are diode-connected for common-mode operation. We thus have well-defined dc operating points, and also low common-mode gain, since each side of the circuit is then loaded by its own diode-connected transistor, i.e. the common-mode load per half circuit is $g_{m3,5}^{-1}$ (no current flows through $R_{1,2}$, so the resistors play no role here).

For pure differential operation, the mid-point X of $R_{1,2}$ acts as a virtual ground. The bias voltage $V_{GS3,5}$ is thus not changed (it is set only by the common-mode operation) and thus M_3 and M_5 operate as current sources. The differential load impedance is high and is given by $R_{load} = (R_1 + R_2) \parallel (g_{ds3}^{-1} + g_{ds5}^{-1})$.

In addition, we realize that $V_{GS4} = V_{GS3} = V_{GS5} = V_{GS6}$ for common-mode operation, hence the quiescent current of $M_{4,6}$ is set in a current-mirror-like fashion by the diode-connected $M_{3,5}$.

For differential operation, the differential pair of $M_{1,2}$ is loaded by R_{load} and provides fairly high gain. The second gain stage is formed by current-source-loaded common-source stages $M_{4,6}$ and provides additional gain (of course, this is a function of the load impedance).

As soon as we implement a two-stage amplifier we need to look into stability. We likely have more than two poles, and in the case of the amplifier in Figure 107 we have a low-frequency pole at the drains of $M_{1,3}$ and $M_{2,5}$ and a further low-frequency pole at the output. Any additional pole will add further phase shift making stability critical. We now need a method to stabilize this amplifier and thus we will look into *Miller compensation*.

Of course, loop gain analysis of differential OTAs can and should be carried out. Exemplary testbenches where the loop gain is simulated with Middlebrook's and Tian's method can be found for the 5T-OTA and for the improved OTA; the same approach carries over to the differential case, where the loop has to be broken in both the differential and the common-mode path.

13.1 Miller Compensation

A popular way to stabilize a multi-pole feedback-system is to make one pole dominant, and try to shift the other poles to sufficiently high frequencies [38], that we have enough phase margin in the closed-loop system. We may strive for 60° as this will only cause a minor peaking in the frequency response [1].

The question now is where to implement this dominant pole. In order to create a low-frequency pole we need a high-impedance point and a large capacitance. Placing just a large capacitor is unwelcome, as this causes large area consumption on chip.

Luckily, we know from the analysis in Section 17.1 that we can use voltage gain to increase the apparent value of a capacitor by feedback. Inspecting our circuit in Figure 107 we see that we have voltage gain from node A to node B and node A' and B' , respectively. This means we have an opportunity to strap a capacitor between those nodes, and create a dominant pole at node A (and A').

We can now add these so-called “Miller capacitors” to our circuit. The result is shown in Figure 108. (We have also added resistors in series with the capacitors; we ignore these resistors for the time being).

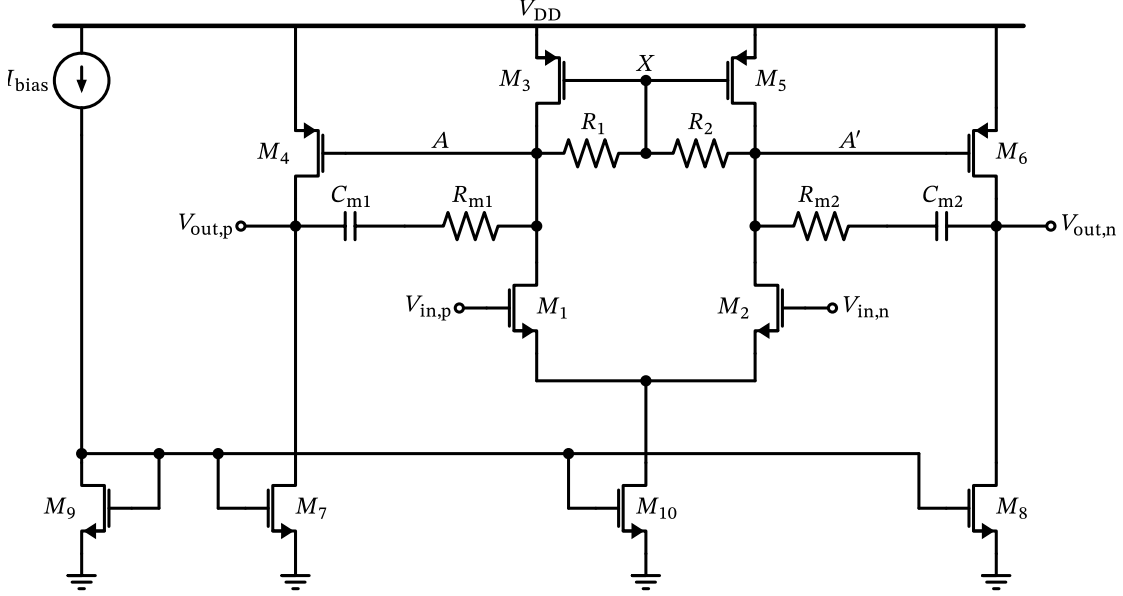


Figure 108: Differential two-stage OTA with resistive load and Miller compensation.

It is instructive to look at the small-signal equivalent circuit of the common-source stage M_4 loaded by current-source M_7 . The resulting model is shown in Figure 109 (we are ignoring the bulk effect of M_4 , and lump components of $M_{4,7}$ into the input and the output impedances formed by C_L , C_{in} , g_{in} and g_{out}).

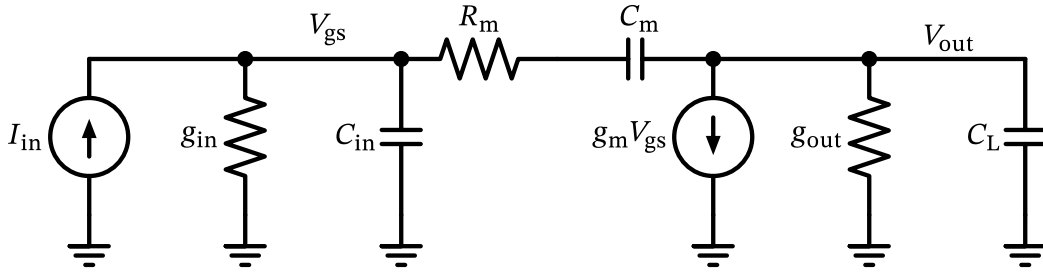


Figure 109: Small-signal model of common-source stage with Miller compensation.

In order to analyze the transfer function and thus the poles and zeros of this configuration we formulate KCL at the input and output node and the current through C_m (we set $R_m = 0$ for now):

$$I_{in} + I_m - V_{gs}(sC_{in} + g_{in}) = 0 \quad (52)$$

$$-I_m - g_m V_{gs} - V_{out}(sC_L + g_{out}) = 0 \quad (53)$$

$$I_m = sC_m(V_{out} - V_{gs}) \quad (54)$$

Using Equation 54 in Equation 52 and Equation 53 and then calculating the transfer function we arrive at

$$\frac{V_{\text{out}}}{I_{\text{in}}} = \frac{sC_m - g_m}{(sC_m + sC_L + g_{\text{out}})(sC_m + sC_{\text{in}} + g_{\text{in}}) - (sC_m - g_m)sC_m}. \quad (55)$$

In order to check Equation 55 we can set $sC_m = 0$ and see whether we can interpret the result:

$$\frac{V_{\text{out}}}{I_{\text{in}}} = -\frac{g_m}{(sC_L + g_{\text{out}})(sC_{\text{in}} + g_{\text{in}})} = -\frac{g_m}{g_{\text{out}}g_{\text{in}}} \frac{1}{1 + \frac{sC_L}{g_{\text{out}}}} \frac{1}{1 + \frac{sC_{\text{in}}}{g_{\text{in}}}} \quad (56)$$

We find that Equation 56 looks reasonable, as we have the correct dc gain of $-g_m/(g_{\text{out}}g_{\text{in}})$ and two poles, one at the input and one at the output.

We now return to the more interesting case of $sC_m \neq 0$. We use the reasonable assumption that $g_m \gg g_{\text{in},\text{out}}$ to simplify the algebra and result in an interpretable result. After quite a few pages of algebraic manipulations (please try for yourself!) we arrive at

$$\frac{V_{\text{out}}}{I_{\text{in}}} = -\frac{g_m}{g_{\text{out}}g_{\text{in}}} \frac{\left(1 - \frac{sC_m}{g_m}\right)}{\left(1 + s\frac{C_L + C_{\text{in}} + \frac{C_{\text{in}}C_L}{C_m}}{g_m}\right)\left(1 + s\frac{C_m\frac{g_m}{g_{\text{out}}}}{g_{\text{in}}}\right)}. \quad (57)$$

Looking at Equation 57 we can identify important changes compared to Equation 56. We have the intended low-frequency pole s_{p1} at the input where the capacitor C_m is increased by the dc gain of the common-source stage g_m/g_{out} :

$$s_{p1} = -\frac{g_{\text{in}}}{C_m \frac{g_m}{g_{\text{out}}}}$$

We further have a high frequency pole s_{p2} where the pole at the output has been shifted to higher frequencies! This is a very welcome effect called *pole splitting*, and it helps to stabilize the feedback system, as the nondominant (output) pole is shifted out in frequency while the dominant (input) pole is pulled in.

$$s_{p2} = -\frac{g_m}{C_L + C_{\text{in}} + \frac{C_{\text{in}}C_L}{C_m}}$$

Together, the movement of poles s_{p1} and s_{p2} is a great deal in terms of stability. However, not all is rosy, as we have to also look at the numerator of Equation 57. Here we see that a zero s_z has been formed, unfortunately a quite bad one. Calculating its location as

$$s_z = +\frac{g_m}{C_m} \quad (58)$$

we see that it is located in the *right half-plane* of the s -domain. Such a zero, abbreviated as RHPZ, leads to a rise of the magnitude of the transfer function (this is generally not a bad thing), but the phase contribution of this zero is negative. This means that we are losing phase margin, yet we push available gain to higher frequencies; in other words, we are degrading phase- and gain-margin!

A circuit-level interpretation of this effect is that while the Miller capacitor is wanted at the input of the amplifier (i.e., the feedback path), it also allows the input signal to pass to the

output (i.e., the forward path). Since in normal operation the signal is inverted and in feed-forward mode it is not we have this unwanted effect of phase shift. A more detailed analysis of this RHPZ can be found in [39].

Luckily, there are several techniques to break the feed-forward path while keeping the feedback path (e.g., using a source follower to drive the output side of the Miller capacitor). For our purposes, we use a slightly simpler technique of adding a resistor in series to the Miller capacitor (see Figure 108 and Figure 109). By doing this, we can modify the location of this zero, and even push it into the left-half-plane. This is excellent news for stability, as now this zero helps to improve gain- and phase-margin!

Repeating the calculation of the transfer function $V_{\text{out}}/I_{\text{in}}$ including R_m we see that the zero location is changed and can be calculated as (the pole locations are also slightly changed due to the addition of R_m , but we will not discuss the resulting equations here)

$$s_z = \frac{g_m}{C_m(1 - g_m R_m)} \quad (59)$$

If we do not use the resistor (i.e., $R_m = 0$) then Equation 59 collapses to Equation 58. If $g_m R_m < 1$ then the zero stays in the right half-plane; if $g_m R_m > 1$ then the zero moves into the left half-plane (this is what we want). If $g_m R_m = 1$ then we have compensated (i.e., removed) the zero; however, in practice exact compensation is not easy to establish across conditions, so we want to move the zero into the left half-plane. Adding a bit of margin, we want to size

$$R_m > \frac{2}{g_m}.$$

13.2 Common-Mode Regulation

In fully-differential (i.e., differential inputs and outputs) OTAs, we have a new issue concerning common-mode voltage control: Depending on the feedback network around the OTA, we might or might not have a defined dc operating point (common-mode wise). Think of the following scenario: If we implement an integrator with an OTA, then the feedback network from output to input consists of a capacitor. This means that the output of the OTA is loaded very high ohmic, and any small current mismatch between M_4/M_7 or M_6/M_8 (see Figure 108) will cause a strong deviation of the dc operating point at the output!

We cannot accept that the dc operating points in a circuit are ill-defined. We thus need a way to establish the dc operating point. Using the diode-resistive load for the differential pair in Figure 108 the dc operating point there is well-defined by the diode-connected $M_{3,5}$. However, the output stage is different, and we need to add circuitry to also control the dc operating point there.

One well-known way is to sense the common-mode voltage using two resistors (similar to $R_{1,2}$ in Figure 108), and compare this measured common-mode voltage to a reference voltage using an error amplifier. Then the output of the error amplifier controls the common-mode voltage, e.g., by driving the gates of $M_{7,8}$ in Figure 108.

! Differential and Common-Mode Loops

When using an error amplifier to regulate a common-mode point keep in mind that you need to check the differential and common-mode stability of these various loops! This can lead to tricky situations, especially under large-signal excitation where the common-mode sensing might not work as expected!

In order to get a differential circuit stable one often has to make the common-mode loop faster than the differential loops. So simple, high-speed error amplifiers are an advantage.

In summary, stability investigations are critically important for differential circuits, and you should never forget to check for common-mode stability as well!

Instead of a common-mode regulation loop (and all its complications regarding stability) often a common-mode setting is sufficient (after all, a somewhat imprecise setting of the dc points is good enough). A common-mode setting has the advantage that no error amplifier is required. We will also use this approach of a common-mode setting in the adapted differential OTA shown in Figure 110.

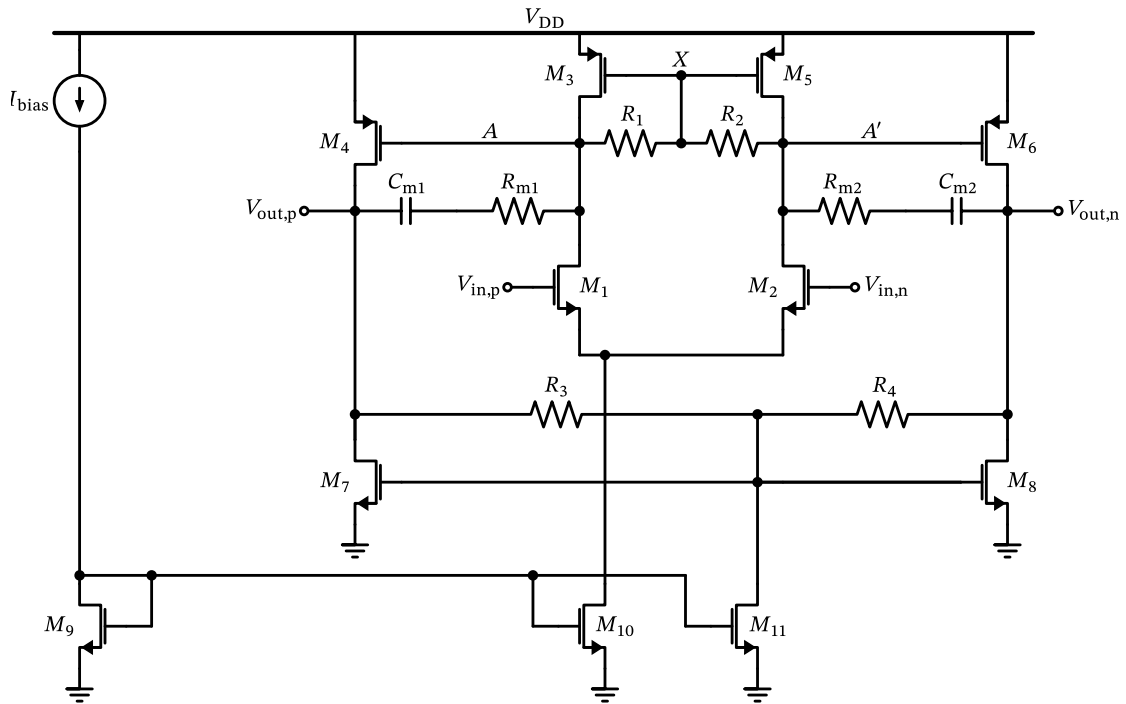


Figure 110: Differential two-stage OTA with resistive load, Miller compensation and output common-mode control.

Resistors $R_{3,4}$ sense the output voltages and create a replica of the common-mode point (assuming $R_3 = R_4$). This common-mode point is connected to the gates of $M_{7,8}$ to essentially connect $M_{7,8}$ like a diode (only for common-mode operation); in differential mode, M_7 and M_8 act as current source, like the load of the differential pair $M_{3,5}$. However, since we want to set the common-mode voltage at the output independently from $V_{GS7,8}$ we also pull a current through $R_{3,4}$ to cause $V_{DS7,8} \neq V_{GS7,8}$; essentially, this is a diode connection including a voltage shift! The output common-mode voltage is then given by

$$V_{\text{out,cm}} = V_{\text{GS7,8}} + \frac{R_{3,4}I_{\text{D11}}}{2}.$$

We can realize the advantage of using the resistor/MOSFET load in the input as well as the output stage when we calculate the common-mode gain of the OTA. We realize that we can use half-circuits due to the inherent symmetry of the circuit in Figure 107. The gain of the first stage (the MOSFET-diode loaded differential pair $M_{1,2}$) is given by (using Equation 13)

$$A_{\text{cm},1} \approx -\frac{1}{g_{\text{m3,5}}} \cdot \frac{g_{\text{m1,2}}g_{\text{ds10}}}{2g_{\text{m1,2}} + g_{\text{ds10}}} \approx -\frac{g_{\text{ds10}}}{2g_{\text{m3,5}}}. \quad (60)$$

The common-mode gain of the second stage is similarly given by

$$A_{\text{cm},2} \approx -\frac{g_{\text{m4,6}}}{g_{\text{m7,8}}}. \quad (61)$$

Combining Equation 60 and Equation 61 we arrive at (assuming that $g_{\text{m3,5}} \approx g_{\text{m4,6}}$)

$$A_{\text{cm}} = A_{\text{cm},1} \cdot A_{\text{cm},2} \approx \frac{g_{\text{ds10}}}{2g_{\text{m7,8}}} \quad (62)$$

which is a low common-mode gain with very likely $A_{\text{cm}} < 1$, which is very good news for the common-mode stability!

Likewise, we can compute the differential gain of the OTA by formulating the voltage gain of the first stage as

$$A_{\text{d},1} \approx \frac{g_{\text{m1,2}}}{R_{1,2}^{-1} + g_{\text{ds3,5}} + g_{\text{ds1,2}}} \quad (63)$$

and the differential voltage gain of the second stage as

$$A_{\text{d},2} = \frac{g_{\text{m4,6}}}{R_{3,4}^{-1} + g_{\text{ds7,8}} + g_{\text{ds4,6}}}. \quad (64)$$

Combining Equation 63 and Equation 64, we arrive at the total differential voltage gain (of an **unloaded** OTA) of

$$A_{\text{d}} = A_{\text{d},1}A_{\text{d},2} = \frac{g_{\text{m1,2}}g_{\text{m4,6}}}{(R_{1,2}^{-1} + g_{\text{ds3,5}} + g_{\text{ds1,2}})(R_{3,4}^{-1} + g_{\text{ds7,8}} + g_{\text{ds4,6}})} \quad (65)$$

which can lead to significant differential voltage gain, ultimately limited by the g_{ds} of the MOSFETs M_{1-8} .

Modify Bias Points with Currents

Keep the technique shown in Figure 110 (using $R_{3,4}$ and M_{11}) in mind: You can always modify a bias point by injecting a dc current into a node, or by pulling a dc current out of a node (or do both to increase or lower the quiescent current through a resistor or transistor)! Since we likely have already current mirrors in the circuit it is usually a minor effort adding MOSFETs to create these bias currents.

13.3 Final Differential OTA

When designing the OTA with the above-mentioned techniques like Miller compensation and the common-mode setting, we find that we have issues with common-mode stability. There is one issue not obvious at first sight with the MOSFET-R load of the first stage: At the node X there is significant capacitance due to the gates of $M_{3,5}$. This capacitance forms a low-pass response with the resistance of $R_{1,2}$ and thus creates a low-frequency pole. This pole is in the common-mode path, and leads to a zero for the common-mode gain.

In other words: At low frequencies, the common-mode gain is given by Equation 62, but at higher frequencies (above the pole at node X) the gates of $M_{3,5}$ can no longer follow the drains, so these transistors stop acting as diodes and behave as current sources instead. The common-mode load of a half circuit consequently increases from $g_{m3,5}^{-1}$ to $R_{1,2} \parallel g_{ds3,5}^{-1}$, and the common-mode gain increases significantly. We need to counteract this effect by adding a capacitor in parallel to $R_{1,2}$, as shown in Figure 111. We use the opportunity to also add a series resistor to this capacitor to introduce an additional zero to improve phase margin.

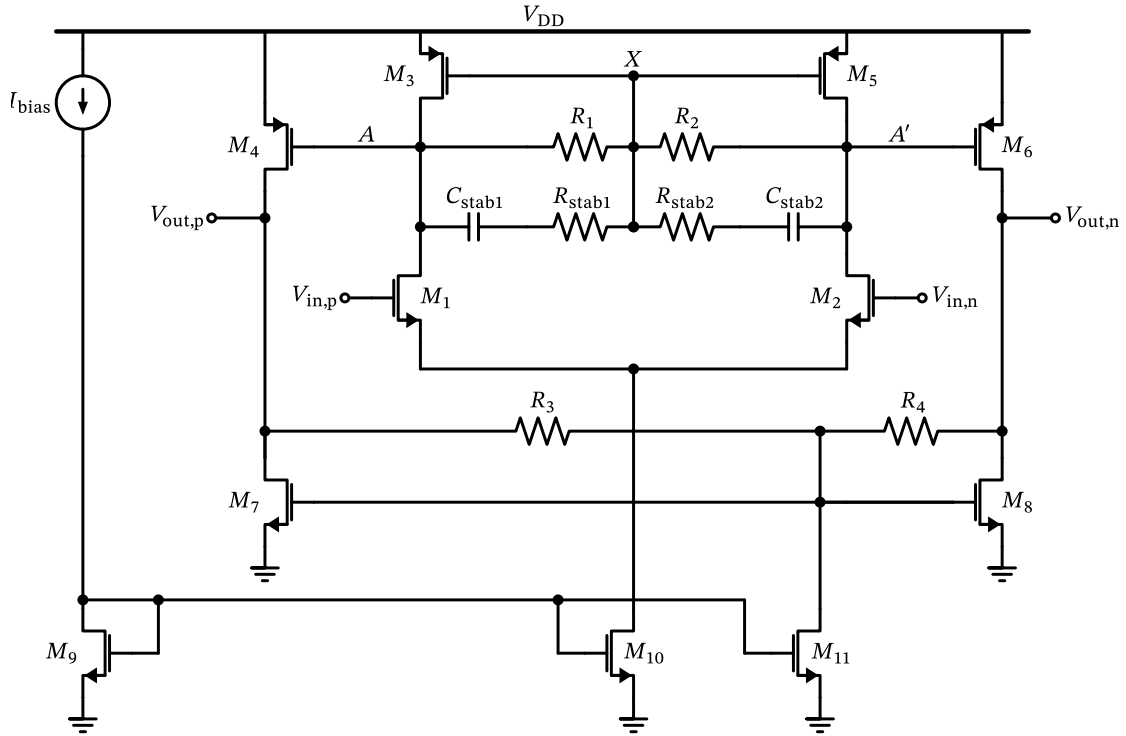


Figure 111: Differential two-stage OTA with adapted MOSFET-R load of first stage and output common-mode control by MOSFET-R load in second stage.

This OTA is sized for a considerably more demanding target than the voltage buffer of Section 8, namely a gain-bandwidth product of $GBW = 1 \text{ GHz}$. You can find the sizing script for the differential OTA here, as well as the circuit-level design in Xschem here. The testbench for differential and common-mode gain analysis can be found here.

The final Xschem schematics of the differential OTA and the testbench are also shown in the figures below.

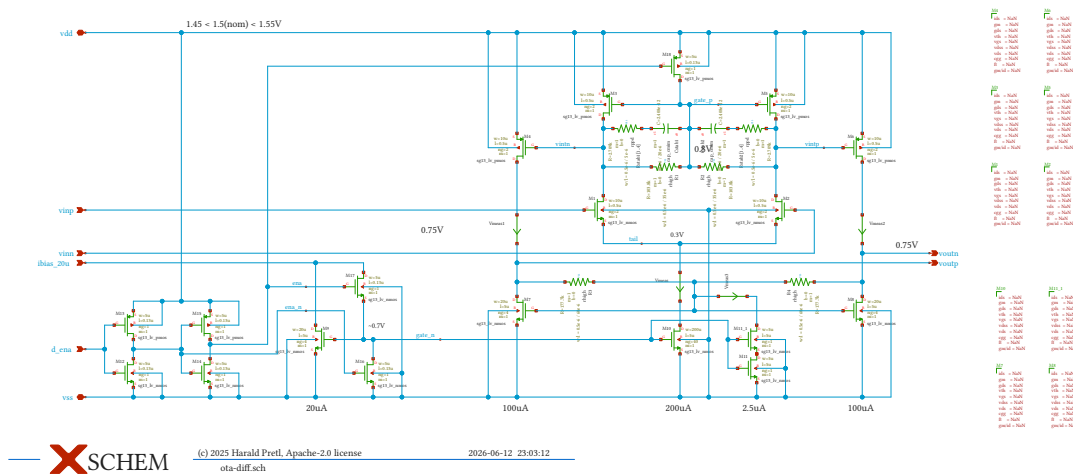


Figure 112: Differential OTA design in Xschem.

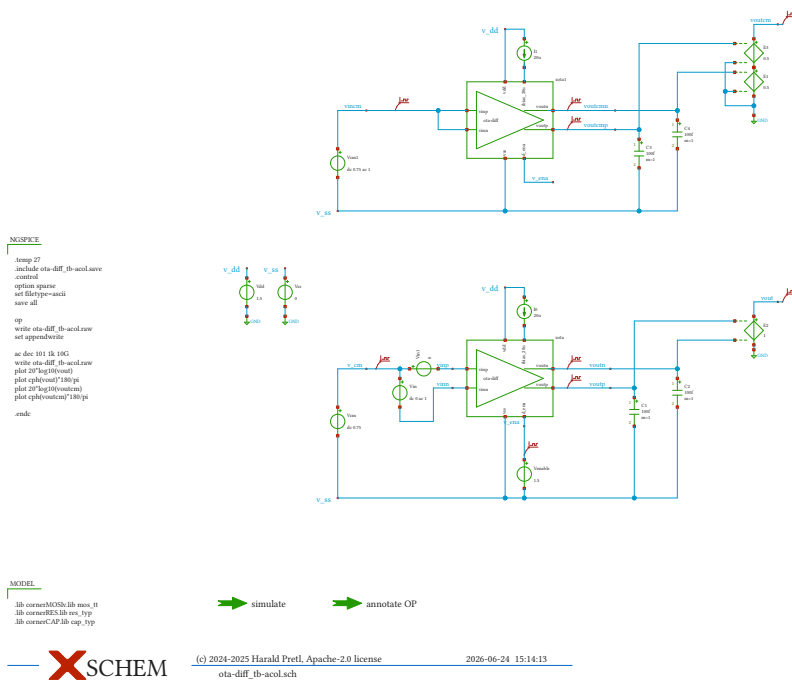


Figure 113: Simulation testbench of the differential OTA design (DM and CM gain analysis).

As you can see when you run the simulation, the differential OTA is stable for differential and common-mode gain. However, the stabilization measures resulted in a GBW that falls considerably short of the target value of 1 GHz. Here we would need to start another round of optimization, either giving up some stability margin, or increasing the power dissipation, or using a more advanced topology.

13.4 Differential OTA Variants

For inspiration we want to discuss two further variants of the differential OTA. The first one is shown in Figure 114 and is a telescopic OTA. The telescopic OTA is a single-stage OTA and is the differential version of the single-ended OTA shown in Figure 76. It shares its advantages and disadvantages: Stability is often not an issue (because it is single-stage), and the current consumption is low, as there is only one main current branch. The biggest disadvantage is the limited output swing, as we have to stack six MOSFETs on top of each other. Accounting for a minimum headroom per transistor of about 0.1 V, we require at least 0.6V, likely more in practice. This might be an issue in low-voltage designs.

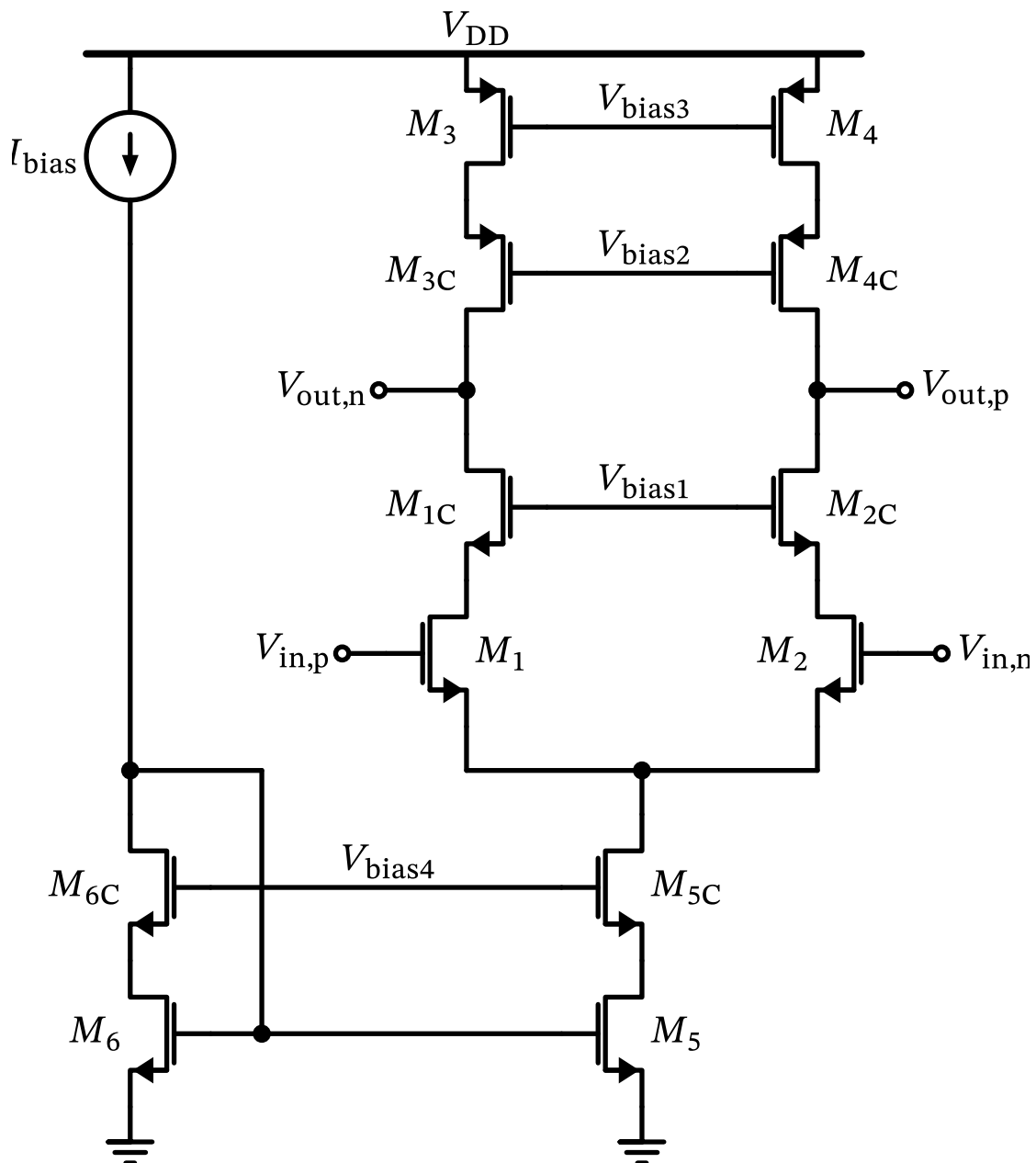


Figure 114: The telescopic differential OTA (output common-mode regulation and biasing details are not shown).

class-A operation. You can design simple amplifiers based on OTA structures. In summary, you are well on your way to becoming a skilled analog or mixed-signal circuit designer!

! Feedback

We hope you have enjoyed these lecture notes! If you have feedback, suggestions, additions, or corrections, please send us an e-mail, create a GitHub issue, or provide a GitHub pull request. Thank you in advance for your contributions!

i Further Reading

For interested circuit designers, Chapter 5 of [13] is recommended as a further read. It explains additional circuits, such as the beta-multiplier reference, an OTA with a telescopic input stage, and a push-pull output stage, designs them with the g_m/I_D methodology, and simulates them in Xschem and with CACE. Hence, the design flow is the same as proposed in this course.

16 Appendix: Middlebrook's Method

If we want to do a closed-loop gain analysis (for stability or other investigations), we have the need to break the loop at one point, apply a stimulus, and monitor the response on the other end. By doing this we want to keep the loading (i.e. the impedance) on both ends similar to the original case. To achieve this, we break the loop at one point by inserting (1) an ac voltage source, and (2) attaching an ac current source, as shown in Figure 116 and Figure 117. The derivation of this approach is presented in [17], and has the big advantage that loading is not changed compared to the closed-loop situation, and the bias points are also unchanged.

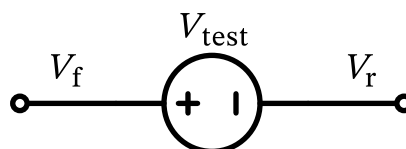


Figure 116: Middlebrook voltage loop gain simulation.

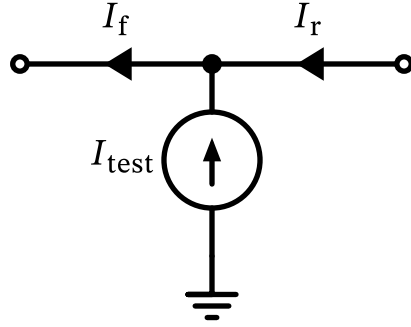


Figure 117: Middlebrook current loop gain simulation.

For both cases we do an ac analysis, and find the corresponding transfer functions T_v and T_i as

$$T_v = -\frac{V_r}{V_f}$$

and

$$T_i = -\frac{I_r}{I_f}.$$

Then, we can calculate the open-loop transfer function $T(s) = H_{ol}(s)$ as

$$T(s) = \frac{T_v T_i - 1}{T_v + T_i + 2} = \frac{V_r I_r - V_f I_f}{2V_f I_f - V_r I_f - V_f I_r}.$$

The four ac quantities V_f , V_r , I_f , and I_r we can readily find by circuit simulation or calculation.

Please note that Middlebrook's method works well for $|T| \gg 1$, so it will show inaccuracies at the crossover frequency of the open-loop gain at $|T(s)| \approx 1$. An improved method (slightly more complicated) can be found in [18].

17 Appendix: Useful Circuit Theorems

17.1 Miller's Theorem

Using Miller's theorem we can find the equivalent circuit of an impedance connected between two nodes, if we know the transfer function between these nodes. The original situation is shown in Figure 118, and the equivalent circuit is shown in Figure 119.

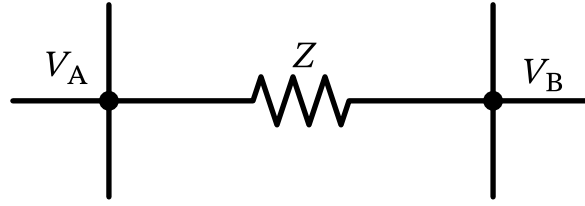


Figure 118: An impedance connected between two nodes A and B.

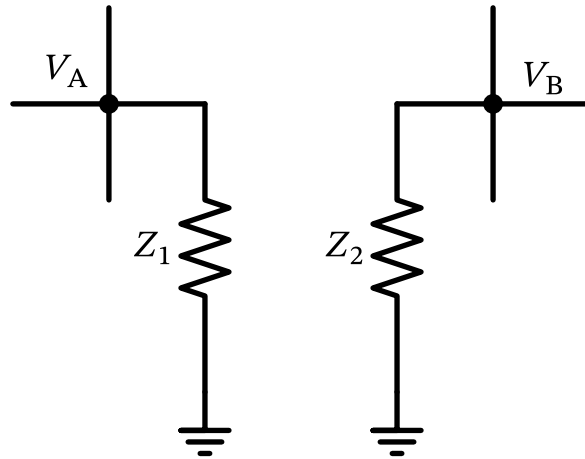


Figure 119: An equivalent circuit using Miller's theorem.

Using Miller's theorem [40] we can calculate

$$Z_1 = \frac{Z}{1 - A} = \frac{Z}{1 - V_B/V_A}$$

and

$$Z_2 = \frac{Z}{1 - A^{-1}} = \frac{Z}{1 - V_A/V_B}$$

to arrive at an equivalent circuit, given that $A = V_B/V_A$ is the voltage gain between nodes A and B. A derivation of this theorem is relatively straightforward considering the current through Z when looking into the impedance from either node A or node B and calculating an equivalent impedance causing the same current.

Note that if $V_A = V_B$ then there is no current flow through Z , and accordingly the impedances $Z_1 = Z_2 = \infty$.

Miller's theorem can be quite handy when an impedance is strapped between two nodes, and we want to break this connection in a calculation, e.g., considering the effect of C_{GD} in a MOSFET.

i Miller's Secret

Note that Miller's compensation is so much more than just making a big capacitor out of a small one. There are layers upon layers of subtlety, and huge hidden benefits which can be read in [38] and [39].

17.2 Bode's Noise Theorem

The total integrated noise of any (no matter how complicated) RLC network (interpreted as a one-port) is given by

$$\overline{V_n^2} = kT \left(\frac{1}{C_\infty} - \frac{1}{C_0} \right),$$

where C_∞ is the capacitance looking into the network with all resistors and inductors open-circuited, and C_0 is the capacitance looking into the circuit when all inductors and resistors are shorted [41].

Reference [41] is an excellent read deriving Bode's noise theorem from different angles.

18 Appendix: 5T-OTA Small-Signal Output Impedance

This section gives additional details to the analysis presented in Section 8.3. Here we provide the full calculation of the output impedance/conductance of the 5T-OTA for frequencies below the dominant pole, i.e., we neglect any capacitors.

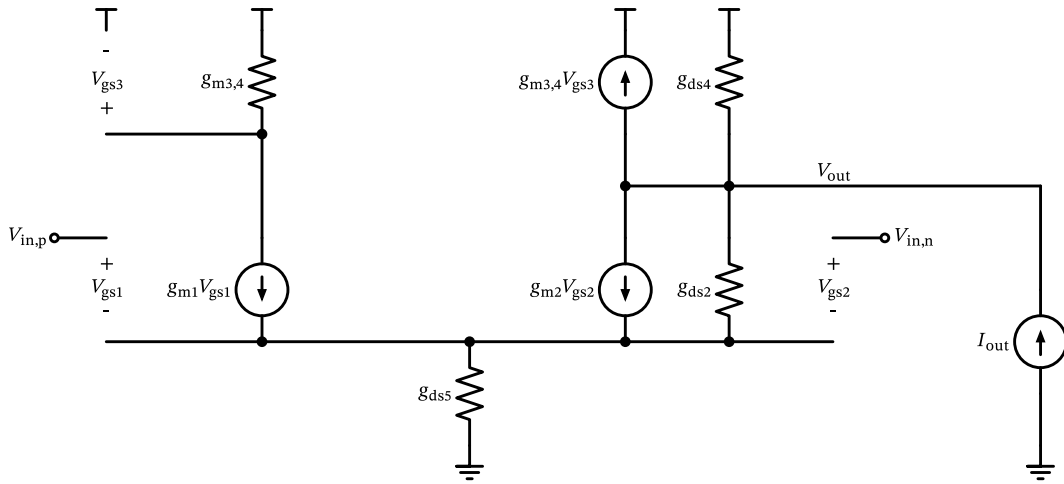


Figure 120: 5-transistor OTA small-signal model for output impedance calculations.

18.1 Open-Loop Configuration

For the open-loop case, the gates of M_1 and M_2 are tied to ground (and since M_1 and M_2 are matched $g_{m1} = g_{m2} = g_{m1,2}$), which means that the gate-source voltages of M_1 and M_2 are identical:

$$V_{in,p} = V_{in,n} = 0 \rightarrow V_{gs1} = V_{gs2} = V_{gs1,2} \quad (66)$$

KCL at the output node:

$$I_{\text{out}} - g_{\text{ds4}} V_{\text{out}} - g_{\text{m3,4}} V_{\text{gs3}} - I_{g_{\text{ds2}}} - g_{\text{m1,2}} V_{\text{gs1,2}} = 0 \quad (67)$$

KCL at the tail node:

$$2g_{\text{m1,2}} V_{\text{gs1,2}} + I_{g_{\text{ds2}}} + g_{\text{ds5}} V_{\text{gs1,2}} = 0$$

We can solve for $I_{g_{\text{ds2}}}$.

$$I_{g_{\text{ds2}}} = -(2g_{\text{m1,2}} + g_{\text{ds5}}) V_{\text{gs1,2}} \quad (68)$$

Furthermore, we need an expression for V_{gs3} . Ohm's law at the transconductance $g_{\text{m3,4}}$ will suffice.

$$V_{\text{gs3}} = -\frac{g_{\text{m1,2}}}{g_{\text{m3,4}}} V_{\text{gs1,2}} \quad (69)$$

KVL from the output node down to ground (traversing g_{ds2} and g_{ds5}) in combination with Equation 68 gives us an expression for $V_{\text{gs1,2}}$

$$V_{\text{gs1,2}} = -\frac{g_{\text{ds2}}}{2g_{\text{m1,2}} + g_{\text{ds2}} + g_{\text{ds5}}} V_{\text{out}} \quad (70)$$

Now, we can plug in all quantities into Equation 67. First, Equation 68 is inserted, which provides an expression for the current through the output conductance g_{ds2} of M_2 :

$$I_{\text{out}} - g_{\text{ds4}} V_{\text{out}} - g_{\text{m3,4}} V_{\text{gs3}} + (g_{\text{m1,2}} + g_{\text{ds5}}) V_{\text{gs1,2}} = 0$$

Second, V_{gs3} is substituted by Equation 69. Since we have assumed a matched pair of transistors for the current mirror comprised of M_3 and M_4 , $g_{\text{m3,4}}$ perfectly cancels out of the equation, and is effectively replaced by the transconductance $g_{\text{m1,2}}$ of the input transistor M_1 :

$$I_{\text{out}} - g_{\text{ds4}} V_{\text{out}} + (2g_{\text{m1,2}} + g_{\text{ds5}}) V_{\text{gs1,2}} = 0$$

Third, Equation 70 gives us an expression for the last remaining unknown $V_{\text{gs1,2}}$. Thus, the factor in front of V_{out} defines the conductance at the output node.

$$I_{\text{out}} - \left[g_{\text{ds4}} + (2 \cdot g_{\text{m1,2}} + g_{\text{ds5}}) \frac{g_{\text{ds2}}}{2g_{\text{m1,2}} + g_{\text{ds2}} + g_{\text{ds5}}} \right] V_{\text{out}} = 0 \quad (71)$$

Before we interpret this result, we slightly rearrange the equation to give us more insight:

$$I_{\text{out}} - \left[g_{\text{ds4}} + \frac{g_{\text{ds2}} \cdot (2 \cdot g_{\text{m1,2}} + g_{\text{ds5}})}{g_{\text{ds2}} + (2 \cdot g_{\text{m1,2}} + g_{\text{ds5}})} \right] V_{\text{out}} = 0 \quad (72)$$

Now, we can identify the common equation of the total resistance of two parallel resistors. However, we are dealing with conductances here, so the same equation describes the total conductance of two conductances in series, while parallel conductances are simply summed. In parallel to g_{ds4} , there is effectively the series connection of g_{ds2} and $2 \cdot g_{\text{m1,2}} + g_{\text{ds5}}$ at work.

If we apply the general assumption of $g_{\text{m}} \gg g_{\text{ds}}$, only the parallel connection of g_{ds4} and g_{ds2} remains:

$$\frac{I_{\text{out}}}{V_{\text{out}}} \approx g_{\text{ds4}} + g_{\text{ds2}} \quad (73)$$

18.2 Closed-Loop Configuration

In contrast to the open-loop case, we keep the gate of M_1 connected to ground and tie the input of M_2 to the output node V_{out} :

$$V_{\text{in},n} = V_{\text{out}} \quad \text{and} \quad V_{\text{in},p} = 0 \quad (74)$$

KCL at the output node:

$$I_{\text{out}} - g_{\text{ds4}} V_{\text{out}} - g_{\text{m3},4} V_{\text{gs3}} - g_{\text{ds2}} V_{\text{gs2}} - g_{\text{m1},2} V_{\text{gs2}} = 0 \quad (75)$$

We use KVL from the output node down to ground to find an expression for V_{gs2} .

$$V_{\text{gs2}} = V_{\text{out}} + V_{\text{gs1}} \quad (76)$$

KCL at the tail node:

$$g_{\text{m1},2} V_{\text{gs1}} + g_{\text{m1},2} V_{\text{gs2}} + g_{\text{ds2}} V_{\text{gs2}} + g_{\text{ds5}} V_{\text{gs1}} = 0 \quad (77)$$

Using Equation 76 to substitute V_{gs2} in Equation 77 we find an equation for V_{gs1} :

$$V_{\text{gs1}} = -\frac{g_{\text{m1},2} + g_{\text{ds2}}}{2g_{\text{m1},2} + g_{\text{ds2}} + g_{\text{ds5}}} V_{\text{out}} \quad (78)$$

Again, we derive the output conductance by plugging Equation 76, Equation 69 and Equation 78 step by step into Equation 75. First, we use Equation 76 to eliminate V_{gs2} :

$$I_{\text{out}} - (g_{\text{ds4}} + g_{\text{ds2}} + g_{\text{m1},2}) V_{\text{out}} - g_{\text{m3},4} V_{\text{gs3}} - (g_{\text{ds2}} + g_{\text{m1},2}) V_{\text{gs1}} = 0$$

Second, Equation 69 also holds for the closed-loop case and lets us eliminate V_{gs3} :

$$I_{\text{out}} - (g_{\text{ds4}} + g_{\text{ds2}} + g_{\text{m1},2}) V_{\text{out}} - g_{\text{ds2}} V_{\text{gs1}} = 0$$

Third, we use Equation 78 to eliminate the remaining unknown V_{gs1} :

$$\begin{aligned} & I_{\text{out}} - (g_{\text{ds4}} + g_{\text{ds2}} + g_{\text{m1},2}) V_{\text{out}} \\ & + g_{\text{ds2}} \frac{g_{\text{m1},2} + g_{\text{ds2}}}{2g_{\text{m1},2} + g_{\text{ds2}} + g_{\text{ds5}}} V_{\text{out}} = 0 \end{aligned}$$

A simpler result can be obtained if we neglect g_{ds2} and g_{ds5} in Equation 78 ($g_{\text{m}} \gg g_{\text{ds}}$):

$$I_{\text{out}} - \left(g_{\text{ds4}} + \frac{1}{2} g_{\text{ds2}} + g_{\text{m1},2} \right) V_{\text{out}} \approx 0$$

If we apply $g_{\text{m}} \gg g_{\text{ds}}$ again we arrive at:

$$I_{\text{out}} - g_{\text{m1},2} V_{\text{out}} \approx 0 \rightarrow \frac{I_{\text{out}}}{V_{\text{out}}} \approx g_{\text{m1},2}$$

19 Appendix: Linux Cheatsheet

The most useful commands for the Linux command line are:

- `ls` to list files and directories
- `cd` to change directory (e.g. `cd analog-circuit-design/xschem`)
- `cd ..` to move one directory level up
- `mkdir` to create a new directory (e.g. `mkdir my_directory`)
- `touch` to create an empty file (e.g. `touch file.txt`)
- `rm` to remove files (e.g. `rm file.txt`)
- `rm -r` to remove recursively, for example a directory (e.g. `rm -r my_directory`)
- `cp` to copy files (e.g. `cp file.txt destination`)
- `cp -r` to copy recursively a directory (e.g. `cp -r directory destination`)
- `mv` to rename files (e.g. `mv file.txt new_name.txt`)
- `mv` to move files into other directories (e.g. `mv file.txt directory`)
- `cat` to view the contents of a file (e.g. `cat file.txt`)
- `find` to search for files and directories (e.g. `find /path -name "*.txt"`)
- `nano` to edit file (e.g. `nano file.txt`)
- `Ctrl + C` to forcefully terminate a running process
- `htop` to open the “task manager”

More advanced commands can be found under <https://www.geeksforgeeks.org/linux-commands-cheat-sheet>.

20 Appendix: Xschem Cheatsheet

When opening Xschem, using `Help -> Keys` a pop-up window comes up with many useful shortcuts. The most useful are listed below. A complete reference is available in the Xschem command manual.

20.0.0.1 File operations:

- `Ctrl-o` to open (load) a schematic or symbol
- `Ctrl-Shift-o` to reload the most recent schematic
- `Ctrl-s` to save the current schematic
- `Ctrl-Shift-s` to save the schematic under a new name (save-as)
- `Ctrl-Shift-Alt-s` to save the current view as a symbol
- `Ctrl-n` to clear the schematic (start a new one)
- `Ctrl-Shift-n` to clear the symbol (start a new one)
- `Ctrl-w` to close the current schematic/tab
- `b` to merge another schematic file into the current one
- `Ctrl-q` to exit Xschem

20.0.0.2 Moving around in a schematic:

- `Cursor` keys to pan the view (move around)
- `Space` (drag) or `Ctrl-p` to pan the schematic with the mouse
- `f` full zoom on schematic
- `Shift-z` or scroll-wheel up to zoom in
- `Ctrl-z` or scroll-wheel down to zoom out
- `z` to zoom into a box (rubber-band selection)
- `Ctrl-Shift-f` to zoom-fit the selected elements
- `e` to descend into the schematic of the selected symbol
- `i` to descend into the symbol view of the selected symbol

- **Ctrl-e** or **Backspace** to go back to the parent schematic
- **Alt-e** / **Alt-i** to open the selected schematic/symbol in a new window
- **Ctrl-Left** / **Ctrl-Right** to switch between tabs (tabbed interface)
- **** (backslash) to toggle fullscreen mode
- **%** to toggle the drawing grid on/off

20.0.0.3 Editing schematics:

- **Del** to delete selected elements
- **Ins** to insert an element from the component library
- **Escape** to abort an operation / unselect / redraw
- **u** to undo, **Shift-U** to redo
- **Ctrl-a** to select all
- **Ctrl-c** / **Ctrl-x** / **Ctrl-v** to copy / cut / paste via the clipboard
- **c** to copy the selected objects (in-place duplicate)
- **m** to move the selected objects
- **Shift-M** to move and insert wires between separated pins
- **h** / **v** to constrain a move/copy to horizontal / vertical
- **Shift-R** to rotate the selected objects (90° CCW)
- **Shift-F** to mirror / flip horizontally
- **Shift-V** to mirror / flip vertically
- **q** to edit the properties of the selected object
- **Shift-Q** to edit properties in **vim** (or external editor)
- **Ctrl-Shift-q** to view properties (read-only)
- **t** to place a text label
- **Shift-T** to toggle the **ignore** flag on an instance (excluded from netlist)
- **Ctrl-f** to find/select objects by substring or regular expression
- **Ctrl-#** to rename components with duplicate names (refdes)
- **#** to highlight components with duplicate names
- **Alt-u** to align selected objects to the current grid
- **g** / **Shift-G** to halve / double the snap (grid) factor

20.0.0.4 Wires, nets, and labels:

- **w** to draw a wire
- **Shift-W** to draw a wire and snap to the closest pin or net endpoint
- **l** to draw a line, **r** to draw a rectangle, **p** to draw a polygon
- **&** to join, break, and collapse wires
- **!** to break selected wires at any pin or junction
- **Alt-Shift-l** to add a wire label (**lab_wire.sym**)
- **Alt-l** to add a label pin (**lab_pin.sym**)
- **k** to highlight the selected net
- **Ctrl-k** to unhighlight the selected net
- **Shift-K** to unhighlight all nets
- **Alt-k** to select all nets attached to the selected wire/label/pin
- **j** to print the list of highlighted nets/pins
- **A** to make a symbol from the current schematic (auto-generate symbol)
- **Alt-p** to add a symbol pin
- **Alt-h** to create symbol pins from the schematic pins

20.0.0.5 Viewing and simulating schematics:

- `5` to only view probes
- `Shift-o` to toggle the light/dark color scheme
- `Ctrl-b` to toggle showing text inside symbols
- `Alt-b` to toggle showing symbol details vs. only bounding boxes
- `Shift-A` to toggle netlist display
- `n` to generate a hierarchical netlist
- `Shift-N` to generate a top-level-only netlist
- `Ctrl-Shift-v` to toggle the netlist format (SPICE / VHDL / Verilog)
- `Alt-s` to reload the circuit (e.g. after changes in a subcircuit)
- `s` to run a simulation (asks for confirmation)
- `Alt-g` to send the highlighted nets to the `gaw` waveform viewer
- `a` and `b` to add cursors to an in-circuit simulation graph
- `f` full zoom on the y- or x-axis in an in-circuit simulation graph
- `Shift-*` to print the schematic to PostScript / PDF
- `Ctrl-Shift-*` to export the schematic as XPM / PNG
- `Alt-Shift-*` to export the schematic as SVG

21 Appendix: ngspice Cheatsheet

Here is an unsorted list of useful ngspice settings and commands:

21.1 Commands

- `ac dec|lin points fstart fstop` performs a small-signal ac analysis with either linear or decade sweep
- `dc sourcename vstart vstop vincr [src2 start2 stop2 incr2]` runs a dc-sweep, optionally across two variables
- `display` shows the available data vectors in the current plot
- `echo` can be used to display text, `$variable` or ``${vector}`, can be useful for debugging
- `let name = expr` to create a new vector; `unlet vector` deletes a specified vector; access vector data with ``${vec`
- `linearize vec` linearizes a vector on an equidistant time scale, do this before an FFT; with `set specwindow=windowtype` a proper windowing function can be set
- `meas` can be used for various evaluations of measurement results (see ngspice manual for details)
- `noise v(output <ref>) src (dec|lin) pts fstart fstop` runs a small-signal noise analysis
- `op` calculates the operating point, useful for checking bias points and device parameters
- `plot expr vs scale` to plot something
- `print expr` to print it, use `print all` to print everything
- `remzerovec` can be useful to remove vectors with zero length, which otherwise cause issues when saving or plotting data
- `rusage` plot information about resource usage like memory
- `save all` or `save signal` specifies which data is saved during simulation; this lowers RAM usage during simulation and size of RAW file; do save before the actual simulation statement
- `setplot` show a list of available plots

- `set var = value` to set the value of a variable; use variable with `$var`; `unset var` removes a variable
- `set enable_noisy_r` to enable noise of behavioral resistors; usually, this is a good idea
- `shell cmd` to run a shell command
- `show : param`, like `show : gm` shows the g_m of all devices after running an operating point with `op`
- `spec` plots a spectrum (i.e. frequency domain plot)
- `status` shows the saved parameters and nodes
- `tf` runs a transfer function analysis, returning transfer function, input and output resistance
- `tran tstep tstop <tstart <tmax>>` runs a transient analysis until `tstop`, reporting results with `tstep` step size, starting to plot at `tstart` and performs time steps not larger than `tmax`
- `wrdata` writes data into a file in a tabular ASCII format; easy to further process
- `write` writes simulation data (the saved nodes) into a RAW file; default is binary, can be changed to ASCII with `set filetype=ascii`; with `set appendwrite` data is added to an existing file

21.2 Options

Use `option option=val option=val` to set various options; important ones are:

- `abstol` sets the absolute current error tolerance (default is 1pA)
- `gmin` is the conductance applied at every node for convergence improvement (default is 1e-12); this can be critical for very high impedance circuits
- `klu` sets the KLU matrix solver
- `list` print the summary listing of the input data
- `maxord` sets the numerical order of the integration method (default is 2 for Gear)
- `method` set the numerical integration method to `gear` or `trap` (default is `trap`)
- `node` prints the node table
- `noinit` suppresses printing of the initial transient solution (to quiet the output)
- `nomod` suppresses printing of the model table (to quiet the output)
- `opts` prints the option values
- `temp` sets the simulation temperature
- `reltol` set the relative error tolerance (default is 0.001 = 0.1%)
- `savecurrents` saves the terminal currents of all devices
- `sparse` sets the sparse matrix solver, which can run noise analysis, but is slower than `klu`
- `vntol` sets the absolute voltage error tolerance (default is 1μV)
- `warn` enables the printing of the SOA warning messages

21.3 Convergence Helper

- `option gmin` can be used to increase the conductance applied at every node
- `option method=gear` can lead to improved convergence
- `.nodeset` can be used to specify initial node voltage guesses
- `.ic` can be used to set initial conditions

21.4 Internal Variables

Variables can be set using `set var=value` and accessed with `$var`. Useful internal variables are:

- To set the fontsize of plots, use `xfont_size`

- To append data to an existing RAW file, use `appendwrite=1`
- Get the name of the current plot with `curplot`
- The filetype of the RAW file can be set with `filetype`, either `binary` (default) or `ascii`
- The number of threads can be set with `num_threads`
- The noise PSDs will be given in V^2/Hz or A^2/Hz when setting `sqrnoise=1` (otherwise V/rtHz or A/rtHz)

22 Appendix: Circuit Designer's Etiquette

22.1 Prolog

A consistent naming and schematic drawing style, as well as VHDL/Verilog coding scheme, is a huge help in avoiding errors and increasing productivity. Even if just one person works on a design, the error rate is lowered. If multiple persons work together in a team, a consistent working style is a big help for smooth cooperation without misunderstanding each other's intentions. Consistency also helps to reuse existing blocks. In a well-done design, the documentation is included in the schematic/source code, so there is no searching for a piece of documentation somewhere else (which is often not found anyway).

22.2 Pins

- Name package pins (interfacing with the outside the IC) in **UPPERCASE**, and all internal signals in **lowercase**.
- Supply voltages like VDD/VCC and ground like VSS/GND need to start with either `VDD`, `VCC`, `VSS`, `VEE` or `GND`, plus a suitable suffix. Examples: `VDD1`, `VDD_AMP`, `vdd_lldo_out`, `VSS_ANA` (uppercase means connected to a pin, lowercase means a VDD is created on-chip by, e.g., an LDO).
- Preferred are `VDD/VSS` for CMOS and `VCC/GND` for bipolar circuits. In BiCMOS circuits `VDD/VSS` are preferred, as usually, the digital content is the major part.
- Digital signals in an analog schematic should start with `di_` (for digital input) or `do_` (for digital output). Example: `di_ctrl1`. In the rare case of a bi-directional digital signal `dio_` can be used.
- Name digital signals consistently: `di_pon` is active-high, `di_pon_b` is active-low (`_b` standing for the negating "bar"); as an alternative, this last signal could be named `di_disable`. `di_reset` is an active-high reset, but often a reset is active-low, so it needs to be named `di_reset_b` (an alternative is `di_resetcn`).
- In mixed-voltage designs, it might be useful to append the voltage level of a signal to avoid connecting incompatible inputs and outputs. Example: `do_comp_1v2` or `di_poweron_3v3`.
- Digital buses always have the MSB to the left and LSB to the right. Example: `do_adc[7:0]`.
- Analog signals should start with a `v` for a voltage signal or `i` for a current signal. It is often useful to include a value for bias signals or make the naming meaningful. RF signals, which are often neither voltage nor current signals, start the name with `rf_`. Examples: Signal and pin names like `ibias_30u` (30uA of bias current), `vbg_1v2` (a bandgap voltage of 1.2V), `vin_p`, `v_filt_out_n`, and `rf_lna_i` speak for themselves.
- Appending analog signals with `_i` and `_o` might be useful if a clear direction is obvious in the signal flow. If a signal is bi-directional, it is better to skip `_io`. If using `_p` or `_n` in combination with `_i` or `_o` then use `_pi/_ni` or `_po/_no`.

- Consistently use pin types `input`, `output`, or `inout` to indicate signal flow. Power supply pins are of `inout` type.

22.3 Schematics

- In analog schematics, add a textual note about basic circuit performance. For example, in an amplifier, note things like suitable supply range, typical and w.c. current consumption, gain, GBW, input voltage range, PSRR, and other useful information.
- If a circuit has a quirk or is particularly clever, add a note on how it works, so others can understand the function without excessive analysis (reviewing a circuit should not be a brain teaser).
- Use provided borders or drawing templates for schematics, and fill the data in, like circuit designer name, date, change history, project name, etc.
- Use a versioning system for your data, and check in often. This avoids data loss, and going back to an earlier design stage is simple. `SVN` is often preferable to `GIT` for binary data.
- Draw uncluttered clear circuits. Ideally, the circuit function is apparent by inspection **quickly**. Everyone can obscure an inverter so that it takes 5 minutes to recognize it, but this is not a good design.
- Don't alter the standard grid setting while drawing schematics (also make sure that the pins in your drawn symbols are on the standard grid)! Off-grid schematic elements will haunt you and your colleagues forever!
- Once a schematic is finished, take the time to name component instances properly (you can use speaking names like `Rstab` or simply use `R1`, `R2`, etc.). Use iterated instances to clean up the circuit. Use wire bundles to clean up circuits where useful. A clever technique is to use bundles and iterated instances to efficiently draw large resistor ladders, for example (however, use with care).
- Avoid connection-by-name, as it makes the circuit hard to read. However, there is a fine line to not cluttering circuits. Signals with many connections (`vdd`, `vss`, `pon`, `pon_b`) are often better done with connection-by-name instead of drawing a wire.
- Some tools allow the use of colored wires, which might be used to mark signal paths, bias lines, etc. However, this should not be overdone; use it with care.
- If you add auxiliary elements like current probes, ensure they get proper treatment when creating the netlist for the LVS (some elements should be shorted, and some elements simply taken out). Ideally, only use a single schematic for simulation, LVS, etc. By using tool features this can usually be done, and avoids the need to keep multiple schematics of one block in sync.
- Use annotations in the schematics to (1) denote current levels in branches, (2) denote bias voltage levels, (3) explain the function of logic input signals, and (4) put in logic tables if not obvious.
- Add comments concerning the layout, like matching devices, certain considerations of placement, sensitive nodes, etc.
- Add simple ASCII diagrams for timing signals if useful.
- Name internal signals (signals connected to pins are anyway named like the port) in a meaningful way; this makes tracking signals in simulation or layout much easier (automatic net names like `net0032` are of not much help).
- Properly name instances, not just `I1` or `I2`; better is `amp1`, `inv2`, etc. (a descriptor in a tool output like `I1/I13/I5/net017` is not helpful; compare that to `adc1/bias/bg/vref_int`).

- On check-and-save, never ignore warnings; just fix them! They will annoy you and others forever and might flag critical design flaws.
- Name cells interpretably, ideally making the function clear already by the name. It is often useful to prefix or postfix a cell by the project name and design iteration. Example: In the project `GIGAPROJECT`, the cells which are changed in the second design step are prefixed with `g2_`, like `g2_amp_bias`. Of course, more letters as a project abbreviation are useful if a name collision is likely to happen.
- Cell names in lowercase are a good choice, as otherwise, capitalization leads to inconsistency in cell names. Use `_` to break words instead of `CamelCase`, like `amp_bias_startup`.
- When building a design, start with the hierarchy first; plan a suitable design structure, and define all interfaces. Implement simple behavioral models for every circuit block (either with controlled sources or using Verilog-A or VHDL/Verilog digital models). In this way, you can simulate the overall design early and find issues in the hierarchy or the interconnects. Then, populate the hierarchy with the detailed circuit designs in the leaf cells. At each point in the design process, you have a design that can be simulated, with some blocks as behavioral models and some blocks already designed. Try to avoid scattered circuit elements (digital or analog) in the hierarchy; it is better to push all components into the leaf cells.
- Avoid huge schematics, better break them down into smaller, maintainable, and self-contained blocks, and provide a simulation test bench for these simple blocks. In this way, later re-simulation across the hierarchy is easily possible.
- When building up the hierarchy, choose pin names and signal names as consistently as possible. Example: use the signal name `vref_int` when connecting two leaf cells with the pin names `vref_int_o` and `vref_int_i`.
- Avoid the excessive use of net breakers like small resistors, as they inhibit net tracing and can lead to simulation convergence issues. If a net breaker is needed (or a current should be probed) use a 0V dc voltage source.

22.4 Symbols

- Spend time drawing nice symbols! Ideally, the underlying circuit functionality is apparent by just looking at the symbol.
- Arrange the pins in a meaningful way.
- Group pins that belong together. An often useful arrangement is to locate the inputs on the left side, outputs on the right, digital control inputs at the bottom, and supplies at the top.
- Make the origin of a symbol in the top-left corner. In this way, symbols can be changed more easily, for example, by swapping out different versions of blocks.
- The cell name (and potentially library name) should be visible in the symbol, not only in the properties.

22.5 Design Robustness

- It is good practice to buffer incoming digital signals with a local inverter (connected to the local block supply) before connecting it to internal nodes. This improves the slew rate of the control signal and lowers the chance of unwanted cross-talk.
- Consider dummy elements for good matching, and try to make useful unit sizes of components. This will make the layout creation much smoother.

- The golden rule of good analog performance is good matching, and good matching is achieved by identical components (size, orientation, surroundings)! If the layout does not look nice (humans like symmetry), it will not perform well.
- Consider supply decoupling and bias voltage decoupling inside the cells. Often, dummy elements can be used for that. Be aware, however, of unwanted supply resonances (think bond wire L and decoupling C) and slow transients of bias nodes after disturbance.
- Always implement a proper power-down mode. Avoid floating nodes in off-mode. The better defined the on- as well as the off-mode are, the less the chance of leakage currents. Always simulate both modes (on and off), and also simulate a transient power-up of a circuit to identify issues with slow bias start or insufficient turn-off, or nasty feedback loop instabilities during transients.
- When drawing the first schematic, add parasitic capacitances to each node. If all nodes are labeled, a capacitor bank is easily put into one corner of the schematic with parasitic caps tied to the ground. Use 5fF as a starting value (and replace it later with the correct value from parasitic extraction). This accounts for some wiring parasitics in layout and helps to account for these layout impairments early in the design phase and later when simulating the schematic instead of the extracted netlist with parasitics.

22.6 Rules for Good Mixed-Signal and RF Circuits

- Separate analog and digital power supply, connect to package pins with multiple bond wires/bumps, and separate noisy and clean `vdd/vss` from each other!
- Prevent supply loops; keep `vdd` and `vss` lines close to each other (incl. bond wires and PCB traces)! This minimizes L and coupling factor k .
- Some prefer a massive (punched) ground plane, which is possible if you have enough metal levels. With a ground plane, the return path of a signal or supply line is just a few microns away.
- Use chip-internal decoupling capacitors, and decouple bias voltages to the **correct** potential (`vdd` or `vss`, or another node, depending on the circuit)!
- Use substrate contacts and guard rings to lower substrate crosstalk but use a quiet potential for connection; use triple-well if available! Connecting a guard-ring/substrate contact to a noisy supply is a prime noise injector (usually unwanted).
- Physically separate quiet and noisy circuits (at least by the epi thickness)!
- Reduce circuit noise generation as much as possible (avoid switching circuits if possible, use constant-current circuits instead, and use series/shunt regulators for supply isolation).
- Reduce sensitivity of circuits to interference (by using a fully differential design with high PSRR/CMRR, symmetrical layout parasitics, and good matching)!

22.7 VHDL/Verilog Coding Guide

These recommendations are specifically targeted at Verilog; however, they apply similarly to VHDL.

- Use automatic checkers (linters) to see whether your code contains errors or vulnerabilities. Commercial or open-source tools allow this, e.g., Icarus Verilog (`iverilog -g2005 -tnull FILE.v`) or Verilator (`verilator --lint-only -Wall FILE.v`).
- Write readable and maintainable code; use speaking variable names, and use a naming convention for inputs (ending with `_i`) and outputs (ending with `_o`). IO signals are using

`_io`. Active-low signals have an `n` or `b` in their name (coming before the direction), like `reset_ni`. Use comments to explain the intention.

- With a synchronous reset reset-related racing conditions are often avoided. If an asynchronous reset is desirable (which is often the case), ensure the reset signals are free from race conditions.
- Module-local registers and wires could append `_w` (for Verilog `wire`) or `_r` (for Verilog `reg`) to make their function clear. This is not required in SystemVerilog where the unified type `logic` should be used.
- Use an `assign` statement for logic as this often is easier to read than an `always @(*)` block. The ternary operator `COND ? TRUE : FALSE` can help with conditional assignments and is often a better choice than a (nested) `if ... else` statement.
- Declare all outputs explicitly with either `reg` or `wire`.
- Use local parameter definitions with `localparam` in a module to make the code easier to follow. Name parameters in **UPPERCASE**.
- Take care to reset all registers to a defined state (in simulation and HW).
- Use the rule of “one file per module.” The filename shall match the module declaration.
- Use ``default_nettype none` at the beginning of a file containing a module definition. After the module you can use ``default_nettype wire`. This will add a safety net against typos in signal names.
- In a combinational always block, use `always @(*) begin ... end` instead of spelling out the signals in the sensitivity list. Forgetting a signal could lead to serious mismatches between simulation and HW.
- Make your code flexible by making bit widths and other values parameterized using a `localparam` or module parameter.
- Be cautious of implicit type conversions and bit-width adaptations; better make explicit conversions and match bit widths in assignments.
- Use only blocking assignments (`=`) in `always @(*)` blocks, and only non-blocking assignments (`<=`) in clocked `always @(posedge ...)` blocks.
- It is recommended to follow this naming convention for latches and flip-flops: **Synchronous** set and reset should be called `set` (for setting, i.e., `Q=1`) and `res` (for resetting, i.e., `Q=0`). **Asynchronous** set and reset should be called `pre` (for presetting) and `clr` (for clearing). In this way it is immediately clear whether a control input is acting independent of the `clk` (i.e., asynchronous) or dependent on the `clk` (i.e., synchronous).

A comprehensive coding style guide for Verilog/SystemVerilog can be found here, and it is highly recommended to follow it.

22.8 Further Reading

- Good information about drawing schematics, design testbenches, etc: <https://circuit-artists.com>
- Sutherland/Mills, *Verilog and SystemVerilog Gotchas - 101 Common Coding Errors and How to Avoid Them*, Springer, 2010
- B. Razavi, *The Analog Mind*, recurrent column in IEEE Solid-State Circuits Magazine

23 Exemplary Examination Questions

This appendix contains a collection of exemplary examination questions covering the main topics of this course. The questions are organized by topic and include both conceptual understanding and quantitative problem-solving.

23.1 MOSFET Fundamentals

i Question 1.1 – Small-Signal Parameters

Question: Define the two main small-signal parameters of a MOSFET (g_m and g_{ds}) and explain their physical meaning.

Solution:

- **Transconductance** $g_m = \partial I_D / \partial V_{GS}$: Describes how the drain current changes with gate-source voltage. It represents the amplification capability of the transistor.
- **Output conductance** $g_{ds} = \partial I_D / \partial V_{DS} = r_{out}^{-1}$: Describes how the drain current varies with drain-source voltage (ideally zero in saturation, but finite due to channel-length modulation). It limits the maximum achievable voltage gain. In the triode region, g_{ds} is the conductance of the channel (i.e., the channel resistance is $R_{on} = 1/g_{ds}$), which can be electrically controlled by V_{GS} .

i Question 1.2 – Operating Regions

Question: State the conditions for a MOSFET to operate in the triode region versus the saturation region. Why is saturation preferred for analog amplifier design?

Solution:

- **Triode region:** $V_{DS} < V_{ds,sat}$
- **Saturation region:** $V_{DS} \geq V_{ds,sat}$

Saturation is preferred for analog amplifiers because:

1. The drain current is largely independent of V_{DS} , resulting in high output impedance ($r_{out} = 1/g_{ds}$)
2. The transistor acts as a voltage-controlled current source
3. High intrinsic gain (g_m/g_{ds}) can be achieved
4. Linear relationship between small-signal input voltage and output current given by g_m

The triode region is important when operating the MOSFET as a (variable) resistor or switch.

i Question 1.3 – Transit Frequency

Question: Define the transit frequency f_T of a MOSFET. How does it relate to the transistor's speed capability?

Solution:

The transit frequency is defined as:

$$f_T = \frac{g_m}{2\pi C_{gg}} = \frac{g_m}{2\pi(C_{gs} + C_{gd} + C_{gb})}$$

It represents the frequency at which the current gain of the transistor drops to unity. A higher f_T indicates:

- Faster switching capability
- Higher potential bandwidth in amplifier applications
- Better high-frequency performance

The f_T increases with higher g_m (higher bias current or larger W/L) and decreases with larger parasitic capacitances (larger device area).

23.2 gm/ID Sizing Methodology

i Question 2.1 – gm/ID in Different Inversion Regions

Question: Derive the theoretical limits of g_m/I_D in weak inversion (V_{GS} small) and strong inversion (V_{GS} large). What is the typical range of g_m/I_D used in practical analog design?

Solution:

Weak inversion (subthreshold):

$$g_m/I_D = \frac{1}{nV_T}$$

where $n \approx 1.2 - 1.5$ is the subthreshold slope factor and $V_T = kT/q \approx 25.8$ mV at room temperature.

This gives $g_m/I_D \approx 26 - 32$ V⁻¹ as the maximum (for the LV NMOS of SG13G2 the tables yield about 28 V⁻¹, i.e. $n \approx 1.38$).

Strong inversion (square-law approximation):

$$g_m/I_D = \frac{2}{V_{GS} - V_{th}} = \frac{2}{V_{od}}$$

For typical overdrive voltages of 100–300 mV, this gives $g_m/I_D \approx 7 - 20$ V⁻¹.

Practical range: g_m/I_D between 5 and 25 V⁻¹ is commonly used, with:

- High g_m/I_D (15–25 V⁻¹): Low power, but slower and larger area
- Medium g_m/I_D (8–15 V⁻¹): Balanced trade-off
- Low g_m/I_D (5–8 V⁻¹): High speed, but more current and headroom needed

i Question 2.2 – Design Trade-offs

Question: Explain the trade-offs involved when choosing a high versus low g_m/I_D target in transistor sizing.

Solution:

Parameter	High g_m/I_D (>15)	Low g_m/I_D (<8)
Current consumption	Lower (for same g_m)	Higher
Speed (f_T)	Lower	Higher
$V_{ds,sat}$	Lower	Higher (more headroom needed)
Operating region	Weak/moderate inversion	Strong inversion

The choice depends on application requirements:

- For low-power applications: High g_m/I_D
- For high-speed applications: Low g_m/I_D
- For voltage headroom-limited designs: High g_m/I_D (lower $V_{ds,sat}$)

i Question 2.3 – Saturation Voltage

Question: A transistor is sized for $g_m/I_D = 15 \text{ V}^{-1}$. Estimate the minimum V_{DS} required to keep it in saturation.

Solution:

The saturation voltage can be estimated from:

$$V_{ds,sat} \approx \frac{2}{g_m/I_D} = \frac{2}{15} \approx 133 \text{ mV}$$

To ensure safe operation in saturation with some margin, a V_{DS} of at least 150–200 mV should be allocated.

Note: This approximation is based on the strong inversion relationship and provides a reasonable estimate for moderate inversion as well.

23.3 MOSFET Diode

i Question 3.1 – Small-Signal Impedance

Question: Derive the small-signal impedance of a MOSFET diode (gate connected to drain) and identify its frequency behavior.

Solution:

For a MOSFET with gate shorted to drain, applying KCL at the drain node (we only keep g_m , g_{ds} , and C_{gs} from the small-signal model):

$$i_{\text{test}} = g_m v_{gs} + g_{ds} v_{ds} + sC_{gs} v_{gs}$$

Since $v_{gs} = v_{ds} = v_{\text{test}}$:

$$i_{\text{test}} = (g_m + g_{ds} + sC_{gs})v_{\text{test}}$$

Therefore:

$$Z_{\text{diode}}(s) = \frac{v_{\text{test}}}{i_{\text{test}}} = \frac{1}{g_m + g_{ds} + sC_{gs}}$$

At dc: $Z_{\text{diode}} \approx \frac{1}{g_m}$ (since $g_m \gg g_{ds}$)

Corner frequency: $f_c = \frac{g_m + g_{ds}}{2\pi C_{gs}} \approx \frac{g_m}{2\pi C_{gs}} \approx f_T$

The impedance is resistive ($\approx 1/g_m$) at low frequencies and becomes capacitive at (very) high frequencies.

i Question 3.2 – Noise Consideration

Question: What is the output noise voltage (RMS) of a MOSFET diode, and how does it relate to kT/C noise?

Solution:

The integrated output noise of a MOSFET diode follows the kT/C relationship:

$$V_{n,\text{rms}}^2 = \frac{kT\gamma}{C_{gs}}$$

where γ is the thermal noise excess factor (approximately 2/3 for long-channel devices, higher for short-channel).

This is analogous to the kT/C noise of an RC network, with the effective capacitance being C_{gs} . To reduce noise:

- Increase C_{gs} (larger device)
- Note: Bandwidth also decreases with larger C_{gs}

23.4 Current Mirror

i Question 4.1 – Basic Current Mirror

Question: For a basic NMOS current mirror with input transistor M_1 and output transistor M_2 , derive the output current ratio. What are the main sources of error in a practical current mirror?

Solution:

Ideal output current:

$$I_{\text{out}} = I_{\text{ref}} \cdot \frac{(W/L)_2}{(W/L)_1}$$

Main error sources:

1. **Channel-length modulation:** Different V_{DS} on M_1 and M_2 causes current mismatch

$$\frac{\Delta I}{I} \approx \frac{\Delta V_{\text{DS}} \cdot g_{\text{ds}}}{I_{\text{D}}}$$

2. **Threshold voltage mismatch:** Random ΔV_{th} variations

$$\frac{\Delta I}{I} \approx \frac{g_{\text{m}} \cdot \Delta V_{\text{th}}}{I_{\text{D}}} = g_{\text{m}}/I_{\text{D}} \cdot \Delta V_{\text{th}}$$

3. **W/L mismatch:** Lithographic variations in device dimensions during manufacturing
4. **Temperature gradients:** Different operating temperatures for the transistors
5. **Finite output resistance:** Limits the current source quality ($r_{\text{out}} = 1/g_{\text{ds}}$)

i Question 4.2 – Output Resistance

Question: Calculate the output resistance of a simple current mirror. How can it be improved?

Solution:

Simple current mirror: $r_{\text{out}} = r_{\text{ds}} = \frac{1}{g_{\text{ds}}}$

Improvements:

1. **Cascode current mirror:**

$$r_{\text{out}} = r_{\text{ds,casc}} + r_{\text{ds}} \cdot (1 + g_{\text{m,casc}} \cdot r_{\text{ds,casc}}) \approx g_{\text{m,casc}} \cdot r_{\text{ds,casc}} \cdot r_{\text{ds}}$$

2. **Source degeneration:**

$$r_{\text{out}} = r_{\text{ds}} + R_{\text{deg}} \cdot (1 + g_{\text{m}} \cdot r_{\text{ds}}) \approx g_{\text{m}} \cdot r_{\text{ds}} \cdot R_{\text{deg}}$$

3. **Regulated cascode:**

$$r_{\text{out}} \approx r_{\text{ds}} \cdot g_{\text{m,casc}} \cdot r_{\text{ds,casc}} \cdot g_{\text{m,aux}} \cdot r_{\text{ds,aux}}$$

The improvement factor for cascoding is approximately $g_{\text{m}}/g_{\text{ds}}$ (intrinsic gain).

i Question 4.3 – High-Swing Cascode

Question: Explain the principle of a high-swing (low-voltage) cascode current mirror. What is the minimum output voltage for proper operation?

Solution:

In a high-swing cascode, the bias voltage V_{bias} for the cascode transistor is chosen such that both the main transistor and the cascode transistor operate just at the edge of saturation:

$$V_{\text{bias}} = V_{\text{GS[,casc]}} + V_{\text{ds,sat,main}}$$

Minimum output voltage:

$$V_{\text{out,min}} = V_{\text{ds,sat,casc}} + V_{\text{ds,sat,main}} = 2 \cdot V_{\text{ds,sat}}$$

For typical $g_{\text{m}}/I_{\text{D}} = 15 \text{ V}^{-1}$: $V_{\text{out,min}} \approx 2 \times 133 \text{ mV} \approx 270 \text{ mV}$

This is significantly lower than a standard cascode where $V_{\text{out,min}} = V_{\text{GS}} + V_{\text{ds,sat}}$ (typically $>500 \text{ mV}$).

23.5 Differential Pair

i Question 5.1 – Differential vs. Common-Mode

Question: For an ideal differential pair with tail current source I_{tail} , derive the differential-mode and common-mode transconductance.

Solution:

Differential mode: With $v_{\text{in,dm}} = v_{\text{in,p}} - v_{\text{in,n}}$ applied:

- The tail node acts as a virtual ground
- Each transistor sees $v_{\text{gs}} = v_{\text{in,dm}}/2$
- $i_{\text{out}} = g_{\text{m}} \cdot v_{\text{in,dm}}/2 - (-g_{\text{m}} \cdot v_{\text{in,dm}}/2) = g_{\text{m}} \cdot v_{\text{in,dm}}$

$$G_{\text{m,dm}} = g_{\text{m}}$$

Common mode: With $v_{\text{in,cm}}$ applied to both inputs:

- The tail current source presents impedance $r_{\text{tail}} = 1/g_{\text{ds,tail}}$
- Due to source degeneration: $G_{\text{m,cm}} = \frac{g_{\text{m}}}{1+2 \cdot g_{\text{m}} \cdot r_{\text{tail}}} \approx \frac{1}{2 \cdot r_{\text{tail}}}$

Common-mode rejection ratio (CMRR):

$$\text{CMRR} = \frac{G_{\text{m,dm}}}{G_{\text{m,cm}}} = 2 \cdot g_{\text{m}} \cdot r_{\text{tail}}$$

i Question 5.2 – Input-Referred Offset

Question: Derive the input-referred offset voltage of a differential pair due to threshold voltage mismatch ΔV_{th} and transconductance mismatch $\Delta g_{\text{m}}/g_{\text{m}}$.

Solution:

The input-referred offset voltage has two components:

$$\sigma\{V_{\text{os}}\} = \sqrt{\sigma^2\{\Delta V_{\text{th}}\} + \left(\frac{V_{\text{GS}} - V_{\text{th}}}{2}\right)^2 \cdot \sigma^2\left\{\frac{\Delta g_{\text{m}}}{g_{\text{m}}}\right\}}$$

Or equivalently:

$$\sigma\{V_{\text{os}}\} = \sqrt{\sigma^2\{\Delta V_{\text{th}}\} + \left(\frac{V_{\text{od}}}{2}\right)^2 \cdot \sigma^2\left\{\frac{\Delta(W/L)}{(W/L)}\right\}}$$

Note that the offset is a *random* quantity, so what these expressions give is its standard deviation, not a single deterministic value.

To minimize offset:

- Use large device area (mismatch $\propto 1/\sqrt{WL}$)
- Use moderate $g_{\text{m}}/I_{\text{D}}$ (not too low overdrive)
- Match layout carefully (common-centroid, dummy devices)

23.6 Basic 5-Transistor OTA

i Question 6.1 – DC Gain Derivation

Question: Derive the dc voltage gain of an unloaded basic 5-transistor OTA with differential pair (M_1, M_2), current mirror load (M_3, M_4), and tail current source (M_5).

Solution:

The small-signal analysis yields:

$$A_0 = \frac{v_{\text{out}}}{v_{\text{in,dm}}} = \frac{g_{m1,2}}{g_{ds2} + g_{ds4}}$$

where:

- $g_{m1,2}$ is the transconductance of the input transistors
- g_{ds2} is the output conductance of the NMOS input transistor
- g_{ds4} is the output conductance of the PMOS load transistor

This can be rewritten as:

$$A_0 = \frac{g_{m1,2}}{g_{ds2}} \cdot \frac{1}{1 + g_{ds4}/g_{ds2}} = \frac{(g_m/g_{ds})_{1,2}}{1 + g_{ds4}/g_{ds2}}$$

For equal output conductances: $A_0 \approx \frac{(g_m/g_{ds})_{1,2}}{2}$

i Question 6.2 – Bandwidth and GBW

Question: For a 5T-OTA driving a load capacitance C_L , derive the dominant pole frequency and the gain-bandwidth product (GBW).

Solution:

Dominant pole: The output node has total capacitance C_L (assuming $C_L \gg$ parasitic capacitances) and total conductance $g_{ds2} + g_{ds4}$:

$$f_p = \frac{g_{ds2} + g_{ds4}}{2\pi C_L}$$

Gain-bandwidth product:

$$\text{GBW} = A_0 \cdot f_p = \frac{g_{m1,2}}{g_{ds2} + g_{ds4}} \cdot \frac{g_{ds2} + g_{ds4}}{2\pi C_L} = \frac{g_{m1,2}}{2\pi C_L}$$

Note that GBW is independent of the output conductances and depends only on g_m and C_L .

Design implication: For a given GBW requirement and load capacitance:

$$g_{m1,2} = 2\pi \cdot \text{GBW} \cdot C_L$$

i Question 6.3 – Unity-Gain Buffer Accuracy

Question: A 5T-OTA with dc gain $A_0 = 50$ dB is configured as a unity-gain buffer. Calculate the closed-loop gain error.

Solution:

For a unity-gain buffer (100% feedback):

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{A_0}{1 + A_0}$$

With $A_0 = 50$ dB = 316:

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{316}{317} = 0.9968$$

Gain error:

$$\epsilon = 1 - \frac{A_0}{1 + A_0} = \frac{1}{1 + A_0} \approx \frac{1}{A_0} = \frac{1}{316} = 0.32\%$$

For higher accuracy, the dc gain must be increased (e.g., using cascode structures).

23.7 Improved (Telescopic) OTA

i Question 7.1 – Gain Enhancement with Cascodes

Question: How does adding cascode transistors to a 5T-OTA improve the dc gain? Derive the new gain expression.

Solution:

With cascode transistors (M_{2C} , M_{4C}) added:

$$A_0 = \frac{g_{m1,2}}{g_{out,n} + g_{out,p}}$$

where:

$$g_{out,n} = g_{ds2} \cdot \frac{g_{ds,2C}}{g_{m,2C}} \quad \text{and} \quad g_{out,p} = g_{ds4} \cdot \frac{g_{ds,4C}}{g_{m,4C}}$$

Therefore:

$$A_0 \approx \frac{g_{m1,2}}{g_{ds2} \cdot \frac{g_{ds,2C}}{g_{m,2C}} + g_{ds4} \cdot \frac{g_{ds,4C}}{g_{m,4C}}}$$

If all transistors have similar g_m/g_{ds} :

$$A_0 \approx \frac{(g_m/g_{ds})^2}{2}$$

Gain improvement: Factor of g_m/g_{ds} compared to simple 5T-OTA.

i Question 7.2 – Output Swing

Question: What is the output voltage swing limitation of a telescopic OTA? Compare with a folded-cascode topology.

Solution:

Telescopic OTA output swing:

$$V_{\text{out,max}} = V_{\text{DD}} - V_{\text{ds,sat,M4}} - V_{\text{ds,sat,M4C}}$$

$$V_{\text{out,min}} = V_{\text{ds,sat,M2}} + V_{\text{ds,sat,M2C}} + V_{\text{ds,sat,M5C}} + V_{\text{ds,sat,M5}}$$

Total swing: $V_{\text{DD}} - 6 \cdot V_{\text{ds,sat}}$

Folded-cascode OTA output swing:

$$V_{\text{out,max}} = V_{\text{DD}} - 2 \cdot V_{\text{ds,sat}}$$

$$V_{\text{out,min}} = 2 \cdot V_{\text{ds,sat}}$$

Total swing: $V_{\text{DD}} - 4 \cdot V_{\text{ds,sat}}$

Key difference: The folded-cascode OTA allows a higher output swing and has a wider input common-mode range at the cost of increased power consumption; the telescopic OTA has limited input common-mode range and smaller swing, but only one current path.

23.8 Cascode Stage

i Question 8.1 – Output Impedance

Question: Derive the output impedance looking into the drain of a cascode transistor, assuming the source is connected to a current source with output resistance $r_{ds,CS}$.

Solution:

Using small-signal analysis with test voltage v_{test} at the drain:

$$g_{out} = \frac{i_{test}}{v_{test}} = \frac{g_{ds} \cdot G_S}{G_S + g_m + g_{ds}}$$

where $G_S = 1/r_{ds,CS} = g_{ds,CS}$ is the source conductance.

For $g_m \gg g_{ds}$ and $g_m \gg G_S$:

$$g_{out} \approx \frac{g_{ds} \cdot G_S}{g_m} = g_{ds,CS} \cdot \frac{g_{ds}}{g_m}$$

Therefore:

$$r_{out} = \frac{1}{g_{out}} = r_{ds,CS} \cdot \frac{g_m}{g_{ds}} = r_{ds,CS} \cdot (g_m/g_{ds})$$

Conclusion: The cascode increases the output impedance by a factor equal to the intrinsic gain (g_m/g_{ds}).

i Question 8.2 – Input Impedance

Question: Calculate the input impedance looking into the source of a cascode transistor when its drain is connected to a low-impedance load.

Solution:

With drain shorted to ac ground ($G_D \rightarrow \infty$):

$$g_{in} = \frac{(g_m + g_{ds}) \cdot G_D}{g_{ds} + G_D} \approx g_m + g_{ds} \approx g_m$$

Therefore: $Z_{in} \approx 1/g_m$

This low input impedance makes the cascode an effective “current buffer” that isolates the high-impedance current source from the output node variations.

23.9 Biasing and Bandgap Reference

i Question 9.1 – Bandgap Principle

Question: Explain the principle of a bandgap voltage reference. Why does the output voltage equal approximately 1.2 V?

Solution:

A bandgap reference combines two voltages with opposite temperature coefficients, usually derived from a bipolar transistor:

1. V_{BE} (CTAT): $\frac{\partial V_{BE}}{\partial T} \approx -2 \text{ mV/K} < 0$

2. ΔV_{BE} (PTAT): $\Delta V_{BE} = \frac{kT}{q} \cdot \ln\left(\frac{J_1}{J_2}\right)$, where $\frac{\partial(\Delta V_{BE})}{\partial T} = \frac{k}{q} \cdot \ln\left(\frac{J_1}{J_2}\right) > 0$

Reference voltage:

$$V_{\text{ref}} = V_{BE} + K \cdot \Delta V_{BE}$$

where K is chosen such that the temperature coefficients cancel:

$$\frac{\partial V_{\text{ref}}}{\partial T} = \frac{\partial V_{BE}}{\partial T} + K \cdot \frac{\partial(\Delta V_{BE})}{\partial T} = 0$$

At the zero-TC point, V_{ref} equals the extrapolated bandgap voltage of silicon at 0 K:

$$V_{\text{ref}} = V_{g0} \approx 1.205 \text{ V}$$

i Question 9.2 – PTAT Current

Question: Design a PTAT (Proportional To Absolute Temperature) current source. What determines the temperature coefficient?

Solution:

A PTAT current is generated by forcing ΔV_{BE} across a resistor:

$$I_{PTAT} = \frac{\Delta V_{BE}}{R} = \frac{kT}{qR} \cdot \ln\left(\frac{J_1}{J_2}\right) = \frac{kT}{qR} \cdot \ln(N)$$

where $N = J_1/J_2$ is the current density ratio (often implemented by area ratio).

Temperature coefficient:

$$\frac{\partial I_{PTAT}}{\partial T} = \frac{k \ln(N)}{qR}$$

$$\frac{1}{I_{PTAT}} \frac{\partial I_{PTAT}}{\partial T} = \frac{1}{T} \approx +3300 \text{ ppm/K at } 300 \text{ K}$$

The TC is determined by:

- Current density ratio N (affects magnitude)
- Resistor value R (affects magnitude)
- Temperature coefficient of R (should be low for accurate PTAT behavior)

23.10 Noise Analysis

i Question 10.1 – MOSFET Thermal Noise

Question: Write the expression for the thermal noise current of a MOSFET in saturation. What is the noise excess factor γ ?

Solution:

Thermal noise current spectral density:

$$\overline{i_n^2} = 4kT\gamma g_{d0} [\text{A}^2 / \text{Hz}]$$

where:

- $k = 1.38 \times 10^{-23}$ J/K is Boltzmann's constant
- T is absolute temperature
- γ is the noise excess factor
- g_{d0} is the zero-bias drain conductance ($\approx g_m$ in saturation and $\approx g_{ds}$ in triode)

Noise excess factor γ :

- Long-channel theory: $\gamma = 2/3$
- Short-channel devices: $\gamma > 2/3$ (can be 1–2 for deep submicron)
- Depends on bias point (increases at lower g_m/I_D)

Input-referred noise voltage:

$$\overline{v_{n,in}^2} = \frac{\overline{i_n^2}}{g_m^2} = \frac{4kT\gamma}{g_m} [\text{V}^2 / \text{Hz}]$$

i Question 10.2 – OTA Output Noise

Question: Derive the total output noise of a 5T-OTA in a unity-gain buffer configuration with load capacitance C_L .

Solution:

The integrated output noise (kT/C noise):

$$V_{n,out,rms}^2 = \frac{kT}{C_L} \left(2\gamma_{1,2} + 2\gamma_{3,4} \frac{g_{m3,4}}{g_{m1,2}} \right)$$

Analysis:

1. Input pair (M_1, M_2): Each contributes $\gamma_{1,2}$, total factor $2\gamma_{1,2}$
2. Load pair (M_3, M_4): Each contributes $\gamma_{3,4} \cdot g_{m3,4}/g_{m1,2}$ when referred to the input

To minimize noise:

- Increase C_L (but reduces bandwidth; increase g_m to compensate for a given GBW)
- Minimize $g_{m3,4}/g_{m1,2}$ ratio (keep load g_m low)
- Use large input transistors (reduces flicker noise)

23.11 Mismatch and Variability

i Question 11.1 — Pelgrom's Law

Question: State Pelgrom's law for MOSFET threshold voltage mismatch. How should transistors be sized to achieve 1 mV offset in a differential pair (assuming $A_{vth} = 5 \text{ mV} \cdot \mu\text{m}$)?

Solution:

Pelgrom's law:

$$\sigma\{\Delta V_{th}\} = \frac{A_{vth}}{\sqrt{WL}}$$

where A_{vth} is a technology-dependent constant (typical: 3–10 mV·μm for modern CMOS).

For 1 mV offset: With $A_{vth} = 5 \text{ mV} \cdot \mu\text{m}$:

$$1 \text{ mV} = \frac{5 \text{ mV} \cdot \mu\text{m}}{\sqrt{WL}}$$

$$\sqrt{WL} = 5 \mu\text{m} \Rightarrow WL = 25 \mu\text{m}^2$$

For example: $W = 5 \mu\text{m}$, $L = 5 \mu\text{m}$ or $W = 10 \mu\text{m}$, $L = 2.5 \mu\text{m}$

Note: Using longer L also improves intrinsic gain but reduces speed.

i Question 11.2 – Monte Carlo Analysis

Question: Explain the difference between process corners (SS, TT, FF, etc.) and Monte Carlo mismatch simulation. When should each be used?

Solution:

Process corners:

- Model systematic variations across wafer/lot
- All transistors on a chip shift together
- Corners: SS (slow-slow), FF (fast-fast), TT (typical), SF, FS
- Used for: Worst-case timing, power, functionality

Monte Carlo mismatch:

- Models random variations between adjacent devices
- Each device varies independently
- Based on statistical distributions (Pelgrom)
- Used for: Offset, matching-critical circuits

When to use:

Analysis	Process Corners	Monte Carlo
Operating point range	✓	
Power consumption	✓	
Timing margins	✓	
Input offset		✓
Current mirror accuracy		✓
CMRR, PSRR	✓	✓
Yield estimation	✓	✓

Best practice: Combine both – run Monte Carlo at each process corner.

23.12 Design Problems

i Question 12.1 – OTA Design

Question: Design a 5T-OTA to meet the following specifications using gm/ID methodology:

- GBW = 10 MHz with $C_L = 5$ pF
- DC gain > 50 dB
- Power supply: $V_{DD} = 1.5$ V
- Power consumption < 100 μ W

Solution:

Step 1: Calculate required g_m

$$g_m = 2\pi \cdot \text{GBW} \cdot C_L = 2\pi \cdot 10 \text{ MHz} \cdot 5 \text{ pF} = 314 \mu \text{ S}$$

Step 2: Choose g_m/I_D and calculate current

For a moderate speed/power trade-off, choose $g_m/I_D = 15 \text{ V}^{-1}$:

$$I_D = \frac{g_m}{g_m/I_D} = \frac{314 \mu \text{ S}}{15 \text{ V}^{-1}} = 21 \mu \text{ A}$$

Total tail current: $I_{\text{tail}} = 2 \times 21 \mu \text{ A} = 42 \mu \text{ A}$

Power: $P = V_{DD} \cdot I_{\text{tail}} = 1.5 \text{ V} \times 42 \mu \text{ A} = 63 \mu \text{ W}$

Step 3: Check dc gain requirement

Required: $A_0 > 50 \text{ dB} = 316$

$$A_0 = \frac{g_m}{g_{ds2} + g_{ds4}} = \frac{(g_m/g_{ds})}{2}$$

(assuming equal g_{ds})

Need $g_m/g_{ds} > 632$. From lookup tables at $g_m/I_D = 15$, $L = 1 \mu \text{ m}$: $g_m/g_{ds} \approx 38$

Not sufficient! Options:

- Increase L to 10 $\mu \text{ m}$ (increases g_m/g_{ds} to ~75, still not sufficient)
- Use cascode topology
- Accept lower gain – this we will do for this simple design

Step 4: Size transistors

Using lookup tables: I_D/W at $g_m/I_D = 15$, $L = 10 \mu \text{ m}$ $\approx 0.2 \mu \text{ A}/\mu \text{ m}$

$$W_{1,2} = \frac{I_D}{I_D/W} = \frac{21 \mu \text{ A}}{0.2 \mu \text{ A}/\mu \text{ m}} = 105 \mu \text{ m}$$

We assume for this simple design that the current mirror load (M_3 , M_4) is sized to have $g_{m3,4} \approx g_{m1,2}$, so $W_{3,4} = 105 \mu \text{ m}$ as well.

i Question 12.2 – Current Mirror Design

Question: Design a cascode current mirror to provide $I_{\text{out}} = 50 \mu\text{ A}$ from $I_{\text{ref}} = 10 \mu\text{ A}$. Minimize the output compliance voltage while achieving $r_{\text{out}} > 5 \text{ M } \Omega$.

Solution:

Current ratio: $I_{\text{out}}/I_{\text{ref}} = 5$

Step 1: Choose $g_{\text{m}}/I_{\text{D}}$ for minimum $V_{\text{ds,sat}}$

High $g_{\text{m}}/I_{\text{D}} = 18 \text{ V}^{-1}$: $V_{\text{ds,sat}} \approx 2/18 = 111 \text{ mV}$

Step 2: Calculate required $g_{\text{m}}/g_{\text{ds}}$

For simple current mirror: $r_{\text{out}} = 1/g_{\text{ds}}$

Required: $r_{\text{out}} > 5 \text{ M } \Omega$ at $I_{\text{D}} = 50 \mu\text{ A} \rightarrow g_{\text{ds}} < 200 \text{ nS}$

At $g_{\text{m}}/I_{\text{D}} = 18$: $g_{\text{m}} = 18 \times 50 \mu\text{ A} = 900 \mu\text{ S} \rightarrow g_{\text{m}}/g_{\text{ds}} > 900 \mu\text{ S}/200 \text{ nS} = 4500$

This is too high for a single device $\rightarrow$ need cascode!

Step 3: Cascode design

With cascode: $r_{\text{out}} \approx g_{\text{m,casc}} \cdot r_{\text{ds,casc}} \cdot r_{\text{ds,main}} \approx (g_{\text{m}}/g_{\text{ds}})^2/g_{\text{m}}$

For $g_{\text{m}}/g_{\text{ds}} = 75$ (achievable with $L = 10 \mu\text{ m}$) at $g_{\text{m}} = 900 \mu\text{ S}$: $r_{\text{out}} = 75^2/900 \mu\text{ S} = 5625/0.0009 \text{ S} \approx 6.25 \text{ M } \Omega$

This meets the requirement of $r_{\text{out}} > 5 \text{ M } \Omega$

Conclusion: A standard cascode current mirror with $L \approx 10 \mu\text{ m}$ achieving $g_{\text{m}}/g_{\text{ds}} \approx 75$ is sufficient.

Step 4: Minimum output voltage (using high-swing current mirror)

$V_{\text{out,min}} = 2 \times V_{\text{ds,sat}} \approx 2 \times 111 \text{ mV} = 222 \text{ mV}$

i Question 12.3 – Common-Source Amplifier

Question: Design a common-source amplifier for a $50\ \Omega$ measurement system with voltage gain $|A_v| = 10$ (20 dB). The amplifier should be matched to $50\ \Omega$ at input and output.

Solution:

Matching conditions:

- Input: the gate of the MOSFET is essentially capacitive, so the $50\ \Omega$ input match has to be provided by a shunt resistor $R_{sh} = 50\ \Omega$ from the gate to ground
- Output: the drain load resistor is set to $R_D = 50\ \Omega$ so that the amplifier presents a matched source impedance; together with the $50\ \Omega$ load this gives $R_{load,eff} = R_D \parallel R_L = 25\ \Omega$

Voltage gain (from the gate to the load):

$$A_v = -g_m \cdot R_{load,eff} = -g_m \times 25\ \Omega$$

For $|A_v| = 10$:

$$g_m = \frac{10}{25\ \Omega} = 400\ \text{mS}$$

This is very high! At $g_m/I_D = 10$: $I_D = 40\ \text{mA}$ (excessive)

Alternative approach: Use a common-source stage followed by a source follower.

23.13 Short Conceptual Questions

i Question 13.1

Question: Why is it important to use “unit elements” when designing matched current mirrors?

Solution: Unit elements ensure:

1. Same device dimensions and orientation
2. Identical local environment (dummy devices)
3. Common-centroid layout possible
4. Gradient cancellation
5. Consistent parasitic effects

i Question 13.2

Question: What is the purpose of a tail current source in a differential pair?

Solution: The tail current source:

1. Sets the total bias current (operating point)
2. Provides high impedance to common-mode signals (improves CMRR)
3. Creates a virtual ground at the tail node for differential signals
4. Rejects power supply variations

i Question 13.3

Question: Why does the GBW of an OTA depend only on g_m and C_L , not on the output resistance?

Solution:

$$\text{GBW} = A_0 \cdot f_p = \frac{g_m}{g_{\text{out}}} \cdot \frac{g_{\text{out}}}{2\pi C_L} = \frac{g_m}{2\pi C_L}$$

The output conductance g_{out} appears in both the gain ($A_0 = g_m/g_{\text{out}}$) and the pole frequency ($f_p = g_{\text{out}}/(2\pi C_L)$), so it cancels out. This is a fundamental property of single-pole systems.

i Question 13.4

Question: What is the advantage of a folded-cascode over a telescopic OTA?

Solution:

1. **Wider input common-mode range:** Input pair can swing from rail to rail (if NMOS and PMOS input stage are combined)
2. **Decoupled input and output dc levels:** More flexibility in biasing
3. **High output swing:** Using cascoded output transistors then swing is $V_{DD} - 4V_{ds,\text{sat}}$

Disadvantage: Higher power consumption (needs additional bias current for folding transistors)

i Question 13.5

Question: Why is flicker noise more important in the input stage of an OTA than in the load stage?

Solution:

1. Input stage noise is amplified by the full gain of the stage, so it appears at the output essentially undiminished when referred back to the input
2. The noise of the load devices, referred back to the input, is scaled by the ratio of transconductances $g_{m3,4}/g_{m1,2}$ – see Equation 25
3. Since we design for $g_{m3,4} < g_{m1,2}$ anyway (to minimize thermal noise), the load contribution is suppressed by that same ratio
4. For good noise performance: Large input devices (more area $\rightarrow$ less flicker noise); the load devices can be smaller, but only within the limits set by the $g_{m3,4}/g_{m1,2}$ ratio

i Question 13.6

Question: Explain why the regulated cascode achieves higher output impedance than a simple cascode.

Solution:

In a regulated cascode, an auxiliary amplifier forces the drain voltage of the main current source transistor to be constant:

1. Simple cascode: $r_{\text{out}} \approx g_m \cdot r_{\text{ds,casc}} \cdot r_{\text{ds,main}}$
2. Regulated cascode: $r_{\text{out}} \approx A_{\text{aux}} \cdot g_m \cdot r_{\text{ds,casc}} \cdot r_{\text{ds,main}}$

The auxiliary amplifier gain A_{aux} provides an additional multiplication factor, dramatically increasing output impedance. This is essentially applying negative feedback to stabilize the drain voltage.

Bibliography

- [1] P. R. Gray, P. J. Hurst, S. H. Lewis, and R. G. Meyer, *Analysis and Design of Analog Integrated Circuits*. Wiley, 2009.
- [2] B. Razavi, *Design of Analog CMOS Integrated Circuits*. McGraw-Hill, 2017.
- [3] W. M. C. Sansen, *Analog Design Essentials*. Springer, 2006.
- [4] C. Hu, *Modern Semiconductor Devices for Integrated Circuits*. Pearson, 2010.
- [5] Y. Tsividis and C. McAndrew, *Operation and Modeling of the MOS Transistor*. Oxford University Press, 2011.
- [6] H. Pretl and M. Eberlein, “Fifty Nifty Variations of Two-Transistor Circuits: A tribute to the versatility of MOSFETs,” *IEEE Solid-State Circuits Magazine*, vol. 13, no. 3, pp. 38–46, 2021, [Online]. Available: <https://iic-jku.github.io/fifty-nifty-circuits/>

- [7] L. W. Nagel, "SPICE2: A Computer Program to Simulate Semiconductor Circuits," Doctoral dissertation, 1975. [Online]. Available: <http://www2.eecs.berkeley.edu/Pubs/TechRpts/1975/9602.html>
- [8] J. M. Manley and H. E. Rowe, "Some General Properties of Nonlinear Elements-Part I. General Energy Relations," *Proceedings of the IRE*, vol. 44, no. 7, pp. 904–913, 1956, doi: 10.1109/jrproc.1956.275145.
- [9] B. Jakoby, "Achieving signal power amplification using energetically passive devices," *e&i Elektrotechnik und Informationstechnik*, vol. 139, no. 6, pp. 477–484, 2022, doi: 10.1007/s00502-022-01046-9.
- [10] J. C. Maxwell, *A Treatise on Electricity and Magnetism*, vol. 1. Clarendon Press, 1873.
- [11] F. Silveira, D. Flandre, and P. Jespers, "A $\frac{m}{T}$ based methodology for the design of CMOS analog circuits and its application to the synthesis of a silicon-on-insulator micropower OTA," *IEEE Journal of Solid-State Circuits*, vol. 31, no. 9, pp. 1314–1319, 1996, doi: 10.1109/4.535416.
- [12] P. G. A. Jespers and B. Murmann, *Systematic Design of Analog CMOS Circuits: Using Pre-Computed Lookup Tables*. Cambridge University Press, 2017.
- [13] S. Dorrer, "An Open-Source Adaptive Event-Based ADC for Bio-Signal Acquisition in 130\,nm CMOS." [Online]. Available: <https://epub.jku.at/obvulihs/content/titleinfo/12118473?query=dorrer>
- [14] T. C. Carusone, D. Johns, and K. Martin, *Analog Integrated Circuit Design*. Wiley, 2011.
- [15] E. H. Hellen, "Verifying the diode–capacitor circuit voltage decay," *American Journal of Physics*, vol. 71, no. 8, pp. 797–800, Aug. 2003, doi: 10.1119/1.1578070.
- [16] S. Rosenstark, "Loop gain measurement in feedback amplifiers," *International Journal of Electronics*, vol. 57, no. 3, pp. 415–421, 1984, doi: 10.1080/00207218408938921.
- [17] R. D. Middlebrook, "Measurement of loop gain in feedback systems," *International Journal of Electronics*, vol. 38, no. 4, pp. 485–512, 1975, doi: 10.1080/00207217508920421.
- [18] M. Tian, V. Visvanathan, J. Hantgan, and K. Kundert, "Striving for small-signal stability," *IEEE Circuits and Devices Magazine*, vol. 17, no. 1, pp. 31–41, 2001.
- [19] M. Neag, R. Oneț, I. Kovács, and P. Mărtari, "Comparative Analysis of Simulation-Based Methods for Deriving the Phase- and Gain-Margins of Feedback Circuits With Op-Amps," *IEEE Transactions on Circuits and Systems I: Regular Papers*, vol. 62, no. 3, pp. 625–634, 2015, doi: 10.1109/TCSI.2014.2370151.
- [20] A. Sheikholeslami, "Noise and Distortion, Part IV [Circuit Intuitions]," *IEEE Solid-State Circuits Magazine*, vol. 17, no. 3, pp. 29–31, 2025, doi: 10.1109/MSSC.2025.3582840.
- [21] R. Sarpeshkar, T. Delbruck, and C. Mead, "White noise in MOS transistors and resistors," *IEEE Circuits and Devices Magazine*, vol. 9, no. 6, pp. 23–29, 1993, doi: 10.1109/101.261888.
- [22] R. Widlar, "Some Circuit Design Techniques for Linear Integrated Circuits," *IEEE Transactions on Circuit Theory*, vol. 12, no. 4, pp. 586–590, 1965, doi: 10.1109/tct.1965.1082512.
- [23] A. D. Blumlein, "Thermionic Valve Amplifying Circuit." 1937.

- [24] B. Murmann, *Analysis and Design of Elementary MOS Amplifier Stages*. NTS Press, 2013.
- [25] B. Kamath, R. Meyer, and P. Gray, "Relationship between frequency response and settling time of operational amplifiers," *IEEE Journal of Solid-State Circuits*, vol. 9, no. 6, pp. 347–352, 1974, doi: 10.1109/JSSC.1974.1050527.
- [26] A. Kay and C. Wells, "Technical White Paper - Operational Amplifier Stability Theory and Compensation Methods." [Online]. Available: <https://www.ti.com/lit/wp/sboa626/sboa626.pdf>
- [27] M. Pelgrom, A. Duinmaijer, and A. Welbers, "Matching properties of MOS transistors," *IEEE Journal of Solid-State Circuits*, vol. 24, no. 5, pp. 1433–1439, 1989, doi: 10.1109/JSSC.1989.572629.
- [28] R. J. Baker, "Bad Circuit Design 3 - Compensating an Op-Amp." [Online]. Available: https://cmosedu.com/cmos1/bad_design/bad_design3/bad_design_3.htm
- [29] B. Razavi, "The Low Dropout Regulator [A Circuit for All Seasons]," *IEEE Solid-State Circuits Magazine*, vol. 11, no. 2, pp. 8–13, Jan. 2019, doi: 10.1109/mssc.2019.2910952.
- [30] B. Hosticka, "Improvement of the gain of MOS amplifiers," *IEEE Journal of Solid-State Circuits*, vol. 14, no. 6, pp. 1111–1114, 1979, doi: 10.1109/jssc.1979.1051324.
- [31] V. V. Ivanov and I. M. Filanovsky, *Operational Amplifier Speed and Accuracy Improvement*. Kluwer Academic Publishers, 2004.
- [32] R. Widlar, "New developments in IC voltage regulators," *IEEE Journal of Solid-State Circuits*, vol. 6, no. 1, pp. 2–7, Feb. 1971, doi: 10.1109/jssc.1971.1050151.
- [33] K. E. Kuijk, "A precision reference voltage source," *IEEE Journal of Solid-State Circuits*, vol. 8, no. 3, pp. 222–226, Jun. 1973, doi: 10.1109/JSSC.1973.1050378.
- [34] A. Brokaw, "A simple three-terminal IC bandgap reference," *IEEE Journal of Solid-State Circuits*, vol. 9, no. 6, pp. 388–393, Dec. 1974, doi: 10.1109/JSSC.1974.1050532.
- [35] H. Banba *et al.*, "A CMOS bandgap reference circuit with sub-1-V operation," *IEEE Journal of Solid-State Circuits*, vol. 34, no. 5, pp. 670–674, 1999, doi: 10.1109/4.760378.
- [36] M. Eberlein, G. Panagopoulos, and H. Pretl, "A 40nW, Sub-IV Truly 'Digital' Reverse Bandgap Reference Using Bulk-Diodes in 16nm FinFET," *2018 IEEE Asian Solid-State Circuits Conference (A-SSCC)*, pp. 99–102, Nov. 2018, doi: 10.1109/asscc.2018.8579306.
- [37] B. Razavi, "The Design of a Low-Voltage Bandgap Reference [The Analog Mind]," *IEEE Solid-State Circuits Magazine*, vol. 13, no. 3, pp. 6–16, 2021, doi: 10.1109/mssc.2021.3088963.
- [38] C. Mangelsdorf, "Miller's Secret [Shop Talk: What you didn't Learn in School]," *IEEE Solid-State Circuits Magazine*, vol. 17, no. 1, pp. 21–27, 2025, doi: 10.1109/MSSC.2024.3503792.
- [39] C. Mangelsdorf, "Miller's Wrong Half-Plane Zero [Shop Talk: What you didn't Learn in School]," *IEEE Solid-State Circuits Magazine*, vol. 17, no. 2, pp. 19–29, 2025, doi: 10.1109/MSSC.2025.3562109.

- [40] A. Sheikholeslami, "Miller's Theorem [Circuit Intuitions]," *IEEE Solid-State Circuits Magazine*, vol. 7, no. 3, pp. 9–10, 2015, doi: 10.1109/mssc.2015.2446457.
- [41] S. Pavan, "An Alternative Approach to Bode's Noise Theorem," *IEEE Transactions on Circuits and Systems II: Express Briefs*, vol. 66, no. 5, pp. 738–742, 2019, doi: 10.1109/TCSII.2019.2907860.